

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK
KEMENTERIAN PENDIDIKAN TINGGI**

JABATAN KEJURUTERAAN ELEKTRIK

PEPERIKSAAN AKHIR

SESI JUN 2016

DEE2023: SEMICONDUCTOR DEVICES

**TARIKH : 01 NOVEMBER 2016
MASA : 8.30 AM - 10.30 AM (2 JAM)**

Kertas ini mengandungi **SEPULUH (10)** halaman bercetak.

Bahagian A: Objektif (10 soalan)

Bahagian B: Struktur (4 soalan)

Bahagian C: (2 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

SECTION A: 10 MARKS
BAHAGIAN A: 10 MARKAH

INSTRUCTION:

This section consists of TEN (10) objective questions. Mark your answers in the OMR form provided.

ARAHAH:

Bahagian ini mengandungi SEPULUH (10) soalan objektif. Tandakan jawapan anda di dalam borang OMR yang disediakan.

CLO1
C1

1. How many electrons are present at the outmost orbit of Silicon?

Berapakah bilangan electron pada orbit paling luar bagi Silikon?

- A. 4
- B. 14
- C. 8
- D. 3

CLO1
C2

2. In pure state, Silicon has the properties of _____.

Dalam keadaan tulen, Silikon mempunyai ciri-ciri _____.

- A. a conductor
pengalir
- B. no charge at all
tiada cas
- C. an insulator
penebat
- D. a semiconductor
bahan separuh pengalir

- CLO1
C1
3. When a diode in its non-conducting state it has _____.
Apabila diod dalam keadaan tidak berfungsi ia _____.

- A. a very low resistance
mempunyai rintangan yang rendah
- B. a very high resistance
mempunyai rintangan yang tinggi
- C. no resistance at all
tiada rintangan langsung
- D. forward bias connection
dalam sambungan pincang hadapan

- CLO2
C3
4. The zone in a semiconductor diode where there are no free charge carriers exist is known as _____.

Zon di dalam diod separuh pengalir apabila tiada pembawa cas wujud dikenali sebagai _____.

- A. anode region
bahagian anod
- B. cathode region
bahagian katod
- C. depletion region
bahagian kesusutan
- D. reverse biased
pincang balikan

- CLO1
C1
5. Define DC beta, β .

Takrifkan beta, β AT.

- A. The ratio of DC emitter current to DC collector current
Nisbah bagi arus pemancar AT dengan arus pemungut AT
- B. The ratio of DC emitter current to DC base current
Nisbah bagi arus pemancar AT dengan arus tapak AT
- C. The ratio of DC collector current to DC base current
Nisbah bagi arus pemungut AT dengan arus tapak AT
- D. The ratio of DC collector current to DC emitter current
Nisbah bagi arus pemungut AT dengan arus pemancar AT

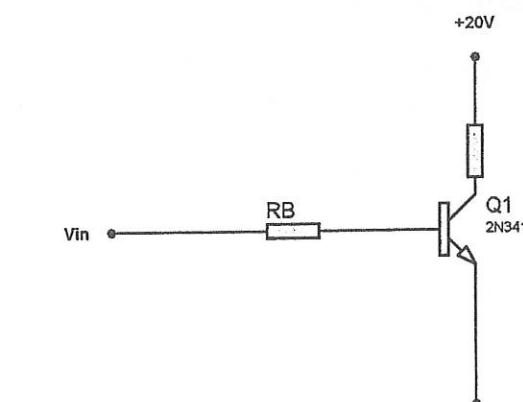


Figure A6 / Rajah A6

- A. 18mA
- B. 8mA
- C. 1.8mA
- D. 7.92mA

- CLO1
C2
7. Describe the function of feedback in an amplifier.

Terangkan fungsi suapbalik di dalam penguat.

- A. Control its output
mengawal keluaran
- B. Increase its gain
meningkatkan gandaan
- C. Decrease its input impedance
mengurangkan galangan masukan
- D. Stabilize its gain
menstabilkan gandaan

- CLO1
C1
8. Which JFET amplifier is also known as a source follower?
Penguat JFET yang manakah dikenali sebagai pengikut sumber?

- A. Common source amplifier
Penguat punca sepunya
- B. Common gate amplifier
Penguat get sepunya
- C. Common Channel amplifier
Penguat saluran sepunya
- D. Common drain amplifier
Penguat saliran sepunya

- CLO1
C2
9. In what mode can a D-MOSFET operate?

- D-MOSFET boleh beroperasi dalam ragam apa?*
- A. Enhancement modes
Ragam peningkatan
 - B. Decreasing modes
Ragam penurunan
 - C. Constant modes
Ragam tetap
 - D. Saturation Modes
Ragam tepu

- CLO1
C1
10. SCR ON state condition depends on _____.

- Syarat keadaan ON bagi SCR bergantung kepada _____.*
- A. gate current
arus Gate
 - B. cathode current
arus katod
 - C. anode current
arus anod
 - D. None of the above
Tiada satu diatas

SECTION B: 60 MARKS
BAHAGIAN B: 60 MARKAH

INSTRUCTION:

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi EMPAT (4) soalan berstruktur. Jawab SEMUA soalan.

QUESTION 1

SOALAN 1

- CLO1
C1
- a) List **THREE (3)** types of electrical material classification.

Senaraikan TIGA (3) jenis klasifikasi bahan elektrik.

[3 marks]
[3 markah]

- CLO1
C2
- b) In semiconductor materials, atoms link together with one another sharing their outer electrons. These links are called covalent bonds. Draw the covalent bonds for silicon atoms.

Dalam semikonduktor, atom-atom bercantum dengan satu sama lain melalui perkongsian elektron luar mereka. Pautan ini dikenali sebagai ikatan kovalen. Lukiskan ikatan kovalen untuk atom-atom silikon.

[5 marks]
[5 markah]

- CLO2
C3
- c) Forward bias is the condition that allows current through the PN junction. Illustrate the connection of PN junction during forward bias and describe **TWO (2)** conditions that allow forward bias to occur.

Pincang hadapan adalah keadaan yang membenarkan arus melalui simpang PN. Ilustrasikan sambungan simpang pn semasa pincang hadapan dan jelaskan DUA (2) syarat yang membolehkan pincang hadapan berlaku.

[7 marks]
[7 markah]

CLO1
C1**QUESTION 2**
SOALAN 2

- a) List THREE (3) operation regions for JFET as stated in IV Characteristic Curve.

Senaraikan TIGA (3) kawasan operasi untuk JFET seperti yang terdapat di dalam Lengkuk Ciri IV.

[3marks]
[3 markah]

CLO2
C2

- b) Explain FIVE (5) differences between FET and BJT.

Terangkan LIMA (5) perbezaan di antara FET dan BJT.

[5 marks]
[5 markah]

CLO2
C3

- c) By using a suitable diagram, illustrate how PMOS and NMOS function as switches.

Dengan menggunakan rajah yang bersesuaian, ilustrasikan bagaimana PMOS dan NMOS berfungsi sebagai suis.

[7 marks]
[7 markah]

QUESTION 3
SOALAN 3CLO1
C2

- a) Explain TWO (2) concepts of feedback in multistage amplifier.

Terangkan DUA (2) konsep suapbalik di dalam penguat berbilang peringkat.

[3 marks]
[3 markah]

CLO2
C3

- b) Draw the circuit for Transformer Coupling configuration and explain TWO (2) advantages of the coupling.

Lukiskan litar untuk konfigurasi gandingan pengubah dan jelaskan DUA(2) kelebihan gandingan tersebut.

[6 marks]
[6 markah]

CLO2
C3

- c) For a multistage amplifier, stage 1 has an input voltage, $V_{in1} = 20mV$ and an output voltage, $V_{out1} = 1V$. Stage 2 has an output voltage, $V_{out2} = 10V$. Calculate the gain of stage 1, gain of stage 2 and overall gain of this amplifier.

Bagi sebuah penguat berbilang peringkat, voltan input bagi peringkat 1 adalah $V_{in1} = 20mV$ dan voltan keluarannya ialah $V_{out1} = 1V$. Bagi Peringkat 2 mempunyai voltan keluaran $V_{out2} = 10V$. Kirakan gandaan peringkat 1, gandaan peringkat 2 dan gandaan keseluruhan bagi penguat ini.

[6 marks]
[6 markah]

QUESTION 4
SOALAN 4CLO1
C1

- a) Draw the schematic symbol and physical structure for DIAC.

Lukiskan simbol skematik dan struktur fizikal untuk DIAK.

[3 marks]
[3 markah]

CLO1
C3

- b) Figure B4 (b) shows a DIAC application as a heat control circuit. Interpret how the circuit works.

Rajah B4 (b) menunjukkan aplikasi DIAK sebagai litar pengawal suhu. Interpretasikan bagaimana litar tersebut berfungsi.

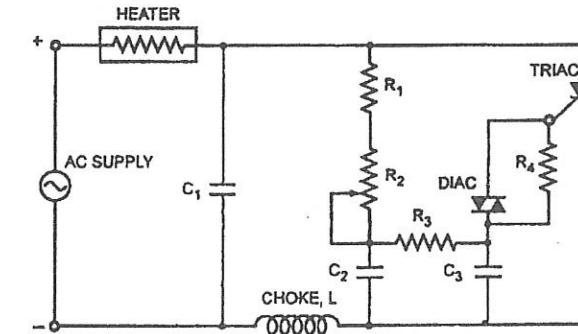


Figure B4 (b) / Rajah B4 (b)

[5 marks]
[5 markah]

CLO2
C3

- c) Draw an IV Characteristic Curve of Silicon Controlled Rectifier (SCR) and explain the characteristics for forward and reverse bias.

Lukiskan cirian IV bagi Penerus Silikon Terkawal (SCR) dan terangkan ciri-ciri pincangan hadapan dan pincangan songsang.

[7 marks]
[7 markah]

SECTION C: 30 MARKS
BAHAGIAN C: 30 MARKAH
INSTRUCTION:

This section consists of TWO (2) essay questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi DUA (2) soalan eseи. Jawab SEMUA soalan.

QUESTION 1**SOALAN 1**

CLO2
C3

Referring to circuit as shown in Figure C1, calculate V_B , V_E , I_C , V_C and V_{CE} . Draw and label the DC load line that includes saturation region, cutoff region and Q point.

Merujuk kepada litar yang ditunjukkan dalam Rajah C1, kirakan V_B , V_E , I_C , V_C dan V_{CE} dan lakarkan garis beban AT termasuklah kawasan tepu, kawasan potong dan titik Q .

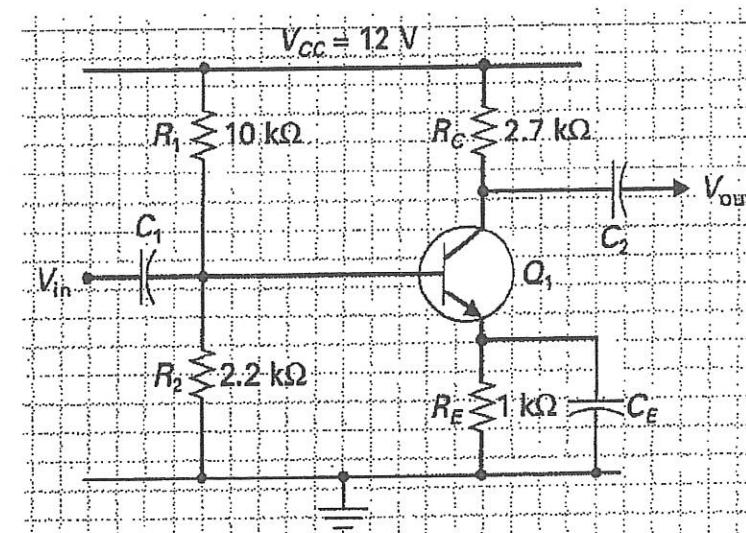


Figure C1 / Rajah C1

[15 marks]
[15 markah]

QUESTION 2
SOALAN 2

CLO2
C3

Sketch a center-tapped full-wave rectifier circuit with the direction of current flow. The load resistor, R_L is $2\text{k}\Omega$ and the diode resistance is neglected. If the peak to peak voltage across the secondary winding is 220V , calculate Output Voltage (V_o), Average Voltage (V_{avg}) and Average Current (I_{avg}).

Lakar gambarajah litar penerus gelombang penuh sadap tengah berserta arah pengaliran arusnya. Nilai rintangan beban, R_L ialah $2\text{k}\Omega$ dan rintangan diod diabaikan. Sekiranya bekalan voltan puncak ke puncak merentasi bahagian sekunder ialah 220V , kirakan Voltan Keluaran (V_o), Voltan Purata (V_{avg}) dan Arus Purata (I_{avg}).

[15 marks]
[15 markah]

SOALAN TAMAT