

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK
KEMENTERIAN PENDIDIKAN TINGGI**

JABATAN KEJURUTERAAN ELEKTRIK

**PEPERIKSAAN AKHIR
SESI JUN 2016**

DET2033: ELECTRICAL CIRCUITS

**TARIKH : 03 NOVEMBER 2016
MASA : 8.30 AM - 10.30 AM (2 JAM)**

Kertas ini mengandungi **DUA BELAS (12)** halaman bercetak.

Bahagian A: Objektif (10 soalan)

Bahagian B: Struktur (4 soalan)

Bahagian C: Esei (2 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

SECTION A : 10 MARKS
BAHAGIAN A : 10 MARKAH

INSTRUCTIONS:

This section consists of TEN (10) objective questions. Mark your answers in the OMR form provided.

ARAHAN :

Bahagian ini mengandungi **SEPULUH (10)** soalan objektif. Tandakan jawapan anda di dalam borang OMR yang disediakan.

- CLO1
C1
1. Select the source of alternating current (AC)

Pilih sumber bagi arus ulangalik (AU)

- A. Battery cell
Sel Bateri
- B. Solar cell
Sel solar
- C. AC generator
Penjana AU
- D. AC motor
Motor AU

- CLO1
C2
2. Identify the voltage across the inductance in an RL series circuit

Kenal pasti voltan merintangi aruhan dalam litar siri RL

- A. Current in phase with the source voltage.
Arus sefasa dengan Voltan bekalan
- B. Current lagging the source voltage by 90° .
Arus mengekor 90° Voltan bekalan
- C. Current leading the source voltage by 90° .
Arus mendulu voltan bekalan sebanyak 90° .
- D. Voltage leading the current by 90° .
Voltan mendulu Arus sebanyak 90°

	SULIT	DET2033: ELECTRICAL CIRCUITS	SULIT	DET2033: ELECTRICAL CIRCUITS
CLO1 C2	3. In a series resonant circuit, $V_C = 125\text{ V}$, $V_L = 125\text{ V}$, and $V_R = 40\text{ V}$. Calculate the value of the source voltage. <i>Dalam satu litar salunan siri, $V_C = 125\text{ V}$, $V_L = 125\text{ V}$, dan $V_R = 40\text{ V}$. Kira nilai voltan sumber.</i>		CLO1 C2	6. A 440V/110V transformer has 1000 turns on the primary winding. Calculate the number of turns on the secondary. <i>Sebuah transformer 440V/110V mempunyai 1000 belitan pada bahagian primer. Kira bilangan belitan pada bahagian sekunder.</i>
	A. 200V B. 125V C. 250V D. 40V			A. 550 B. 250 C. 4000 D. 25
CLO1 C2	4. Identify the neutral current in a three-phase system, when the loads are perfectly balanced. <i>Kenalpasti arus neutral dalam sistem tiga fasa bila beban dalam keadaan seimbang.</i>		CLO2 C3	7. Calculate the peak current through the $15\text{k}\Omega$ resistor if the rms voltage drop is 16V. <i>Kirakan nilai arus puncak melalui perintang $15\text{k}\Omega$ sekiranya voltan susut ppgd adalah 16V.</i>
	A. 0 A B. 2 A C. $\sqrt{3}$ A D. 9 A			A. 1.5mA B. 7.5mA C. 1.07mA D. 2.0mA
CLO1 C1	5. Following are the types of transformers EXCEPT; <i>Berikut adalah jenis-jenis pengubah KECUALI;</i>		CLO2 C3	8. Calculate the capacitive reactance of a $10\mu\text{F}$ capacitor when connected to a circuit of 50Hz frequency. <i>Kira regangan kapasitif bagi kapasitor $10\mu\text{F}$ apabila disambungkan kepada litar frekuensi 50Hz.</i>
	A. Center tapped transformer <i>Pengubah tap tengah.</i> B. Multiple winding transformer <i>Pengubah berbilang lilitan.</i> C. Auto transformer <i>Pengubah Auto.</i> D. Manual transformer <i>Pengubah manual</i>			A. $200.5\ \Omega$ B. $318.3\ \Omega$ C. $3.183\ \Omega$ D. $250.3\ \Omega$

	SULIT	DET2033: ELECTRICAL CIRCUITS		SULIT	DET2033: ELECTRICAL CIRCUITS
CLO2 C3	<p>9. A series circuit comprises an inductor of 2mH, a resistor of 50 ohms and a capacitor of 2 mF. Calculate the frequency at which this circuit will be at resonant.</p> <p><i>Satu litar sesiri terdiri dari 2mH peraruh, 50 ohms resistor dan 2 mF pemuat. Kira nilai frekuensi bagi litar ini jika iaanya dalam keadaan salun.</i></p> <p>A. 65.58 Hz B. 79.58 Hz C. 85.58kHz D. 82.58Hz</p>		CLO1 C1	<p>SECTION B : 60 MARKS BAHAGIAN B :60 MARKAH</p> <p>INSTRUCTIONS: This section consists of FOUR (4) structured questions. Answer ALL questions.</p> <p>ARAHAN: <i>Bahagian ini mengandungi EMPAT (4) soalan berstruktur. Jawab SEMUA soalan.</i></p> <p>QUESTION 1 SOALAN 1</p> <p>a) List TWO (2) laws related in generating of alternating current. <i>Senaraikan DUA (2) hukum yang berkaitan dengan penjanaan arus.</i></p> <p>[3 marks] [3 markah]</p> <p>b) Calculate the rms voltage of an average voltage of 24V. <i>Kirakan voltan ppgd daripada voltan purata 24V.</i></p> <p>[5 marks] [5 markah]</p> <p>c) The voltage in AC circuit is given by $V= 10 \sin 62.8t\text{ V}$. Calculate <i>Voltan dalam litar AU diberikan oleh $V = 10 \sin 62.8t\text{ V}$. Kira</i></p> <p>i) The frequency and period time <i>Frekuensi dan tempoh</i></p> <p>ii) The value of the voltage at $t=2\text{ms}$ <i>Nilai voltan pada ketika $t=2\text{ms}$</i></p> <p>[7 marks] [7 markah]</p>	
CLO2 C3	<p>10. A supply three-phase system delivers power to a load delta connection consisting of three 12Ω resistors. If the current 8 A is supplied to each load, calculate the total power supplied by the system.</p> <p><i>Satu bekalan sistem tiga fasa telah mengagihkan kuasa kepada beban sambungan delta yang terdiri dari tiga perintang 12Ω. Jika arus 8A mengalir pada setiap perintang, kira kuasa yang dibekalkan dari bekalan tersebut.</i></p> <p>A. 768 VA B. 900 VA C. 3.2 kVA D. 3.5 kVA</p>		CLO1 C2		
			CLO2 C3		

QUESTION 2**SOALAN 2**CLO1
C1

- a) Draw the graph showing the relation between frequency and resistance(R), inductive reactance (X_L) and capacitive reactance (X_C)

Lakarkan graf yang menunjukkan hubungan antara frekuensi dengan rintangan (R), kearuhan (X_L) dan kemudahan (X_C).

[3 marks]

[3 markah]

CLO1
C2

- b) Express in a phasor diagram showing the relationship between V_R , V_C , V_T , I_T , I_R and I_C for the following circuit.

Nyatakan dalam bentuk rajah phasor menunjukkan hubungan antara V_R , V_C , V_T , I_T , I_R dan I_C bagi litar berikut:

- i) Series RC circuit (I_T as reference)
Litar RC siri (I_T sebagai rujukan)
- ii) Parallel RC circuit (V_T as reference)
Litar RC selari (V_T sebagai rujukan)

[5 marks]

[5 markah]

CLO2
C3

- c) Referring to Figure B1, calculate:

Berdasarkan Rajah B1, kirakan:

- i) total impedance
jumlah galangan
- ii) total current
jumlah arus
- iii) voltage across inductor, L and capacitor, C
voltan merentasi peraruh, L dan pemuat, C

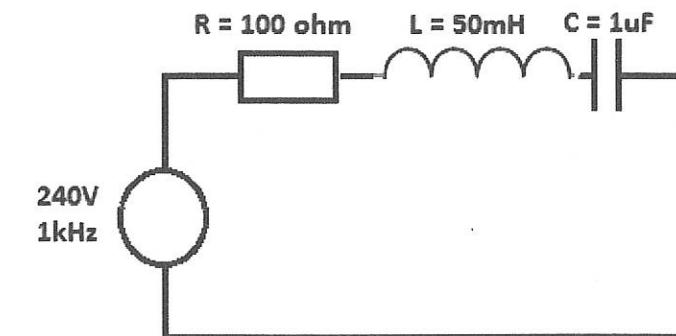


Figure B1 / Rajah B1

[7 marks]

[7 markah]

QUESTION 3**SOALAN 3**CLO1
C1

- a) List THREE (3) advantages of three phase system .

Senaraikan TIGA (3) kebaikan bagi sistem tiga fasa .

[3 marks]

[3 markah]

- CLO1
C2 b) Referring to Figure B2, determine the equation for the waveform, V_R , V_Y and V_B .
Merujuk kepada Rajah B2, kenalpasti persamaan bagi gelombang V_R , V_Y dan V_B .

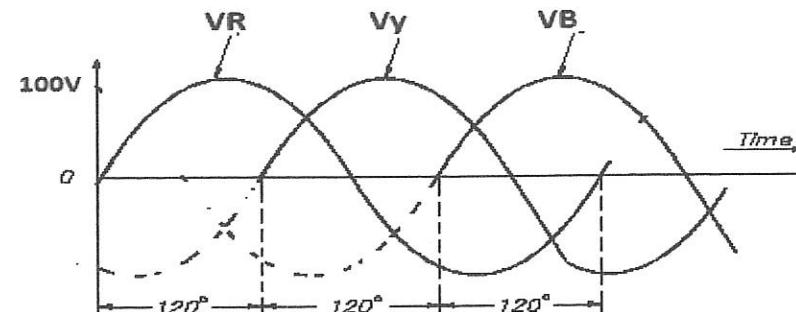


Figure B2 / Rajah B2

[5 marks]
[5 markah]

- CLO2
C3 c) Referring to Figure B3, a three phase supply with 415V, 50Hz was connected to balance load of 40Ω resistance and 0.1H inductance at each phase. If the load is connected in a form of star, calculate the line current (I_L) and the real power (P).

Merujuk kepada Rajah B3, satu bekalan tiga fasa 415V, 50Hz telah disambung kepada beban seimbang dengan perintang 40Ω dan aruhan 0.1H pada setiap fasa. Jika beban tersebut di sambung secara bintang, kirakan arus talian (I_L) dan kuasa sebenar (P).

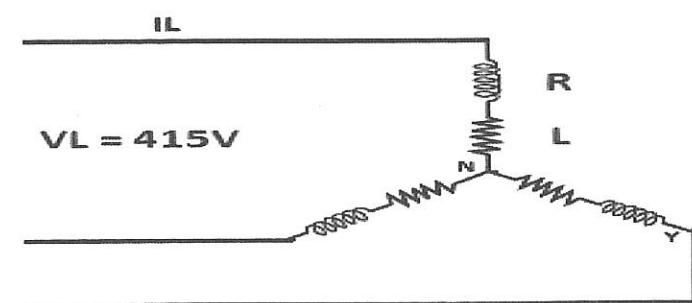


Figure B3 / Rajah B3

[7 marks]
[7 markah]

QUESTION 4
SOALAN 4

- CLO1
C1 a) List THREE (3) types of transformer
Senaraikan TIGA (3) jenis transformer

[3 marks]
[3 markah]


- CLO1
C2 b) The amount of mutual inductance depends upon several factors. Identify FIVE (5) factors that affect mutual inductance.

Jumlah aruhan saling bergantung kepada beberapa faktor. Kenal pasti LIMA (5) faktor yang mempengaruhi aruhan saling.

[5 marks]
[5 markah]

- CLO2
C3 c) Referring to Figure B4, calculate V_p , V_s , I_p and I_s .

Merujuk Rajah B4, kirakan V_p , V_s , I_p dan I_s .

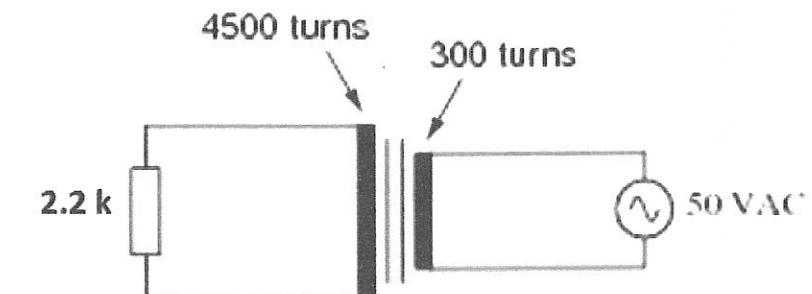Figure B4
Rajah B4

[7marks]
[7 markah]

SECTION C : 30 MARKS**BAHAGIAN C : 30 MARKAH****INSTRUCTIONS:**

This section consists of TWO (2) essay questions. Answer ALL questions.

ARAHAH:

Bahagian ini mengandungi TWO (2) soalan eseai. Jawab SEMUA soalan.

QUESTION 1**SOALAN 1**

CLO2
C3

Referring to Figure C1, calculate the line current I_1 , I_2 , I_T and draw the phasor diagram of currents. Calculate also the power factor, true power and the apparent power.

Merujuk kepada Rajah C1, kirakan I_1 , I_2 , I_T dan lukiskan rajah 'phasor' bagi arus-arus tersebut. Seterusnya kirakan faktor kuasa, kuasa sebenar dan kuasa ketara bagi litar tersebut.

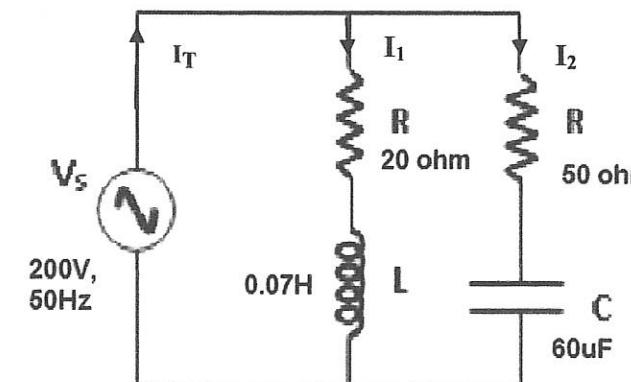


Figure C1 / Rajah C1

[15 marks]

[15 markah]

QUESTION 2**SOALAN 2**

CLO2
C3

A coil of 100Ω resistance and 60mH inductance are connected in series with a capacitance of $0.6\mu\text{F}$ across a 240V with the variable frequency supply. Calculate the upper cut-off frequency and lower cut-off frequency during resonance. Illustrate in detail the corresponding current waveform for all frequencies.

Satu gelung dengan rintangan 100Ω dan kearuhan 60mH disambung secara siri dengan kemantauan $0.6\mu\text{F}$ merentasi bekalan 240V , dengan frekuensi boleh laras. Kirakan nilai frekuensi terpotong atas dan frekuensi terpotong bawah ketika resonan. Lakar dengan lengkap gelombang arus untuk semua frekuensi yang berkaitan.

[15 marks]

[15 markah]

SOALAN TAMAT