

SECTION A : 40 MARKS
BAHAGIAN A : 40 MARKAH

INSTRUCTION:

This section consists of TEN (10) structured questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi SEPULUH (10) soalan berstruktur. Jawab SEMUA soalan.

CLO1 **QUESTION 1**

C3 Explain the function of power diode devices in conversion system.

SOALAN 1

Terangkan fungsi peranti elektronik kuasa dalam Sistem Penukaran.

[4 marks]
[4 markah]

CLO1 **QUESTION 2**

C3 Draw a voltage versus current graph for Silicon Control Rectifier (SCR) characteristic.

SOALAN 2

Lukis graf voltan melawan arus bagi ciri-ciri Control Rectifier (SCR).

[4 marks]
[4 markah]

CLO1 **QUESTION 3**

C3 State the effects of forward and reverse recovery time for power diode.

SOALAN 3

Nyatakan kesan pada Masa Pemulihan Hadapan dan Balikan bagi Diod Kuasa.

[4 marks]
[4 markah]

CLO1 **QUESTION 4**

C3 Draw a waveform for input voltage (V_{in}), and output voltage (V_{out}) for the Bridge Rectifier.

SOALAN 4

Lukiskan gelombang voltan masukan dan voltan keluaran bagi Litar Penerus Jejambat.

[4 marks]
[4 markah]

Kertas ini mengandungi **TUJUH (7)** halaman bercetak.

Bahagian A: Struktur (10 soalan)

Bahagian B: Esei (3 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SECTION B : 60 MARKS
BAHAGIAN B : 60 MARKAH

INSTRUCTION:

This section consists of THREE (3) essay questions. Answer ALL questions

ARAHAN:

Bahagian ini mengandungi **TIGA (3)** soalan ese. Jawab **semua** soalan.

CLO2
C4

QUESTION 1
SOALAN 1

- a. Determine the value of the current and voltage for the Half Wave Control Rectifier circuit with the value given:

Load resistance 10 ohm, frekeunsi 50 Hz, the power supply is 240 volt, the time for full cycle is 1 milli second, and firing angle $\alpha=45^\circ$.

- Design the circuit.
- Determine the output current, $i_o(t)$.
- Calculate the output voltage, $V_o(t)$
- Calculate values for V_{rms} and I_{rms} for output voltage and current.
- Draw the current and voltage waveform by referring to a. ii. and iii.

- a. Kenalpasti nilai voltan dan arus bagi litar tersebut dengan nilai yang diberi adalah seperti berikut:

Beban pada rintangan 10 ohm, frekeunsi 50 Hz, Kuasa bekalan 240 volt, dan masa untuk kitar lengkap adalah 1 mili saat, sudut ‘firing angle’ $\alpha=45^\circ$.

- Buat rekaan bagi Litar yang berkaitan.
- Kenalpasti arus keluaran, $i_o(t)$.
- Kirakan voltan keluaran, $V_o(t)$.
- Dapatkan nilai V_{rms} dan I_{rms} voltan dan arus keluaran.
- Lukiskan gelombang arus dan voltan merujuk pada jawapan a.ii dan iii.

(12 marks)
(12 markah)

CLO1
C3

QUESTION 5

Explain the **FOUR (4)** type of Rectifier Circuit in the conversion system.

SOALAN 5

Terangkan **FOUR (4)** jenis Litar Penerus dalam Sistem Penukar.

[4 marks]
[4 markah]

CLO1
C3

QUESTION 6

Briefly explain the function of step-up chopper.

SOALAN 6

Terangkan secara ringkas fungsi Pemenggal Langkah Naik.

[4 marks]
[4 markah]

CLO1
C3

QUESTION 7

Draw the buck-boost chopper circuit.

SOALAN 7

Lukiskan Litar Pemenggal Buck-Boost.

[4 marks]
[4 markah]

CLO1
C3

QUESTION 8

State two techniques that used to control output voltage of inverters.

SOALAN 8

Nyatakan **DUA (2)** teknik untuk mengawal voltan keluaran bagi Penyonsang.

[4 marks]
[4 markah]

CLO1
C3

QUESTION 9

Sketch the Star load that can be connected to the Three Phase Inverter.

SOALAN 9

Lukiskan beban Bintang yang boleh disambung pada Penyonsang Tiga Fasa.

[4 marks]
[4 markah]

CLO1
C3

QUESTION 10

State types of AC Voltage Controller.

SOALAN 10

Nyatakan jenis Pengawal Voltan AU.

[4 marks]
[4 markah]

- a. Litar Pemenggal Langkah Turun mengandungi transistor BJT, diod dan pearuh. Transistor T_1 pacu 'ON' untuk tempoh 0 hingga δT and 'OFF' untuk tempoh δT hingga T .
- Lukis dan label Litar Pemenggal Langkah Turun tersebut.
 - Lukis gambarajah litar Pemenggal Langkah Turun untuk memacu suis i_B , voltan merintangi transistor, V_{ab} , Arus melalui Kearuhan, i_L dan arus keluaran, i_o untuk tempoh 0 hingga T .
 - Lukis operasi litar yang berkaitan untuk tempoh 0 hingga T .
 - Lukis operasi litar yang berkaitan untuk tempoh δT hingga T .
 - Terangkan secara ringkas mengapa voltan keluaran Pemenggal Langkah Turun ini rendah dibandingkan dengan bekalan masukan.

[10 marks]
[10 markah]

QUESTION 3
SOALAN 3

- Design a 180° conduction type 3 phase Inverter was connected to the star load.
 - Draw and label the circuit diagram.
 - Draw the equivalent circuit for the transistor.
 - Draw the Red Phase Voltage and Line Voltage.
- Rekakan Penyonsang Tiga Fasa Kawalan 180° yang disambungkan pada beban Bintang.
 - Lukis dan labelkan Litar tersebut.
 - Lukis gambarajah litar setara bagi Transistor.
 - Lukis voltan Fasa Merah dan Voltan Talian bagi Penyonsang tersebut.

[12 marks]
[12 markah]

- b. A Three Phase Full Wave Fully Controlled Rectifier is connected to a 240 V, the resistive load is 10Ω and the inductive is 10 mH , and firing angle $\alpha=45^\circ$:
- Design the Rectifier Circuit.
 - Draw the voltage and current waveform.
 - Explain the operation of the circuit.
- b. Penerus Tiga Fasa Gelombang Penuh Terkawal disambungkan pada bekalan 240 Volt, Rintangan Beban 10Ω dan Kearuhan 10 mH dengan nilai firing angle, $\alpha=45^\circ$:
- Rekakan litar Penerus tersebut.
 - Lukis voltan keluaran dan votan masukan pada litar tersebut.
 - Terangkan operasi litar tersebut.

[8 marks]
[8 markah]

QUESTION 2
SOALAN 2

- A step down-chopper circuit is consist of BJT transistor, diode and inductor . The transistor T_1 is drive ON for the period of 0 to δT and OFF for the period δT to T .
 - Draw and label the circuit of step-down chopper.
 - Draw the waveform for drive of switch i_B , voltage across the transistor, V_{AB} , current through inductor, i_L and output current, i_o for the period from 0 to T .
 - Draw the related circuit operation for the period 0 to T .
 - Draw the related circuit operation for the period δT to T .
 - Briefly explain why voltage output of the step-down chopper is lower than supply voltage.

[10 marks]
[10 markah]

- b. Design a Single Phase Bidirectional AC Controller used to control the output of inductive motor with inductive load.
- i. Draw and labels the circuit.
 - ii. State the operation of the circuit by using the circuit b. i.
 - iv. Draw a waveform for output voltage and output current.
- b. *Rekakan Pengawal Arus ulangalik Satu Fasa Bidirectional digunakan untuk mengawal keluaran bagi motor dengan beban kearuhan.*
- i. *Lukis dan labelkan Litar tersebut.*
 - ii. *Nyatakan operasi litar dengan maklumat yang diberi di atas b.i.*
 - iii. *Lukis gelombang voltan keluaran dan arus keluaran.*

[8 marks]
[8 markah]

END OF QUESTIONS

SOALAN TAMAT