

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI
KEMENTERIAN PENGAJIAN TINGGI**

JABATAN KEJURUTERAAN ELEKTRIK

PENILAIAN ALTERNATIF

SESI DISEMBER 2020

DEE10013 : MEASUREMENT DEVICES

NAMA PENYELARAS KURSUS : KHAIRUL NAPISHAM BIN ABD RAZAK

KAEDAH PENILAIAN : PEPERIKSAAN ONLINE

JENIS PENILAIAN : ESEI BERSTRUKTUR (2 SOALAN)

TARIKH PENILAIAN : 30 JUN 2021

TEMPOH PENILAIAN : 1 JAM

LARANGAN TERHADAP PLAGIARISM (AKTA 174)

PELAJAR TIDAK BOLEH MEMPLAGIAT APA-APA IDEA, PENULISAN, DATA ATAU CIPTAAN ORANG LAIN. PLAGIAT ADALAH SALAH SATU PENYELEWENGAN AKADEMIK. SEKIRANYA PELAJAR DIBUKTIKAN MELAKUKAN PLAGIARISM, PENILAIAN BAGI KURSUS BERKENaan AKAN DIMANSUHKAN DAN DIBERI GRED F DENGAN NILAI MATA 0.

(RUJUK BUKU ARAHAN-ARAHAN PEPERIKSAAN DAN KAEDAH PENILAIAN (Diploma) EDISI 6, JUN 2019, KLAUSA 17.3)

SECTION A :50 MARKS
BAHAGIAN A : 50 MARKAH

INSTRUCTION:

This section consists of **TWO (2)** stuctured questions. Answer **ALL** questions.

ARAHAN :

Bahagian ini mengandungi **DUA (2)** soalan berstruktur. Jawab **SEMUA** soalan.

QUESTION 1**SOALAN 1**

- CLO1
C3 (a) The given value for each resistor in Figure A1(a), $R_1=7.5\text{K}\Omega$, $R_2=500\Omega$, $R_3=10\text{K}\Omega$ and total measure value of resistance is $22\text{K}\Omega$. Calculate the total resistance (actual value), absolute error, relative error, percentage of error and percentage of relative accuracy.

Diberi nilai untuk setiap perintang dalam rajah A1(a), $R_1=7.5\text{K}\Omega$, $R_2=500\Omega$, $R_3=10\text{K}\Omega$ dan jumlah rintang secara pengukuran adalah $22\text{K}\Omega$. Kirakan jumlah rintangan (nilai sebenar), ralat mutlak, ralat relatif, peratus ralat dan peratus ketepatan relatif.

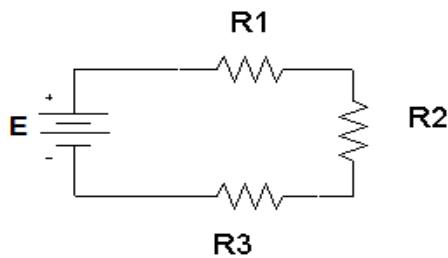


Diagram A1(a) / Rajah A1(a)

[10 marks]
[10 markah]

- CLO1
C3 (b) A moving coil instrument with an internal resistance of 50Ω and full scale deflection current of 4mA is used in the design of a DC voltmeter with voltage ranges of $0-10\text{V}$, $0-30\text{V}$ and $0-70\text{V}$. Draw the circuit of **THREE (3)** ranges DC voltmeter and calculate the value of R_s1 , R_s2 and R_s3 in the circuit.

*Sebuah alat gegelung bergerak mempunyai rintangan dalaman 50Ω dan arus pesongan penuh adalah 4mA digunakan untuk merekabentuk sebuah voltmeter AT yang mempunyai julat voltan $0-10\text{V}$, $0-30\text{V}$ dan $0-70\text{V}$. Lukis litar bagi **TIGA (3)** julat AT voltmeter ini dan kirakan nilai rintangan R_s1 , R_s2 dan R_s3 di dalam litar.*

[15 marks]
[15 markah]

QUESTION 2**SOALAN 2**

- CLO1
C3 (a) A Wheatstone bridge consists of four resistive arms connected together with source of electromagnetic field (e.m.f) and null detector. Draw and label with the aid of the bridge circuit diagram and derive the equation of unknown resistor, Rx. If given $R1=1.5K\Omega$, $R2=4.7K\Omega$ and $R3=12K\Omega$, calculate the value of Rx.

Tetimbang Wheatstone terdiri daripada empat lengan perintang yang disambung bersama dengan bekalan medan elektromagnetik (e.m.f) dan pengesan sifar.

Lukis dan label bersama gambarajah litar tetimbang tersebut dan terbitkan persamaan perintang tidak diketahui, Rx. Jika diberi $R1=1.5K\Omega$, $R2=4.7K\Omega$ dan $R3=12K\Omega$, kirakan nilai Rx.

[10 marks]
[10 markah]

- CLO1
C3 (b) Figure A2(b) shows the waveform at the oscilloscope screen. If the oscilloscope setting is set to Volt/div = 0.5V and Time/div = 0.5 μ s, calculate the voltage peak to peak (V_{p-p}), voltage peak (V_p), voltage Vrms (V_{rms}), periodic time (T), frequency (f) and phase shift between 2 waveform (θ)

Rajah A2(a) menunjukkan bentuk gelombang yang dihasilkan pada skrin osiloskop. Jika osiloskop disetkan untuk Volt/div = 0.5V dan Time/div = 0.5 μ s, kirakan, voltan puncak ke puncak (V_{p-p}), voltan puncak (V_p), voltan V_{rms} (V_{rms}) tempoh masa (T), frekuensi (f) dan perbezaan fasa 2 gelombang (θ)

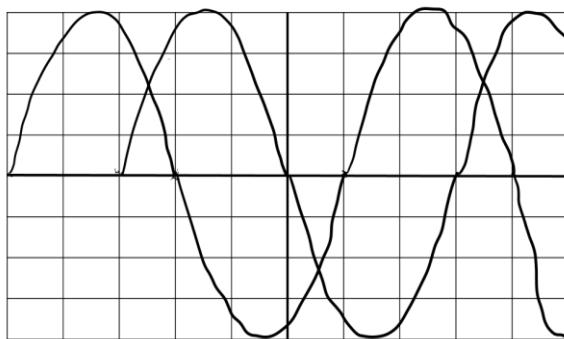


Figure A2(b) / Rajah A2(b)

[15 marks]
[15 markah]

SOALAN TAMAT