

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK
KEMENTERIAN PENDIDIKAN TINGGI**

JABATAN KEJURUTERAAN ELEKTRIK

**PEPERIKSAAN AKHIR
SESI JUN 2015**

DET2033 ELECTRICAL CIRCUIT

**TARIKH : 19 OKTOBER 2015
TEMPOH : 2.30 PM - 4.30 PM (2 JAM)**

Kertas ini mengandungi **SEBELAS (11)** halaman bercetak.

Bahagian A: Objektif (10 soalan)

Bahagian B: Struktur (4 soalan)

Bahagian C: Esei (2 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

SECTION A : 10 MARKS
BAHAGIAN A : 10 MARKAH

INSTRUCTION:

This section consists of TEN (10) objective questions. Mark your answers in the OMR form provided.

ARAHAN:

Bahagian ini mengandungi SEPULUH (10) soalan objektif. Tandakan jawapan anda di dalam borang OMR yang disediakan.

1. The basic equation of voltage sinusoidal waveform is expressed by:

CLO1
C1

Persamaan asas bagi bentuk gelombang sinusoid voltan dinyatakan oleh:.

- A. $E_m = e \sin (\omega t \pm \theta)$
- B. $E_m = e \sin (\omega t \times \theta)$
- C. $e = E_m \sin (\omega t \pm \theta)$
- D. $e = E_m \sin$

2. When the frequency is increased, the capacitive reactance will.....

CLO1
C2

Apabila nilai frekuensi meningkat, regangan kemuatan akan.....

- A. Increase
Meningkat
- B. Become constant
Tetap
- C. Decrease
Menurun
- D. remain unchanged
Tiada perubahan

	SULIT	DET2033: ELECTRICAL CIRCUITS	SULIT	DET2033: ELECTRICAL CIRCUITS
CLO1 C2	3. Identify the condition in a circuit when $XL = XC$. <i>Kenalpasti keadaan yang berlaku dalam litar apabila $XL = XC$.</i>	A. Draw maximum current. <i>Arus maksimum terhasil</i> B. Applied voltage is zero. <i>Voltage gunaan bersamaan dengan kosong.</i> C. At resonance. <i>Dalam keadaan resonan.</i> D. Draw minimum current. <i>Arus minima terhasil.</i>	CLO1 C2	6. Calculate the value of primary voltage required to ensure the turn ratio is 0.1 in which the secondary voltage is 9 V. <i>Berapakah nilai voltan yang diperlukan bagi memastikan nilai nisbah lilitan adalah 0.1 di mana voltan sekunder adalah 9 V.</i> A. 0.9 C. 90 B. 9 D. 900
CLO1 C2	4. Which of the following statements associated with 3-phase delta connected circuits is TRUE. <i>Antara pernyataan berikut yang berkaitan dengan litar 3 fasa sambungan delta adalah benar.</i>	A. Line voltage is equal to phase voltage <i>Voltan adalah bersamaan dengan voltan fasa</i> B. Line current is equal to phase current. <i>Arus talian adalah bersamaan arus fasa</i> C. Line voltage is $\sqrt{3}$ time of phase voltage <i>Voltan talian adalah $\sqrt{3}$ kali voltan fasa</i> D. Line currents are 60° apart. <i>Arus talian 60°</i>	CLO2 C3	7. An alternating voltage is given by $v = 150 \sin(200\pi t - 60^\circ)$ volts. Calculate the period of the given waveform. <i>Satu voltan ulang alik $v = 150 \sin(200\pi t - 60^\circ)$ volts. Kira nilai tempoh bagi gelombang tersebut.</i> A. 100s B. 10ms C. 0.1s D. 1s
CLO1 C1	5. Transformer basically works on, <i>Pengubah secara asasnya berkerja berdasarkan,</i>	A. Mutual induction C. Self induction <i>Aruhan saling Aruhan diri</i> B. Static induction D. None of these <i>Aruhan kekal Tiada berkenaan</i>	CLO2 C3	8. A 10Ω resistance, a 90 mH inductance, and a 0.015 uF capacitance are connected in series across an AC source. Calculate the impedance magnitude at the frequency of 1.2 kHz . <i>Satu rintangan 10Ω, aruhan 90mH dan kemuatan 0.015uF disambung secara sesiri melalui bekalan AU. Kirakan magnitud galangan pada frekuensi 1.2 kHz.</i> A. 816Ω B. 81.6Ω C. 8.16Ω D. $8.16\text{ k}\Omega$

CLO2
C3

9. A series circuit consists of a resistance of 4Ω , an inductance of 250 mH and a variable capacitance connected across a $100 \text{ V}, 60 \text{ Hz}$ supply. Calculate the capacitance required to give series resonance.

Satu litar siri dengan rintangan 4Ω , kearuan 250 mH dan kapasitor boleh laras disambung pada bekalan $100 \text{ V}, 60 \text{ Hz}$. Kirakan nilai kemauan yang akan menghasilkan keadaan resonan siri.

- A. $24.9 \mu\text{F}$
- B. $28.1 \mu\text{F}$
- C. $94.247 \mu\text{F}$
- D. 249.9 mF

CLO2
C3

10. Refer to Figure A10 below. Given $V_{\text{Line}} = 415 \text{ V}, 50\text{Hz}$. Calculate the line current.

Berdasarkan Rajah A10 dibawah. Diberi nilai $V_{\text{Line}} = 415 \text{ V}, 50 \text{ Hz}$. Kira arus talian.

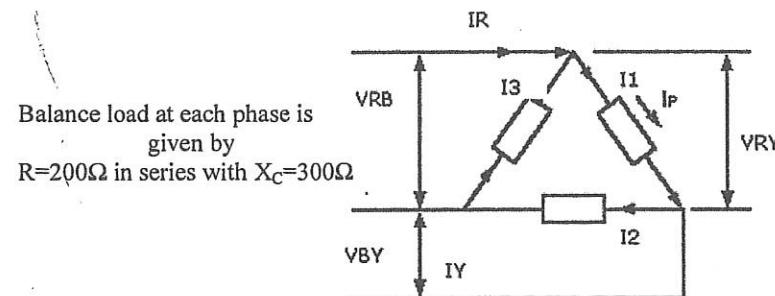


Figure A10 / Rajah A10

- A. 1.15A
- B. 2.05A
- C. 3.47A
- D. 4.53A

CLO1
C1CLO1
C2

SECTION B : 60 MARKS

BAHAGIAN B : 60 MARKAH

INSTRUCTION:

This section consists of FOUR (4) structured questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi EMPAT (4) soalan berstruktur. Jawab SEMUA soalan.

QUESTION 1 SOALAN 1

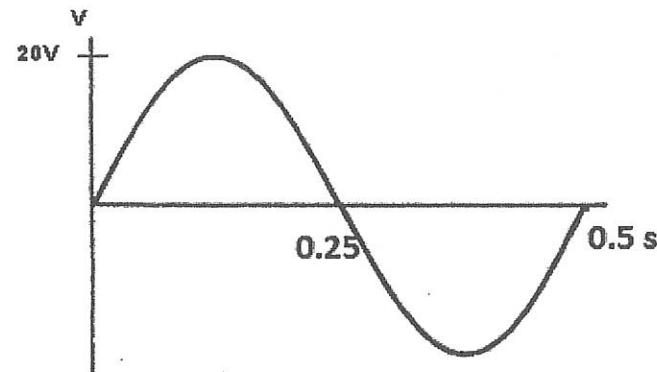


Figure B1(a)/ Rajah B1(a)

- a) Based on Figure B1(a);
Berdasarkan Rajah B1(a);

- i) Define the time period, T of a sine waveform.
Berikan tempoh masa, T bagi gelombang sinus.

[2 marks]
[2 markah]

- ii) Find the value of time period, T.
Dapatkan nilai tempoh masa, T.

[1 mark]
[1 markah]

- b) Based on Figure B1(a);
Berdasarkan Rajah B1(a);

- i) State the peak voltage, V_p .
Nyatakan nilai voltan puncak, V_p .

[2 marks]
[2 markah]

- ii) Write the sinusoidal waveform equation.

Tuliskan persamaan gelombang sinusoidal.

[3 marks]
[3 markah]

- CLO2
C3
c) An alternating voltage is given by $V(t) = 282.8 \sin 314t$ V. Find;

Satu voltan ulang alik mempunyai persamaan $V(t) = 282.8 \sin 314t$ V. Dapatkan nilai;

- i) average voltage (V_{avg}).

Voltan purata (V_{avg}).

[2 marks]
[2 markah]

- ii) frequency (f).

fekuensi (f).

[2 marks]
[2 markah]

- iii) the instantaneous voltage value when $t = 4$ ms.

Nilai voltan seketika apabila $t = 4$ ms.

[3 marks]
[3 markah]

QUESTION 2
SOALAN 2

CLO 1
C1

- a) Draw a phasor diagram to represent relation between current and voltage for a purely resistive AC circuit, a purely inductive AC circuit and a purely capacitive AC circuit.

Lakarkan gambarajah bagi menunjukkan hubungan antara arus dan voltan bagi litar AU rintangan tulen, litar AU induktif tulen dan litar AU kapasitif tulen.

[3 marks]
[3 markah]

CLO 1
C2

- b) A series circuit consist of resistance, $50\ \Omega$ and capacitance, $20\ \mu F$ are connected to supply 200 V, 100 Hz. Calculate:

Satu litar sesiri mengandungi perintang $50\ \Omega$ dan kapasitor $20\ \mu F$ disambungkan kepada bekalan kuasa 200 V, 100 Hz. Kirakan:

- The circuit impedance, Z
Galangan litar, Z
- The current flowing in the circuit
Arus yang mengalir dalam litar
- The phase angle between voltage and current
Beza fasa antara voltan dan arus

[5 marks]
[5 markah]

- CLO 2
C3
c) For the circuit shown in Figure B2 (c), determine the voltage V_1 and V_2 if the supply frequency is 1 kHz. Then calculate the supply voltage V .

Rujuk Rajah B2(c). Jika diberi frekuensi untuk litar tersebut adalah 1kHz , tentukan nilai Voltan pada V_1 dan V_2 . Kemudian kirakan voltan bekalan untuk litar tersebut.

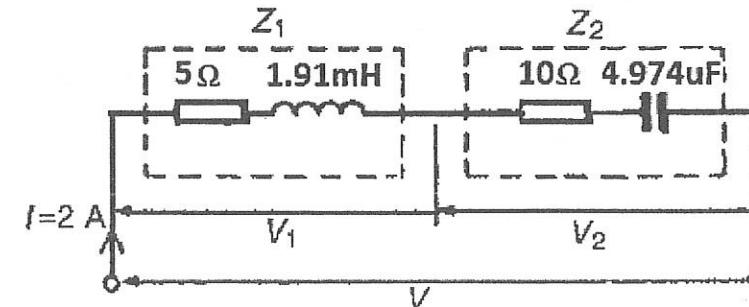


Figure B2(c) / Rajah B2(c)

[7 marks]
[7 markah]

QUESTION 3
SOALAN 3

- a) Explain the differential of connection method of Star (Y) and Delta (Δ) system.

Jelaskan perbezaan di antara sistem sambungan Bintang (Y) dan Delta (Δ).

[3 marks]
[3 markah]

CLO1
C1

CLO1
C2

CLO2
C3

- b) Three load resistance of $40\ \Omega$ is connected in delta to a 415 V, 3 ϕ . Determine phase voltage and phase current for the system.

Tiga beban rintangan $40\ \Omega$ disambung secara delta kepada 415 V, 3 ϕ . Tentukan voltan fasa dan arus fasa untuk sistem ini.

[5 marks]
[5 markah]

- c) Each phase in Delta (Δ) connected consists of $50\ \Omega$ resistor and connected in series with the capacitor, $50\ \mu F$. This three phase load is supplied with line voltage, 440 V and frequency, 50 Hz. Calculate the phase and line currents.

Setiap fasa di dalam sambungan Delta (Δ) terdiri daripada perintang $50\ \Omega$ yang disambung bersiri dengan kapasitor $50\ \mu F$. Beban tiga fasa ini dibekalkan dengan voltan talian 440 V dan frekuensi 50 Hz. Tentukan nilai arus fasa dan arus talian.

[7 marks]
[7 markah]

QUESTION 4
SOALAN 4

- a) Define transformer ratio

Definisikan nisbah pengubah.

[3marks]
[3 markah]

CLO1
C1

CLO1
C2

CLO1
C2

- b) Explain the characteristics of the step up transformer.

Terangkan ciri-ciri pengubah langkah naik.

[5marks]
[5 markah]

- c) By referring to Figure B4(c), calculate :

Merujuk pada Rajah B4(c), kirakan:

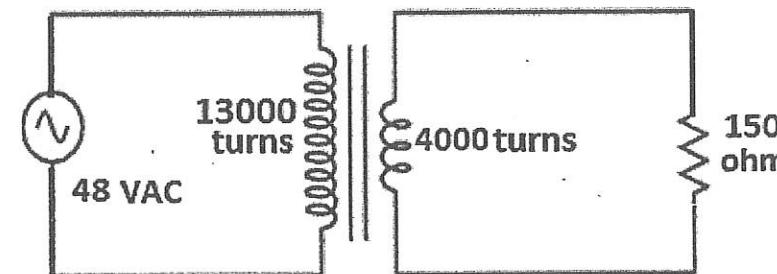


Figure B4(c) / Rajah B4(c)

- (i) Primary voltage

Voltan primer

[1 mark]

[1 markah]

- (ii) Secondary voltage

Voltan sekunder

[2 marks]

[2 markah]

- (iii) Secondary current

Arus sekunder

[2 marks]

[2 markah]

- (iv) Primary current

Arus primer

[2 marks]

[2markah]

SECTION C : 30 MARKS***BAHAGIAN C : 30 MARKAH*****INSTRUCTION:**

This section consists of TWO (2) essay questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi TWO (2) soalan esei. Jawab SEMUA soalan.

QUESTION 1

CLO2
C3

A series of RLC circuit has the following values $R = 8\Omega$, $C = 220 \mu F$ and $L = 25 \text{ mH}$. If the circuit has an instantaneous voltage of $V_s = 17 \sin(377t)$ V, determine the instantaneous current and draw its phasor diagram. What value will this current have at 5.0 m sec?

SOALAN 1

Satu litar siri RLC mengandungi nilai $R = 8 \Omega$, $C = 220 \mu F$ and $L = 25 \text{ mH}$. Sekiranya litar mempunyai nilai voltan seketika iaitu $V_s = 17 \sin(377t)$ V, carikan persamaan nilai arus seketika dan lukiskan gambarajah fasanya. Apakah nilai arus seketika pada 5.0 ms?

[15marks]
[15 markah]

QUESTION 2

CLO2
C3

A coil of inductance 120 mH are connected in series with a capacitance of $2 \mu F$ and a resistance of 12Ω across a 50 V and variable frequency supply. Determine the bandwidth of the circuit during the resonance and voltage across each component.

SOALAN 2

Satu gegelung aruhan 120 mH disambungkan secara siri dengan pemuat $2 \mu F$ dan perintang 12Ω merentasi bekalan 50V dan frekuensi bolehubah. Tentukan nilai jalur lebar litar tersebut dalam keadaan resonan dan nilai voltan pada setiap komponen.

[15 marks]
[15 markah]

END OF QUESTION

SOALAN TAMAT