

SULIT



BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK
KEMENTERIAN PENDIDIKAN TINGGI

JABATAN KEJURUTERAAN ELEKTRIK

PEPERIKSAAN AKHIR
SESI JUN 2015

ET502: POWER ELECTRONICS

TARIKH : 03 NOVEMBER 2015
TEMPOH : 11.15 AM – 1.15 PM (2 JAM)

Kertas ini mengandungi **SEBELAS (11)** halaman bercetak.

Bahagian A: Struktur (10 soalan)

Bahagian B: Esei (3 soalan)

Dokumen sokongan yang disertakan : Kertas Graf dan Rajah Gelombang
Tiga Fasa

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT



SECTION A : 40 MARKS
BAHAGIAN A : 40 MARKAH

INSTRUCTION:

This section consists of TEN (10) structured questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi SEPULUH (10) soalan struktur. Jawab SEMUA soalan.

CLO1
C1

QUESTION 1

P-channel MOSFET is a power electronic device. Draw and label

- (i) The symbol
- (ii) The structure diagram

SOALAN 1

P-channel MOSFET adalah peranti elektronik kuasa. Lukis dan labelkan

- (i) Simbol
- (ii) Gambarajah struktur

[4 marks]
[4 markah]

CLO1
C2

QUESTION 2

Give TWO (2) differences between SCR and BJT.

SOALAN 2

Berikan DUA (2) perbezaan antara SCR dan BJT.

[4 marks]
[4 markah]

CLO1
C1

QUESTION 3

Draw and label the I-V characteristic curve of TRIAC.

SOALAN 3

Lukiskan dan labelkan ciri lengkuk I-V untuk TRIAK.

[4 marks]
[4 markah]

CLO2
C3**QUESTION 4**

Produce the expression of the output voltage of single-phase full-wave controlled rectifier with resistive load. Given the input voltage, $V_i = V_m \sin \omega t$ and the triggering angle is $\omega t = \alpha$.

SOALAN 4

Terbitkan persamaan matematik bagi voltan keluaran bagi penerus terkawal gelombang penuh satu fasa dengan beban resistif. Diberi voltan masukan, $V_i = V_m \sin \omega t$ dan sudut picuan $\omega t = \alpha$.

[4 marks]
[4 markah]

CLO2
C3**QUESTION 5**

A single-phase controlled bridge rectifier has a 50Ω resistive load and an input voltage $240 \text{ V}_{\text{rms}}$, 50 Hz AC source. If the triggering angle, α is 45° , calculate:

- (i) the average load voltage, V_o
- (ii) the average load current, I_o

SOALAN 5

Satu penerus terkawal satu fasa jenis tetimbang mempunyai rintangan beban 50Ω dan voltan masukan $240 \text{ V}_{\text{rms}}$, 50 Hz AU. Jika sudut picuan, α adalah 45° , kirakan:

- (i) voltan keluaran purata, V_o
- (ii) arus keluaran purata, I_o

[4 marks]
[4 markah]

CLO2
C2**QUESTION 6**

Based on Diagram A6, with the aid of an output voltage waveform diagram, explain the operation of single-phase full-wave center-tap controlled rectifier with RL load for 0° firing angle.

SOALAN 6

Berdasarkan Rajah A6, dengan bantuan rajah bentuk gelombang voltan keluaran, terangkan operasi bagi penerus gelombang penuh terkawal satu fasa tap tengah dengan beban RL untuk sudut lengah 0° .

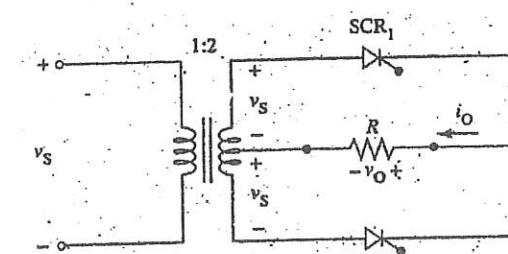


Diagram A6 / Rajah A6

[4 marks]
[4 markah]

CLO2
C3CLO2
C3**QUESTION 7**

Calculate the operation frequency, f for Buck Converter if t_{on} is 4ms, the input voltage is 80V and the output voltage is 40V.

SOALAN 7

Kirakan frekuensi, f ketika Penukar Langkah Turun beroperasi jika $t_{\text{on}} = 4 \text{ ms}$, voltan masukan 80 V dan voltan keluaran ialah 40 V .

[4 marks]
[4 markah]

CLO2
C3**QUESTION 8**

Sketch the waveform of inductor current, I_L of Buck Converter if $t_{\text{on}} = 50 \text{ ms}$ and $t_{\text{off}} = 20 \text{ ms}$.

SOALAN 8

Lakarkan bentuk gelombang arus peraruh, I_L bagi Penukar Langkah Turun untuk $t_{\text{on}} = 50 \text{ ms}$ dan $t_{\text{off}} = 20 \text{ ms}$.

[4 marks]
[4 markah]

CLO2
C3**QUESTION 9**

The single-phase full-bridge inverter has the DC supply voltage input of 120 V. The load resistance and inductive values are 8Ω and 2 mH respectively. Calculate the:

- (i) RMS output voltage, $V_{o,\text{rms}}$
- (ii) RMS output current, $I_{o,\text{rms}}$

SOALAN 9

Sebuah penyongsang satu fasa tetimbang penuh mempunyai voltan masukan AT 120 V . Nilai beban rintangan masing-masing adalah 8Ω dan 2 mH . Kirakan:

- (i) voltan keluaran pmkd, $V_{o,\text{pmkd}}$
- (ii) arus keluaran pmkd, $I_{o,\text{pmkd}}$

[4 marks]
[4 markah]

CLO2
C1**QUESTION 10**

List FOUR (4) applications of DC to AC converter in industries.

SOALAN 10

Senaraikan EMPAT (4) aplikasi penukar AT kepada AU di industri.

[4 marks]
[4 markah]

SECTION B : 60 MARKS
BAHAGIAN B : 60 MARKAH

INSTRUCTION:

This section consists of THREE (3) essay questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi TIGA (3) soalan ese. Jawab SEMUA soalan.

QUESTION 1**SOALAN 1**

CLO1
C3

- (a) The operation of an SCR can be explained based on the analogy of two-transistor model.

Operasi bagi SCR boleh diterangkan berdasarkan analogi model dua-transistor.

- (i) Draw and label the two-transistor model analogy circuit.

Lukis dan labelkan litar analogi model dua-transistor

[4 marks]
[4 markah]

- (ii) Explain the regenerative action using the two-transistor model.

Terangkan operasi penjanaan semula menggunakan model dua-transistor.

[6 marks]
[6 markah]

CLO2
C3

- (b) Figure B1 (b) is the circuit of three-phase half-wave controlled rectifier with resistive load. Based on the diagram, answer the questions below:

Rajah B1(b) adalah litar penerus separuh gelombang terkawal tiga fasa dengan beban resistif. Berdasar rajah tersebut, jawab soalan berikut:

- (i) Draw the waveform of input voltage, V_{in} and output voltage, V_{out} if the firing angle, $\alpha = 30^\circ$.

Lukiskan gelombang bagi voltan masukan, V_{in} dan voltan keluaran, V_{out} jika sudut picuan, $\alpha = 30^\circ$.

[6 marks]
[6 markah]

- (ii) If the input voltage $V_{in} = 132 \sin \omega t$, the firing angle $\alpha = 30^\circ$ and resistive load $R = 1\text{k}\Omega$, calculate the average output voltage ($V_{o,\text{avg}}$).

Sekiranya voltan masukan $V_{in} = 132 \sin \omega t$, sudut picuan $\alpha = 30^\circ$ dan beban resistif $R = 1\text{k}\Omega$, kirakan voltan keluaran purata ($V_{o,\text{purata}}$).

[4 marks]
[4 markah]

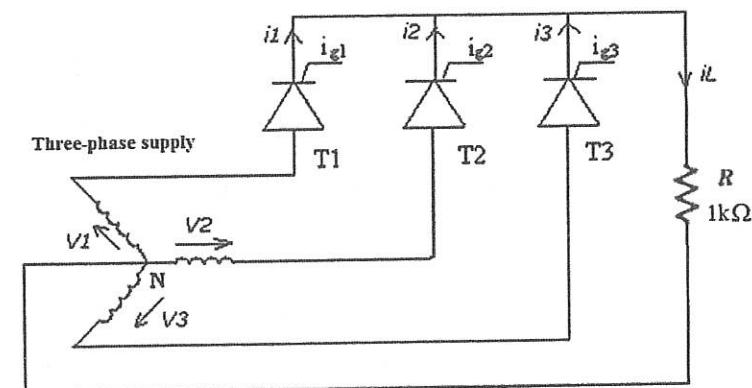


Figure B1(b) / Rajah B1(b)

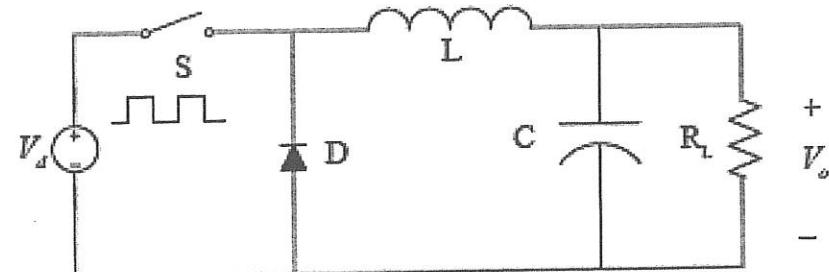
QUESTION 2
SOALAN 2


Figure B2 (a)/ Rajah B2 (a)

CLO2
C2

- (a) Figure B2 (a) shows the schematic circuit for chopper. Based on the figure above, answer the following;

Rajah B2 (a) menunjukkan litar skematik pemenggal. Berdasarkan gambarajah di atas, jawab soalan berikut;

- (i) State the above chopper type

Nyatakan jenis pemenggal diatas.

[1 mark]
[1 markah]

- (ii) Briefly explain the circuit operation

Terangkan secara ringkas operasi litar.

[6 marks]
[6 markah]

- (iii) Sketch and label the inductor current, I_L .

Lukis dan labelkan arus pearuh, I_L .

[3 marks]
[3 markah]

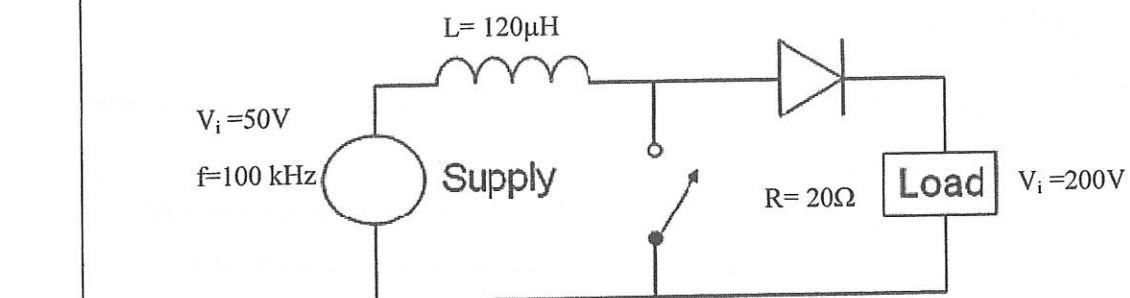


Figure B2 (b)/ Rajah B2(b)

- (b) Figure B2 (b) shows the schematic circuit for step-up chopper. Calculate:

CLO2
C3

Figure B2 (b) menunjukkan litar skematik pemenggal langkah naik. Kirakan:

- (i) the duty cycle, D

Kitar kerja, D

[2 marks]

[2 markah]

- (ii) the minimum and maximum inductor current; $I_{L\min}$ and $I_{L\max}$.

Arus peraruh minimum dan maksimum; $I_{L\min}$ dan $I_{L\max}$.

[5 marks]

[5 markah]

- (iii) If t_{on} is reduced to $6\mu s$ at constant frequency, calculate the new voltage output.

Jika t_{on} dikurangkan menjadi $6\mu s$ pada frekuensi yang sama, kirakan voltan keluaran yang baru

[3 marks]

[3 markah]

QUESTION 3
SOALAN 3


CLO2

C3

- (a) (i) By using transistors, draw a single-phase full-wave bridge inverter with inductive load circuit.

Dengan menggunakan transistor, lukiskan litar penyongsang tetimbang 1 fasa gelombang penuh dengan beban induktif.

[3 marks]
[3 markah]

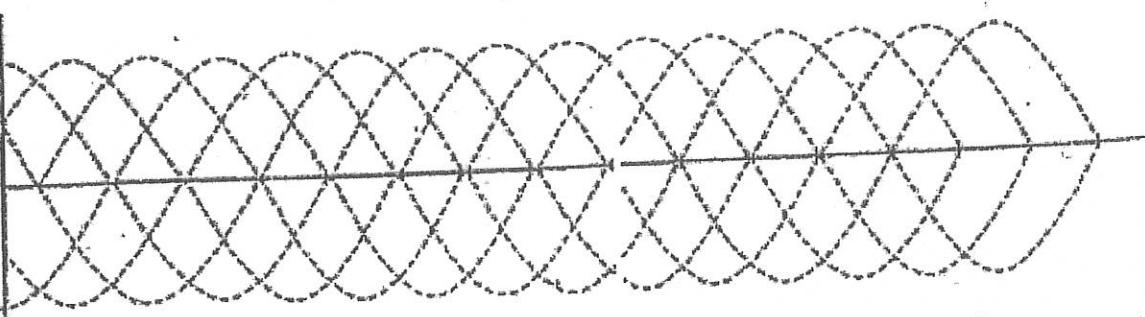


CLO2

C3

- (ii) Draw the waveform of input voltage, V_{in} ; output voltage, V_o ; and output current, I_o based on question (a) i.

Lukis bentuk gelombang untuk voltan masukan, V_{in} ; voltan keluaran, V_o ; dan arus keluaran berdasarkan soalan (a) i.

[4 marks]
[4 markah]

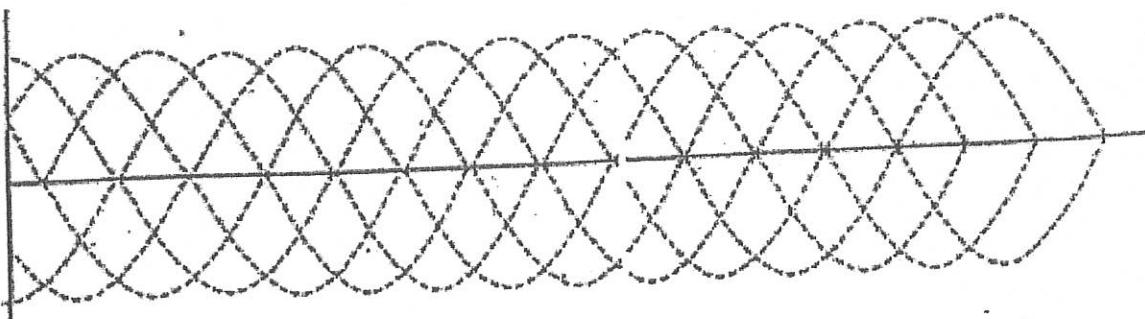


CLO2

C3

- (b) (i) By using SCR, draw a circuit of the three-phase full-wave bridge inverter with resistive load.

Dengan menggunakan SCR, lukiskan litar penyongsang tetimbang tiga fasa gelombang penuh dengan beban resistif.

[5 marks]
[5 markah]

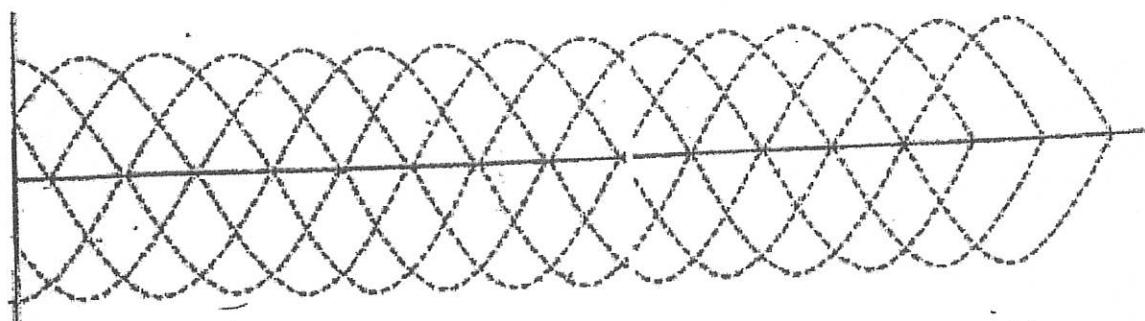

CLO2


C3

- (ii) Draw a full cycle output waveform for:
 (a) 120° conduction of V_{BN} and V_{BC}
 (b) 180° conduction of V_{CA} and I_{S4}

Lukiskan satu kitar gelombang keluaran untuk:

- (a) pengaliran 120° bagi V_{BN} , V_{BC} and I_{S3}
 (b) pengaliran 180° bagi V_{CN} , V_{CA} and I_{S4}

[8 marks]
[8 markah]

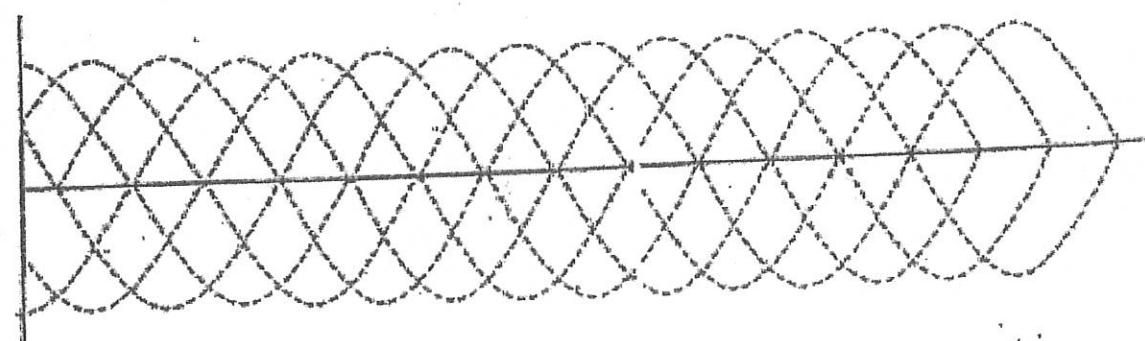

SOALAN TAMAT

