

**SULIT**



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN  
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI  
KEMENTERIAN PENGAJIAN TINGGI**

**JABATAN KEJURUTERAAN ELEKTRIK**

**PEPERIKSAAN AKHIR  
SESI II : 2021/2022**

**DET20033: ELECTRICAL CIRCUITS**

---

**TARIKH : 30 JUN 2022  
MASA : 8.30 PAGI – 10.30 PAGI (2 JAM)**

---

Kertas ini mengandungi **ENAM (6)** halaman bercetak.

Bahagian A: Struktur (3 soalan)

Bahagian B: Esei (1 soalan)

Dokumen sokongan yang disertakan : Tiada

---

**JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN**

(CLO yang tertera hanya sebagai rujukan)

**SULIT**

**SECTION A : 75 MARKS*****BAHAGIAN A : 75 MARKAH*****INSTRUCTION:**

This section consists of **THREE (3)** structured questions. Answer **ALL** questions.

***ARAHAN:***

*Bahagian ini mengandungi **TIGA (3)** soalan berstruktur. Jawab **SEMUA** soalan.*

**QUESTION 1*****SOALAN 1***

- CLO1      (a)      **TWO (2)** AC currents are presented by  $i_1 = 15 \sin \omega t$  A and  $i_2 = 18 \sin (\omega t - \frac{\pi}{5})$  A.  
 C3                  A. Attain sinusoidal expression to represent  $i_1 + i_2$ .

*Terdapat **DUA (2)** arus AC iaitu  $i_1 = 15 \sin \omega t$  A dan  $i_2 = 18 \sin (\omega t - \pi/5)$  A.  
 Dapatkan ungkapan sinusoidal untuk mewakili  $i_1 + i_2$ .*

[8 marks]

[8 markah]

- CLO1      (b)      An AC voltage is given by  $v = 156 \sin (50\pi t - 28.7^\circ)$  V. Calculate the peak-to-peak voltage value, the instantaneous voltage value at  $t = 6\mu s$ , the angular velocity, period and frequency.

*Voltan AC yang diberikan adalah  $v = 156 \sin (50\pi t - 28.7^\circ)$  V. Kirakan nilai voltan puncak ke puncak, nilai voltan seketika pada  $t = 6\mu s$ , halaju sudut, tempoh dan frekuensi.*

[8 marks]

[8 markah]

- CLO1      (c) An instantaneous current,  $i = 4.8 \sin \omega t$  A flows through a pure resistance of 5.95 k $\Omega$ . Calculate the dissipated power, the voltage across the resistor and sketch the sinusoidal waveform.
- Arus seketika,  $i = 4.8 \sin \omega t$  A mengalir melalui rintangan tulen bernilai 5.95 k $\Omega$ . Kira kuasa yang dilesapkan, voltan pada perintang dan lakarkan gelombang sinusoidal tersebut.*
- [9 marks]  
[9 markah]

**QUESTION 2****SOALAN 2**

- CLO1      (a) Derive the resonant frequency equation for the series R-L-C circuit in AC and sketch an appropriate graph of reactance as a function of frequency.
- Terbitkan persamaan frekuensi salun bagi litar sesiri R-L-C pada AC dan lakarkan graf regangan sebagai fungsi pada frekuensi yang bersetujuan*
- [8 marks]  
[8 markah]
- CLO1      (b) A 200 mH inductor, a 60  $\Omega$  resistor and a 20  $\mu\text{F}$  capacitor are connected in parallel across a 20V, variable frequency supply. Calculate the inductive reactance at resonance and the circuit Q- factor.
- Sebuah peraruh bernilai 200 mH, perintang 60  $\Omega$  dan pemuat 20  $\mu\text{F}$  disambungkan secara selari merentasi 20V, bekalan frekuensi berubah-ubah. Kirakan regangan induktif dan Q-faktor sewaktu frekuensi salun berlaku.*
- [8 marks]  
[8 markah]

- CLO1  
C3

(c) A coil of  $100 \Omega$  resistance and  $253 \text{ mH}$  inductance are connected in series with a capacitance of  $100 \text{ nF}$  across a  $10\text{V}$  at resonance frequency  $1000.6\text{Hz}$ . Calculate the voltage across the capacitor at resonance. Also compute the circuit Q-factor and the bandwidth.

Sebuah gegelung dengan rintangan  $100 \Omega$  dan kearuhan  $253 \text{ mH}$  disambung secara sesiri pada pemuat  $100 \text{ nF}$  merentasi  $10V$  pada frekuensi resonans  $1000.6\text{Hz}$ . Kira voltan merentasi kapasitor sewaktu frekuensi salun berlaku. Cari Q-faktor dan jalur lebar litar tersebut.

[9 marks]

[9 markah]

## QUESTION 3

### **SOALAN 3**

- CLO1  
C3 (a) A 100 kVA, 50 Hz single-phase transformer has 100 secondary turns with primary current is 25 A and secondary current, 500A. Calculate the primary voltage, the secondary voltage, and the number of primary turns.

Sebuah pengubah sefasa dengan 100 kVA, 50 Hz mempunyai 100 pusingan lilitan sekunder, dengan arus primer adalah 25 A dan arus sekunder adalah 500 A. Kirakan voltan primer, voltan sekunder dan bilangan pusingan primer.

[8 marks]

[8 markah]

CLO1  
C3

- (b) A 415V, 3-phase, 4 wire, STAR-connected system supplies three resistive loads as shown in Figure A3(b). Calculate the phase voltage and the current in each line.

*Bekalan tiga fasa 415V dengan 4 wayar, disambungkan dalam STAR pada beban tiga perintang seperti Rajah A3(b). Kira voltan fasa dan nilai arus pada setiap talian.*

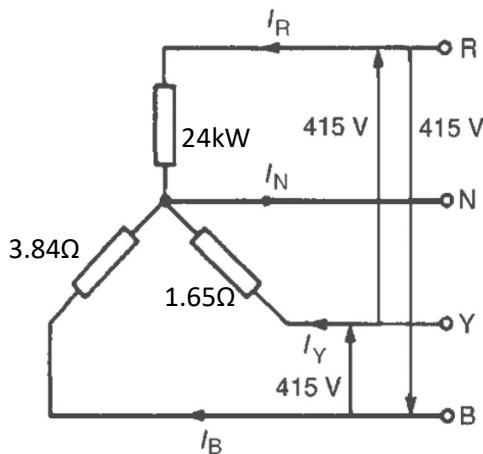


Figure A3(b) / Rajah A3(b)

[8 marks]

[8 markah]

CLO1  
C3

- (c) **THREE (3)** identical coils, each of resistance  $10 \Omega$  and capacitor  $241.3 \mu F$  are connected in DELTA to a 415V, 50 Hz, three phase supplies. Calculate the total power dissipated.

*TIGA (3) gegelung yang sama disambungkan dalam DELTA pada bekalan fasa tiga 415V, 50 Hz. Setiap gegelung memiliki perintang  $10 \Omega$  dan pemuat  $241.3 \mu F$ . Kira jumlah kuasa pelesapan pada setiap gegelung*

[9 marks]

[9 markah]

**SECTION B : 25 MARKS****BAHAGIAN B : 25 MARKAH****INSTRUCTION:**

This section consists of **ONE (1)** essay question. Answer the question.

**ARAHAN:**

*Bahagian ini mengandungi SATU (1) soalan eseai. Jawab soalan tersebut.*

**QUESTION 1****SOALAN 1**

- CLO1  
C3 A resistance  $11\ \Omega$ , an inductance  $280\text{ mH}$  and a  $500\ \mu\text{F}$  capacitor are connected in parallel arrangement across a  $240\text{ V}$ ,  $50\text{ Hz}$  supply as shown in Figure B1. The supply current is equivalent to the total vector of current flows through each component. Calculate the total current and construct the phasor diagram.

*Sebuah litar mengandungi perintang  $11\ \Omega$  dan peraruh bernilai  $280\text{ mH}$ , disambungkan secara sesiri dengan pemuat bernilai  $500\mu\text{F}$  pada bekalan  $240V$ ,  $50\text{Hz}$  dengan merujuk Rajah B1. Hasil tambah vector arus yang mengalir pada setiap komponen adalah bersamaan dengan jumlah arus yang dibekalkan. Kira jumlah arus dan bina gambarajah fasa yang bersesuaian.*

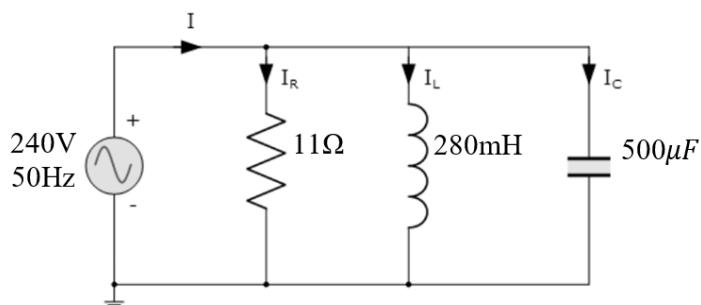


Figure B1 / Rajah B1

[25 marks]

[25 markah]

**SOALAN TAMAT**