

**SULIT**



BAHAGIAN PEPERIKSAAN DAN PENILAIAN  
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI  
KEMENTERIAN PENGAJIAN TINGGI

JABATAN KEJURUTERAAN ELEKTRIKAL

PEPERIKSAAN AKHIR  
**SESI II : 2021/2022**

**BEU10013: ELECTRICAL TECHNOLOGY**

---

**TARIKH : 6 JULAI 2022**  
**MASA : 9.00 PAGI – 12.00 TENGAH HARI (3JAM)**

---

Kertas ini mengandungi **DUA BELAS (12)** halaman bercetak.

Bahagian A: Struktur (3 soalan)

Bahagian B: Esei (1 soalan)

Dokumen sokongan yang disertakan : Tiada

---

**JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN**

(CLO yang tertera hanya sebagai rujukan)

**SULIT**

**SECTION A: 75 MARKS**  
**BAHAGIAN A: 75 MARKAH****INSTRUCTION:**

This section consists of **THREE (3)** structured questions. Answer **ALL** the questions.

**ARAHAN:**

Bahagian ini mengandungi **TIGA (3)** soalan berstruktur. Jawab **SEMUA** soalan.

CLO1  
C3**QUESTION 1**  
**SOALAN 1**

- (a) i) Calculate the L length of copper wire required to produce a 4mW resistor? Assume the diameter of the wire is 1 mm and that resistivity  $r$  of copper is  $1.72 \times 10^{-8}$  Wm.
- ii) Calculate the resistance of a 5m long conductor if it has cross sectional area is  $10\text{mm}^2$  and resistivity is  $0.3 \times 10^{-5}$   $\Omega\text{m}$ .
- i) *Kira panjang L dawai kuprum yang diperlukan untuk menghasilkan perintang 4mW? Andaikan diameter wayar ialah 1 mm dan kerintangan r kuprum ialah  $1.72 \times 10^{-8}$  Wm.*
- ii) *Kira rintangan konduktor sepanjang 5m jika ia mempunyai luas keratan rentas  $10\text{mm}^2$  dan kerintangan  $0.3 \times 10^{-5}$   $\Omega\text{m}$ .*


[8 marks]

[8 markah]

- CLO1 (b) Diagram A1(b) shows some resistor is connected in series and parallel.  
C3 Calculate :  
i) The value of the total resistance.  
ii) Total value of current.

Rajah A1(b) menunjukkan beberapa perintang yang disambung secara siri dan selari. Kirakan:

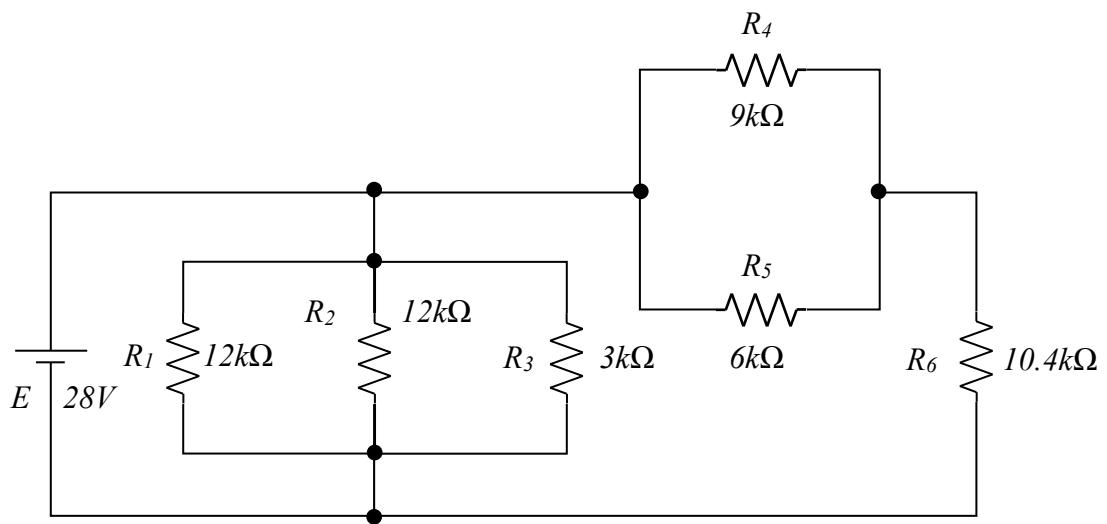- i) *Jumlah rintangan.*
  - ii) *Jumlah Arus.*



### Diagram A1(b) / Rajah A1(b)

[8 marks]

[8 markah]

CLO1  
C3

- (c) Diagram A1(c) shows direct current circuit with the connection of several resistors. This circuit has 24V voltage source. By using wye-delta transformation. Calculate :

- Value of the total resistance ( $R_T$ )
- Current  $I_O$

*Rajah A1(c) menunjukkan litar arus terus yang disambung dengan beberapa perintang. Litar ini mempunyai voltan bekalan 24V. Dengan menggunakan transformasi wye-delta. Kirakan :*

- Nilai rintangan jumlah ( $R_T$ )
- Arus  $I_O$

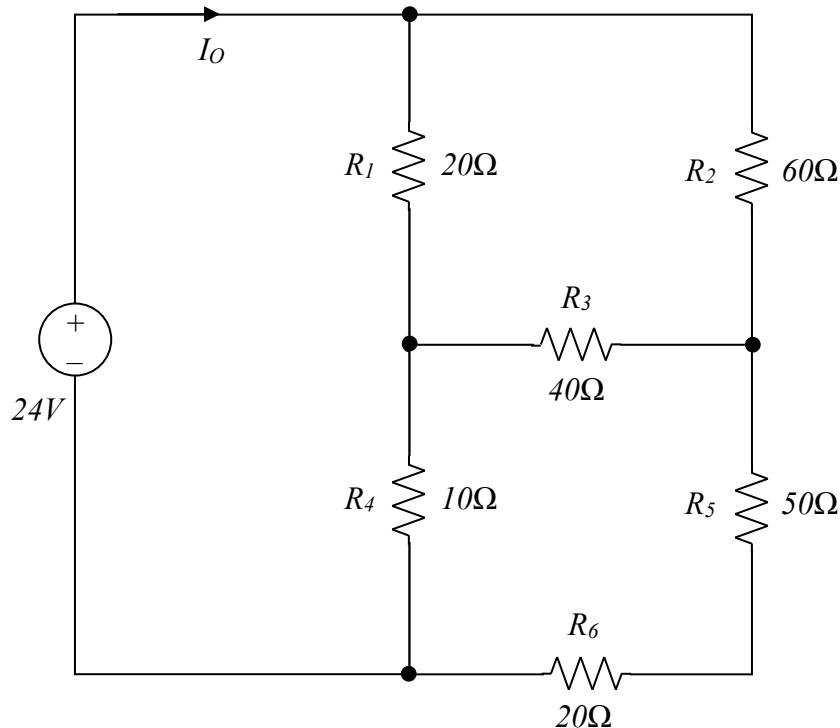


Diagram A1(c) / Rajah A1(c)

[9 marks]

[9 markah]

CLO1  
C3**QUESTION 2**  
**SOALAN 2**

- (a) Diagram A2(a) shows direct current circuit having a voltage source  $E_1 = 20V$  and, is connected with resistor which is connected in series and parallel. Using **Thevenin Theorem** calculate the total Thevenin Resistance  $R_{TH}$ , when the a-b terminal of the load  $Z_L$  is opened.

*Rajah A2(a) menunjukkan litar arus terus yang mempunyai punca voltan  $E_1 = 20V$  disambung dengan beberapa perintang. Dengan menggunakan **Theorem Thevenin** kirakan nilai rintangan Thevenin  $R_{TH}$ , apabila terminal a-b pada beban  $Z_L$  dibuka.*

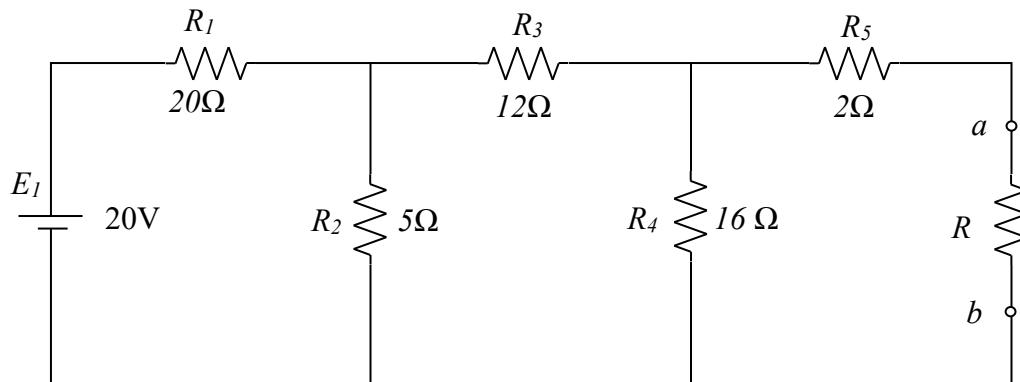


Diagram A2(a) / Rajah A2(a)

[8 marks]

[8 markah]

- CLO1 | (b) The A2(b) circuit diagram has a current supply of 6mA and a supply voltage of 24V. Using the **Superposition Theorem**, calculate voltage drops at  $R_1$ .

*Litar dalam Rajah A2(b) mempunyai satu bekalan arus 6mA dan satu bekalan voltan 24V. Dengan menggunakan **Teorem Tindihan**, kirakan nilai voltan yang susut pada perintang  $R_1$ .*

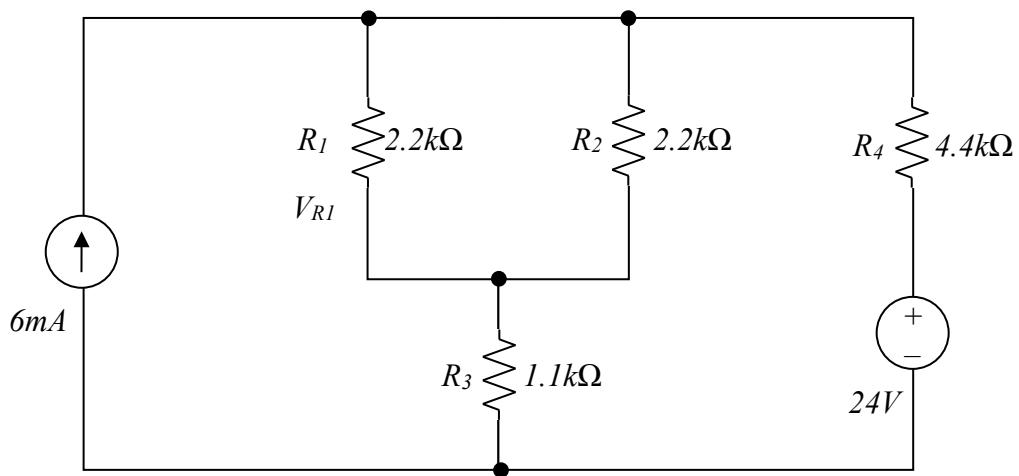


Diagram A2(b) / Rajah A2(b)

[8 marks]

[8 markah]

CLO1  
C3

- (c) Figure A2 (c) shows an electrical circuit. Calculate the Norton resistance ( $R_N$ ) and Norton current ( $I_N$ ) values when terminals a-b on are opened.

*Rajah A2(c) menunjukkan satu litar elektrik. Kirakan nilai rintangan setara Norton ( $R_N$ ) dan arus Norton ( $I_N$ ) apabila terminal a-b pada dibuka.*

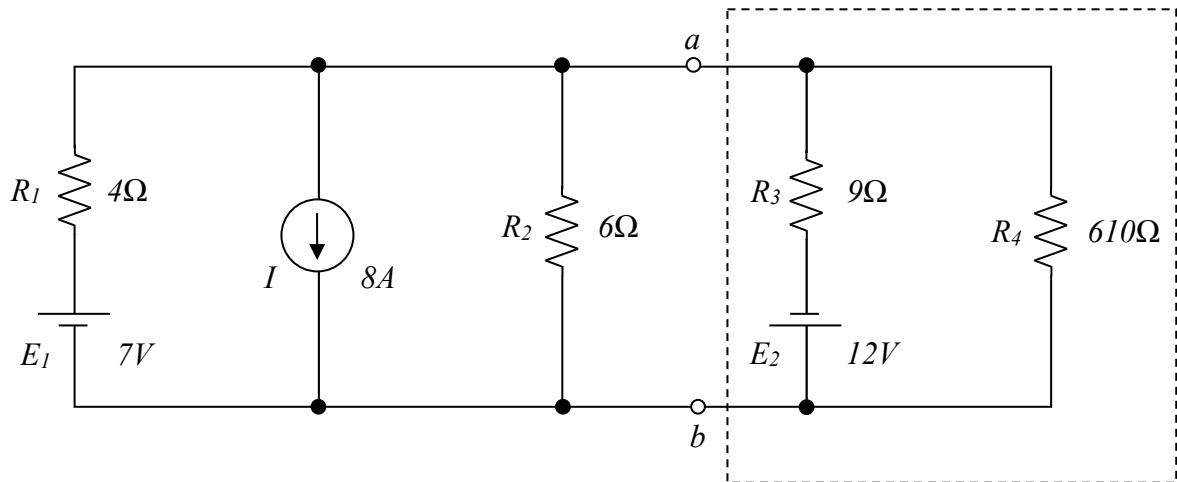


Diagram A2(c) / Rajah A2(c)

[9 marks]

[9 markah]

**QUESTION 3**  
**SOALAN 3**

CLO1  
C3

- (a) Diagram A3(a), shows the inductance circuit connection, Calculate
- Calculate voltage and current across the inductance if the switch is thrown into position 1 at  $t = 0\text{s}$ .
  - The mathematical expressions for the response of  $v_c$  and  $i_c$  if the switch is thrown into position 2 at  $t = 48\text{ms}$ .

*Rajah A3(b), menunjukkan sambungan litar indukten:*

- Kirakan voltan dan arus melintasi indukten jika suis digerakkan ke kedudukan 1 pada  $t = 0\text{s}$ .*
- Ungkapan matematik untuk  $v_c$  dan  $i_c$  jika suis digerakkan ke kedudukan 2 pada  $t = 48\text{ms}$ .*

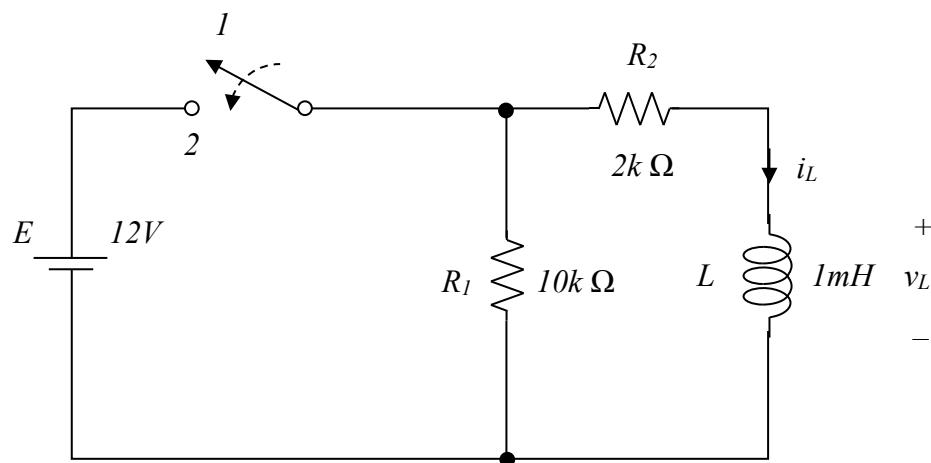


Diagram A3(a) / Rajah A3(b)

[8 marks]

[8 markah]

- CLO1 (b) Diagram A3(b), shows the capacitor circuit connection:
- C3 i) Calculate the voltage and current across the capacitor if the switch is thrown into position 1 at  $t = 0s$ .
- ii) Write the mathematical expressions for the response of  $v_c$  and  $i_c$  if the switch is thrown into position 2 at  $30\mu s$ .

*Rajah A3(b), menunjukkan sambungan litar kapasitor :*

- i) *Kirakan nilai voltan dan arus melintasi kapasitor jika suis digerakkan ke kedudukan 1 pada  $t = 0s$ .*
- ii) *Tuliskan ungkapan matematik untuk  $v_c$  dan  $i_c$  jika suis digerakkan ke kedudukan 2 pada  $t = 30\mu s$ .*

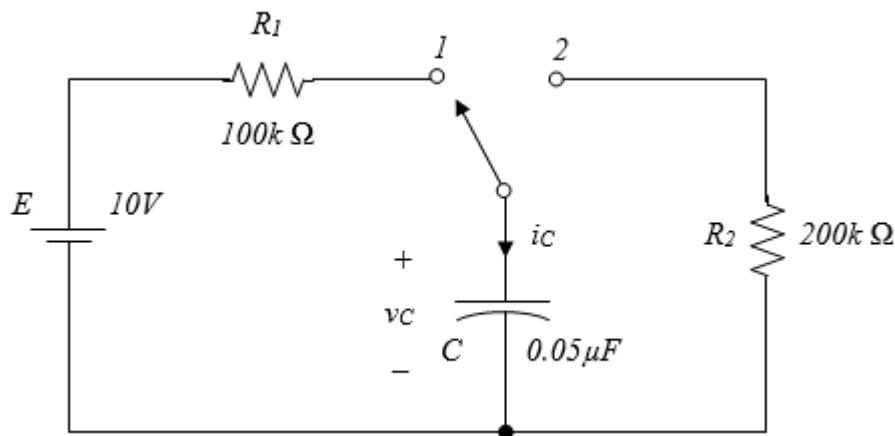


Diagram A3(b) / Rajah A3(b)

[8 marks]

[8 markah]

- CLO1 | (c) (i) Compute the magnetic flux  $\Phi$  established in the series magnetic circuit of Diagram A3(c)(i).

*Hitungkan fluks magnet  $\Phi$  yang terbentuk dalam litar siri magnet seperti dalam Rajah A3(c)(i).*

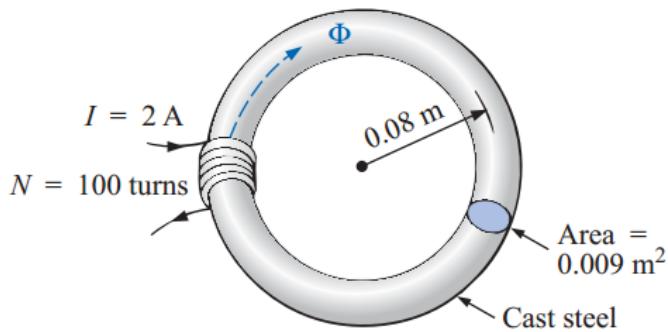


Diagram A3(c)(i) / Rajah A3(c)(i)

[4 marks]  
[4 markah]

- (ii) Calculate the secondary current  $I_2$  for the transformer of Diagram A3(c)(ii) if the resultant clockwise flux in the core is  $1.5 \times 10^{-5}$  Wb.

*Kirakan arus sekunder  $I_2$  untuk pengubah Rajah A3(c)(ii) jika fluks arah jam yang dihasilkan dalam teras ialah  $1.5 \times 10^{-5}$  Wb.*

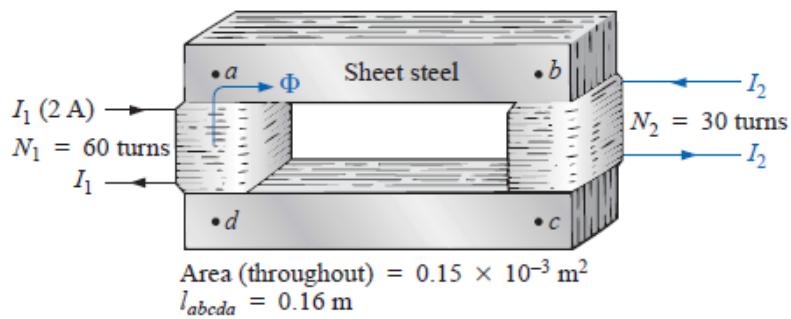


Diagram A3(c)(ii) / Rajah A3(c)(ii)

[5 marks]  
[5 markah]

**SECTION B: 25 MARKS**  
**BAHAGIAN B: 25 MARKAH**

**INSTRUCTION:**

This section consists of **ONE (1)** essay questions. Answer the questions.

**ARAHAN:**

Bahagian ini mengandungi **SATU (1)** soalan eseai. Jawab semua soalan.

CLO1  
C3

**QUESTION 1**  
**SOALAN 1**

- (a) Diagram B1(a) shows the transformer, Calculate:
- the equivalent resistance  $R_e$ .
  - the equivalent reactance  $X_e$ .
  - the equivalent circuit reflected to the primary.
  - the load voltage  $V_L$ .

*Rajah B1(a) menunjukkan pengubah, Kirakan:*

- rintangan setara  $R_e$ .
- reaktan setara  $X_e$ .
- litar setara dipantulkan ke primer.
- voltan beban  $V_L$ .

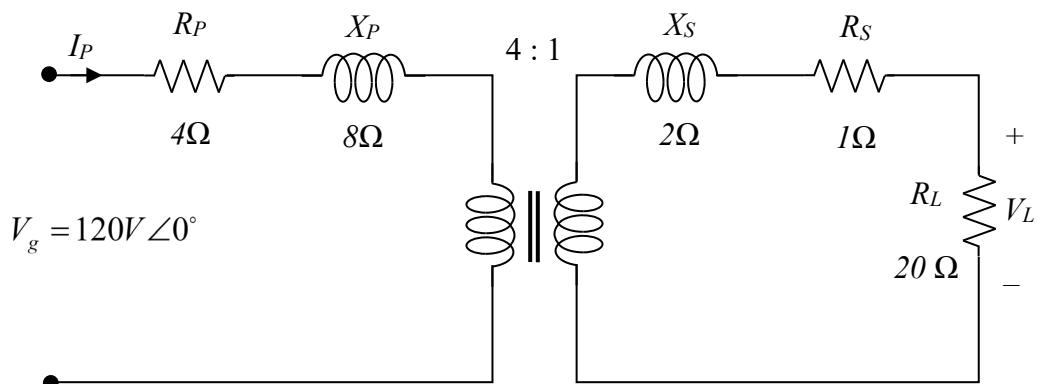


Diagram B1(a) / Rajah B1(a)

[10 marks]

[10 markah]

- (b) Diagram B1(b), shows a circuit with the source's voltage of 8V and 1V is connected with a number of resistors. Calculate the current  $I_1$  using Mesh Analysis.

*Rajah B1(b), menunjukkan litar yang mempunyai voltan bekalan 8V dan 1V, dihubungkan dengan sejumlah perintang. Kirakan nilai arus  $I_1$  dengan menggunakan Mesh Analysis.*

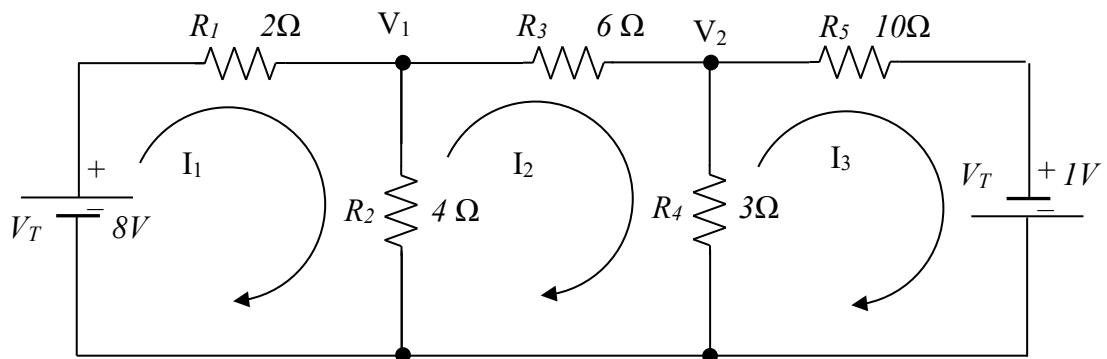


Diagram B1(b) / Rajah B1(b)

[15 marks]

[15 markah]

**SOALAN TAMAT**