

SULIT



**KEMENTERIAN PENDIDIKAN TINGGI
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI**

**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI
KEMENTERIAN PENDIDIKAN TINGGI**

JABATAN KEJURUTERAAN MEKANIKAL

PEPERIKSAAN AKHIR

SESI I : 2023/2024

DJJ20053 : ELECTRICAL TECHNOLOGY

TARIKH : 2 JANUARI 2024

MASA : 8.30 AM – 10.30 PM (2 JAM)

Kertas ini mengandungi **SEMBILAN (9)** halaman bercetak.

Struktur (4 soalan)

Dokumen sokongan yang disertakan : Formula

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

INSTRUCTION:

This paper consists of **FOUR (4)** structured questions. Answer **ALL** questions.

ARAHAN:

*Kertas ini mengandungi **EMPAT (4)** soalan berstruktur. Jawab **SEMUA** soalan.*

QUESTION 1**SOALAN 1**

CLO 1

- (a) Define electrical circuit and state **TWO (2)** types of electric circuit.

*Takrifkan litar elektrik dan nyatakan **DUA (2)** jenis litar elektrik.*

[6 marks]

[6 markah]

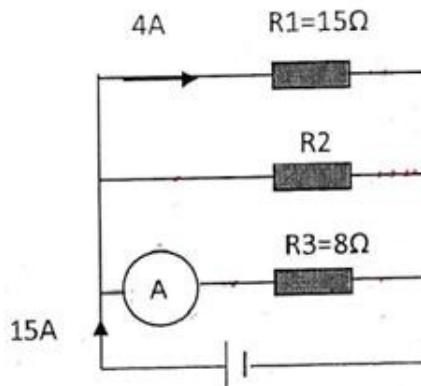


Figure 1 (a) : Electrical Circuit

Rajah 1(a) : Litar Elektrik

CLO 2

- (b) Referring to **Figure 1(a)**, express the value of:

*Berdasarkan kepada **Rajah 1(a)**, tentukan nilai bagi:*

- i. Ammeter reading

Bacaan pada ammeter

[3 marks]

[3 markah]

- ii. Resistance of R_2
Rintangan R_2 [3 marks]
[3 markah]
- iii. Voltage drop across R_2
Voltan susut pada R_2 [2 marks]
[2 markah]

- CLO 2 (c) A housewife bought a new rice cooker of brand X at an electrical store. **Table 1 (c)** shows the specifications of the rice cooker. Referring to **Table 1 (c)**, calculate: *Seorang surirumah telah membeli sebuah periuk nasi baharu berjenama X di sebuah kedai elektrik. Jadual 1(c) menunjukkan spesifikasi periuk nasi tersebut. Berdasarkan Jadual 1(c), kirakan:*

Table 1 (c) : Specifications Of Rice Cooker Brand X
Jadual 1(c): Spesifikasi Peruk Nasi Jenama X


Model <i>Model</i>	PSCL301
Voltage <i>Voltan</i>	240V,50Hz
Power <i>Kuasa</i>	3.45kW
Capacity <i>Kapasiti</i>	3L
Weight <i>Berat</i>	2.4KG

- i. Current, I
Arus, I [4 marks]
[4 markah]

- ii. Resistance, R
Rintangan, R
- [3 marks]
[3 markah]
- iii. Energy, if the rice cooker is switched on for half an hour, E
Kuasa, jika periuk digunakan selama setengah jam, E
- [4 marks]
[4 markah]

QUESTION 2***SOALAN 2***

- CLO 1 (a) Define and give the schematic diagram for both capacitor and inductor.
Takrifkan dan berikan rajah skematik bagi pemuat dan peraruh.
- [6 marks]
[6 markah]
- CLO 2 (b) Express the value of total capacitance of three capacitors, $C_1 = 2 \mu\text{F}$, $C_2 = 4 \mu\text{F}$, $C_3 = 4 \mu\text{F}$ which are connected in:
Nyatakan nilai bagi jumlah kemuatan bagi tiga pemuat, $C1 = 2 \mu\text{F}$, $C2 = 4 \mu\text{F}$, $C3 = 4 \mu\text{F}$ yang disambungkan secara:
- i. Series
Sesiri
- [4 marks]
[4 markah]
- ii. Parallel
Selari
- [3 marks]
[3 markah]

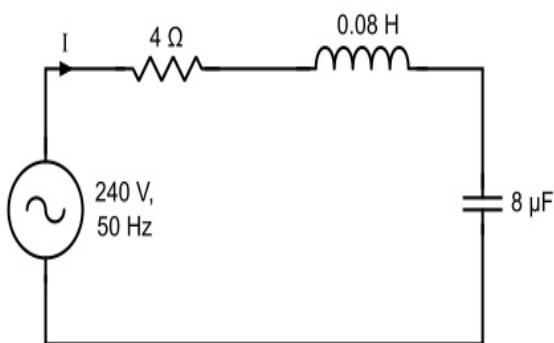**Figure 2 (c) : RLC Circuit****Rajah 2 (c) : Litar RLC**

CLO 2

- (c) RLC circuit as in **Figure 2 (c)** is the combination of resistor, inductor and capacitor in series with AC supply. Calculate:

*Litar RLC seperti dalam **Rajah 2 (c)** ialah gabungan perintang, peraruh dan pemuat secara bersiri dengan bekalan AC. Kirakan:*

- i. Impedance, Z

Galangan, Z

[4 marks]

[4 markah]

- ii. Current, I

Arus, I

[2 marks]

[2 markah]

- iii. Phase angle, Θ

Sudut fasa, Θ

[2 marks]

[2 markah]

- iv. Power factor, pf

Faktor kuasa, pf

[2 marks]

[2 markah]

- v. Real power, P
Kuasa sebenar, P
- [2 marks]
[2 markah]

QUESTION 3***SOALAN 3***

- CLO 1 (a) State **THREE (3)** characteristics of magnetic field lines.
*Nyatakan **TIGA (3)** ciri-ciri medan magnet.*
- [6 marks]
[6 markah]
- CLO 2 (b) A mild steel ring has a radius of 60mm and a cross sectional area of 500mm².
A current of 0.3A flows in a coil wound uniformly around the ring and the flux produced is 0.01mWb. If the relative permeability is 300, express the value of:
Gelang keluli lembut mempunyai jejari 60mm dan luas keratan rentas 500mm². Arus 0.3A mengalir dalam gegelung dililit secara seragam di sekeliling gelang dan fluks yang dihasilkan ialah 0.01mWb. Jika kebolehtelapan relativ ialah 300, nyatakan nilai bagi:
- i. Flux density, B
Ketumpatan fluks, B
- [3 marks]
[3 markah]
- ii Reluctance of the mild steel, S
Keengganan keluli lembut, S
- [3 marks]
[3 markah]

- iii. Magnetic field strength, H
Kekuatan medan magnet, H
[2 marks]
[2 markah]
- CLO 2 (c) A stainless steel cylinder of 150cm length and crossed sectional area 5cm^2 is wounded with 1000 turns of coil and 6A current flowing through it. The value of relative permeability is 1500, calculate:
Sebuah silinder keluli tahan karat dengan panjang 150 cm dan luas keratan rentas 5cm^2 dililit dengan 1000 lilitan gegelung dan arus 6A mengalir melaluinya.
Nilai kebolehtelapan relatif ialah 1500, hitung:
- i. Magnetomotive force, Fm
Daya gerak magnet,Fm.
[2marks]
[2 markah]
- ii. Magnetic field strength, H
Kekuatan medan magnet, H
[3 marks]
[3 markah]
- iii. Flux density, B
Ketumpatan fluks,B
[3 marks]
[3markah]
- iv. The value of flux, Φ
Nilai fluks, Φ
[3 marks]
[3 markah]

QUESTION 4**SOALAN 4**

CLO1

- (a) State **TWO (2)** basic parts of AC Machine and give the structure diagram for each.

*Nyatakan **DUA (2)** bahagian asas struktur Mesin AU dan berikan rajah struktur setiap satunya.*

[6 marks]

[6 markah]

CLO 2

- (b) The frequency of the supply to the stator of 8-poles induction motor is 50 Hz,

the rotor frequency is 3 Hz with 15 conductors/slots. Express the value of:

Frekuensi yang dibekalkan pada pemegun, motor aruan 8 kutub adalah 50Hz, frekuensi pemutar adalah 3 Hz dengan 15 konduktor/slot. Nyatakan nilai bagi:

- i. Synchronous speed, N_s

Kelajuan segerak, N_s

[2 marks]

[2 markah]

- ii. Percentage of slip, %S

Peratus slip, % S

[3 marks]

[3 markah]

- iii. Rotor speed, N_r

Kelajuan rotor, N_r

[2 marks]

[2 markah]

CLO 2

- (c) A single phase transformer has a voltage ratio of 6:1 and high voltage winding is supplied at 540V. The secondary winding provides a full load current of 30A. Neglecting losses, calculate:
- Pengubah fasa tunggal mempunyai nisbah voltan 6:1 dan lilitan voltan tinggi dibekalkan pada 540V. Lilitan sekunder menyediakan arus beban penuh 30A. Abaikan kehilangan, hitungkan:*
- i. Secondary voltage, V_s
Voltan sekunder, V_s [3 marks]
[3 markah]
 - ii. Power supplied to load, P_s
Kuasa pada beban, P_s [2 marks]
[2 markah]
 - iii. Primary current, I_p
Arus primer, I_p [3 marks]
[3 markah]
 - iv. Type of transformer
Jenis pengubah[4 marks]
[4 markah]

SOALAN TAMAT

DJJ20053 – ELECTRICAL TECHNOLOGY

FORMULA

<u>INTRODUCTION TO ELECTRICAL CIRCUITS</u>	<u>ALTERNATING CURRENT CIRCUIT</u>	<u>AC MACHINES</u>
$R = \frac{\rho l}{A}$ $V = IR$ $P = IV$ $E = Pt$ $C = \frac{Q}{V}$	RL CIRCUIT $I = \frac{V}{Z}$ $V_L = IX_L$ $Z = \sqrt{R^2 + X_L^2}$ $\theta = \tan^{-1} \left[\frac{X_L}{R} \right]$ $\cos \theta = \frac{R}{Z}$	$N_s = \frac{120f}{P}$ $\%S = \frac{N_s - N_r}{N_s} \times 100$ $N_r = N_s(1 - S)$ $f_r = Sf$ $E = 2.22 K_d K_p f \phi Z$
KIRCHOFF'S LAW . $V_T = V_1 + V_2 + V_3$ $\sum I_{IN} = \sum I_{OUT}$ $I_1 = I_2 + I_3$	RC CIRCUIT $I = \frac{V}{Z}$ $V_C = IX_C$ $Z = \sqrt{R^2 + X_C^2}$ $\theta = -\tan^{-1} \left[\frac{X_C}{R} \right]$ $\cos \theta = \frac{R}{Z}$	TRANSFORMER $\frac{V_p}{V_s} = \frac{N_p}{N_s} = \frac{I_s}{I_p}$ $E_1 = 4.44 f N_1 \Phi_m$ $E_2 = 4.44 f N_2 \Phi_m$
SERIES $V_T = V_1 + V_2 + \dots + V_n$ $I_T = I_1 = I_2 = \dots = I_n$ $R_T = R_1 + R_2 + \dots + R_n$ $L_T = L_1 + L_2 + \dots + L_n$ $\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$ $V_x = \frac{R_x}{R_T} V_T$	RLC CIRCUIT $I = \frac{V}{Z}$ $V_L = IX_L$ $V_R = IR$ $V_C = IX_C$ $Z = \sqrt{R^2 + (X_L - X_C)^2}$ $\theta = \tan^{-1} \left[\frac{X_L - X_C}{R} \right]$ $\cos \theta = \frac{R}{Z}$	Complex Power, S (VA) = VI Actual Power, P (W) = $VI \cos \theta$ Reactive Power, Q (VAR) = $VI \sin \theta$ $I = \frac{\text{Power}}{\text{Voltage}}$ Power losses = Core losses + $I_p^2 R_p + I_s^2 R_s$ Output power = Power x power factor Input power = output power + power losses Efficiency, $\% \eta = \frac{\text{output power}}{\text{Input power}} \times 100$
PARALLEL $V_T = V_1 = V_2 = \dots = V_n$ $I_T = I_1 + I_2 + \dots + I_n$ $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$ $\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$ $C_T = C_1 + C_2 + \dots + C_n$ $I_x = \frac{R_x}{R_T} I_T$		ELECTROMAGNET $H = \frac{Fm}{l} = \frac{NI}{l}$ $B = \frac{\Phi}{A}$ $B = \mu H$ $\mu = \mu_0 \mu_r$ $S = \frac{Fm}{\Phi} @ \frac{l}{\mu A}$