

SULIT



**KEMENTERIAN PENDIDIKAN TINGGI
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI**

**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI
KEMENTERIAN PENDIDIKAN TINGGI**

JABATAN KEJURUTERAAN ELEKTRIK

PEPERIKSAAN AKHIR

SESI I : 2023/2024

DET20033: ELECTRICAL CIRCUITS

TARIKH : 7 JUN 2024

MASA : 8.30 AM – 10.30 AM (2 JAM)

Kertas ini mengandungi **(7)** halaman bercetak.

Bahagian A: Struktur (4 soalan)

Bahagian B: Esei (1 soalan)

Dokumen sokongan yang disertakan : Formula

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

SECTION A: 80 MARKS
BAHAGIAN A: 80 MARKAH

INSTRUCTION:

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi **EMPAT (4)** soalan berstruktur. Jawab **SEMUA** soalan.

QUESTION 1**SOALAN 1**

- CLO1 (a) Identify **TWO (2)** methods to generate alternating current (AC).

*Kenal pasti **DUA (2)** kaedah untuk menjana arus ulang-alik.*

[4 marks]

[4 markah]

- CLO1 (b) Discuss **THREE (3)** factors that affect the amount of voltage induced in alternating current (AC).

*Bincangkan **TIGA (3)** faktor yang mempengaruhi jumlah voltan teraruh dalam arus ulang-alik.*

[6 marks]

[6 markah]

- CLO1 (c) An alternating circuit (AC) has a voltage value, $v = 240 \sin (300\pi t + 0.5)$ V at instantaneous time, t seconds. Calculate:

Sebuah litar arus ulang alik mempunyai nilai voltan, $v = 240 \sin (300\pi t + 0.5)V$ pada masa ketika , t saat. Kira:

- i. The amplitude

Nilai amplitud

- ii. Root mean square voltage (V_{rms}) and average voltage (V_{avg})

Voltan punca ganda dua (V_{rms}) dan Voltan purata (V_{purata}).

iii. The frequency

Nilai frekuensi

iv. The value of voltage when $t = 2.0 \text{ ms}$

Nilai voltan ketika $t = 2.0 \text{ ms}$

[10 marks]

[10 markah]

QUESTION 2

SOALAN 2

CLO1

- (a) Given $v = 15 \sin(\omega t + 45^\circ) \text{ V}$ and $i = 5 \sin(\omega t + 20^\circ) \text{ A}$. Determine phase relationships and sketch the waveforms.

Diberi $v = 15 \sin(\omega t + 45^\circ) \text{ V}$ dan $i = 5 \sin(\omega t + 20^\circ) \text{ A}$. Tentukan hubungan fasa dan lakarkan bentuk gelombang.

[5 marks]

[5 markah]

CLO1

- (b) Based on Figure A2(b), simplify the inductive circuit to obtain the total inductance.

Berdasarkan Rajah A2(b), permudahkan litar aruhan tersebut untuk mendapatkan jumlah kearuhan.

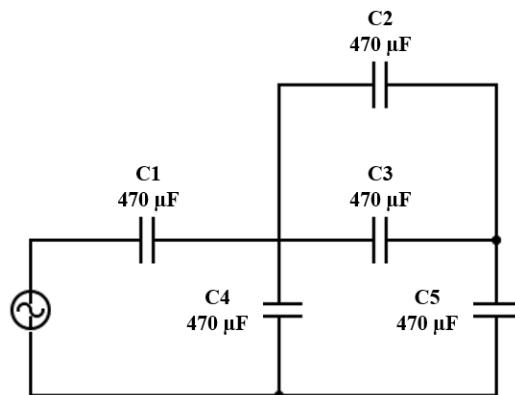


Figure A2(b) / Rajah A2(b)

[5 marks]

[5 markah]

- CLO1 (c) A series resonance circuit consisting of a resistor of 100Ω , a capacitor of $47 \mu F$ and an inductor of 70 mH connected a sinusoidal supply voltage which has a constant output of 5 V at all frequency. Calculate:
- resonance frequency
 - current resonance
 - voltage across the inductor and capacitor at resonance.
 - quality factor, Q

Litar salun siri dengan rintangan 100Ω , pemuat $47 \mu F$ dan pearuh 70 mH disambungkan kepada bekalan voltan sinusoidal yang mempunyai keluaran malar 5 V pada semua frekuensi. Kira:

- frekuensi salun*
- arus salun*
- voltan merentasi peraruh dan pemuat semasa salun.*
- faktor kualiti, Q*

[10 marks]

[10 markah]

QUESTION 3

SOALAN 3

- CLO1 (a) List **FOUR (4)** types of transformer.

*Senarai **EMPAT (4)** jenis pengubah.*

[4 marks]

[4 markah]

- CLO1 (b) Identify **SIX (6)** characteristics of an ideal transformer.

*Kenal pasti **ENAM (6)** ciri-ciri pengubah unggul.*

[6 marks]

[6 markah]

- CLO1 (c) Referring to the Figure A3(c) below, calculate primary voltage (V_P), secondary voltage (V_S), primary current (I_P) and secondary voltage (I_S).

Dengan merujuk kepada Rajah A3(c), kira voltan primer (V_P), voltan sekunder (V_S), arus primer (I_P) dan arus sekunder (I_S).

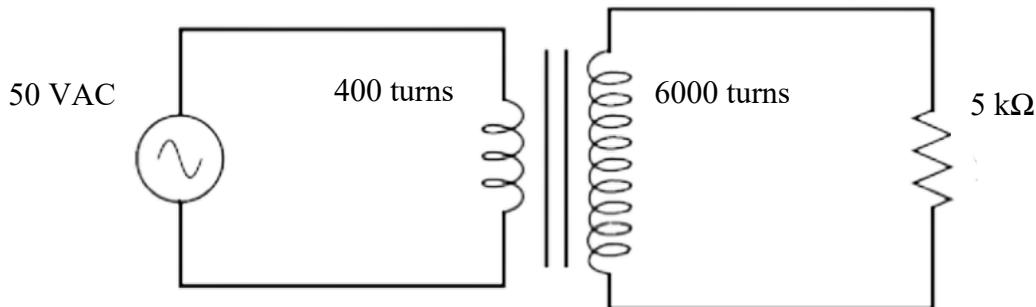


Figure A3(c) / Rajah A3(c)

[10 marks]

[10 markah]

QUESTION 4

SOALAN 4

- CLO1 (a) Explain the effects of changing the frequency to:
- RLC series circuit
 - RLC parallel circuit

Terangkan kesan-kesan penukaran frekuensi kepada:

- Litar sesiri RLC*
- Litar selari RLC*

[5 marks]

[5 markah]

- (b) One type of connection in a three phase system is a STAR connection. Explain the STAR connection in a three-phase system using a circuit diagram.

Salah satu jenis sambungan dalam sistem tiga fasa ialah sambungan STAR. Terangkan sambungan STAR di dalam sistem tiga fasa dengan gambarajah litar yang berkenaan.

[5 marks]

[5 markah]

- CLO1 (c) Three similar coils, each having a resistance of 5Ω and inductive reactance of 4.5Ω are connected in star to a 415 V, three-phase supply. Calculate :
- (i) line and phase voltages
 - (ii) phase and line currents
 - (iii) total power dissipated

Tiga gegelung yang serupa, setiap satu mempunyai rintangan 3.0Ω dan tindak balas induktif 4.5Ω disambungkan dalam bentuk bintang kepada bekalan 3 fasa 415 V. Kirakan :

- (i) voltan talian dan voltan fasa
- (ii) arus fasa dan arus talian
- (iii) jumlah pelepasan kuasa

[10 marks]

[10 markah]

SECTION B: 20 MARKS**BAHAGIAN B: 20 MARKAH****INSTRUCTION:**

This section consists of **ONE (1)** essay question. Answer the question.

ARAHAN:

Bahagian ini mengandungi SATU (1) soalan eseai. Jawab soalan tersebut.

QUESTION 1**SOALAN 1**

- CLO1 An alternating voltage given by $v = 300 \sin 400t$ volts is applied across a series combination of three impedances. The impedances comprise an inductance of 120 mH and 20 Ω resistance, an inductance of 350 mH and 70 Ω resistance, and a capacity of capacitance 270 μF and 45 Ω resistance. Calculate the circuit impedance, circuit current, phase angle, power factor and true power. Then, draw a phasor diagram representing the circuit.

Diberi voltan ulang-alik $v = 300 \sin 400t$ disambung secara siri merentasi tiga galangan. Galangan tersebut terdiri daripada nilai pearuh, 120 mH dan nilai perintang, 20 Ω , nilai pearuh, 350 mH dan nilai perintang, 70 Ω dan nilai pemuat, 270 μF dan nilai perintang, 45 Ω . Kira galangan litar, arus litar sudut fasa, faktor kuasa dan kuasa sebenar. Kemudian, lukis gambar rajah fasa yang yang mewakili litar.

[20 marks]

[20 markah]

SOALAN TAMAT

LAMPIRAN

SENARAI FORMULA

$V_P = \sqrt{2} \times V_{rms}$	$X_L = 2\pi f L$	$I_T = \sqrt{I_R^2 + (I_C - I_L)^2}$
$I_P = \sqrt{2} \times I_{rms}$	$X_C = \frac{1}{2\pi f C}$	$Z_T = \frac{V_S}{I_T}$
$V_{PP} = 2V_P$ <i>if</i> $X_L > X_C$; $X_{eq} = X_L - X_C$ <i>if</i> $X_C > X_L$; $X_{eq} = X_C - X_L$	$Z_T = \sqrt{R^2 + X_{eq}^2}$	$\theta = \tan^{-1} \left(\frac{I_C - I_L}{I_R} \right)$
$I_{PP} = 2I_P$	$I_T = \frac{V_S}{Z_T}$	$i(t) = I_P \sin(\omega t \pm \theta)$
$V_{rms} = \frac{V_P}{\sqrt{2}}$	$\theta = \cos^{-1} PF$	$Q = IV \sin \theta$ $Q = I^2 X_C - X_L $
$I_{rms} = \frac{I_P}{\sqrt{2}}$	$\theta = \tan^{-1} \left(\frac{X_C - X_L}{R} \right)$ $\theta = \tan^{-1} \left(\frac{V_C - V_L}{V_S} \right)$	$S = IV$ $S = I^2 Z$
$V_{ave} = \frac{2V_P}{\pi}$	$\cos \theta = \frac{R}{Z}$	$P = IV \cos \theta$
$I_{ave} = \frac{2I_P}{\pi}$	$V_R = IR$	$Q = IV \sin \theta$
$T = \frac{1}{f}$ $T = \frac{2\pi}{\omega}$	$V_L = IX_L$ $V_C = IX_C$	$\theta = \cos^{-1} PF = \cos^{-1} 1 = 0^\circ$
$f = \frac{1}{T}$ $f = \frac{\omega}{2\pi}$	$\theta = \tan^{-1} \left(\frac{X_C - X_L}{R} \right) = \tan^{-1} \left(\frac{0}{R} \right) = 0^\circ$ $\theta = \tan^{-1} \left(\frac{V_C - V_L}{V_S} \right) = \tan^{-1} \left(\frac{0}{V_S} \right) = 0^\circ$	
$\omega = 2\pi f$ $\omega = \frac{2\pi}{T}$	$S = IV$ $S = I^2 Z$	$\cos \theta = \frac{R}{Z} = \frac{R}{R} = 1$
$v(t) = V_P \sin(\omega t \pm \theta)$	$P = IV \cos \theta$ $P = I^2 R$	$f_r = \frac{1}{2\pi\sqrt{LC}}$
$BW = f_H - f_L = \frac{f_r}{Q}$	$f_L = f_r - \frac{BW}{2}$ $f_L = f_r + \frac{BW}{2}$	$Q = \frac{X_L}{R} = \frac{X_C}{R} = \frac{V_L}{V_S} = \frac{V_C}{V_S} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{f_r}{BW}$

LAMPIRAN

$\eta = \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$	$V_L = V_{RY} = V_{YB} = V_{BR}$ $V_L = \sqrt{3} V_P$	$V_L = V_{RY} = V_{YB} = V_{BR}$ $V_L = V_P$
--	--	---

$V_2 = \frac{N_2}{N_1} \times V_1$	$Z_P = \sqrt{R^2 + X_{eq}^2}$ <i>if</i> $X_L > X_C$; $X_{eq} = X_L - X_C$	$i f X_C > X_L$; $X_{eq} = X_C - X_L$ $Z_P = \frac{V_P}{I_P}$
$V_2 = \frac{P_2}{I_2}$		

$V_1 = \frac{N_1}{N_2} \times V_2$		
$V_1 = \frac{P_1}{I_1}$		

$I_2 = \frac{V_2}{R_L}$

$I_1 = \frac{N_2}{N_1} \times I_2$

$S_1 = S_2$ $I_1 V_1 = I_2 V_2$

$P_1 = I_1 V_1$ $P_2 = I_2 V_2$ or $P_2 = I_2^2 R_L$ $P_1 = P_2$
--

$I_P = \frac{V_P}{Z_P}$	$I_P = \frac{V_P}{Z_P}$
$I_P = I_L$	$I_P = \frac{I_L}{\sqrt{3}}$

$I_L = I_P$	$I_L = \sqrt{3} I_P$
-------------	----------------------

$S = 3 I_P V_P$ $S = \sqrt{3} I_L V_L$

$P = 3 I_P V_P \cos \theta$ $P = \sqrt{3} I_L V_L \cos \theta$
