

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK
KEMENTERIAN PENDIDIKAN TINGGI**

JABATAN KEJURUTERAAN ELEKTRIK

**PEPERIKSAAN AKHIR
SESI JUN 2017**

DET2033 : ELECTRICAL CIRCUITS

**TARIKH : 01 NOVEMBER 2017
MASA : 8.30 PAGI - 10.30 PAGI (2 JAM)**

Kertas ini mengandungi **DUA BELAS (12)** halaman bercetak.

Bahagian A: Objektif (10 soalan)
Bahagian B: Struktur (4 soalan)
Bahagian C: Esei (2 soalan)

Dokumen sokongan yang disertakan: Tiada

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN
(CLO yang tertera hanya sebagai rujukan)

SULIT

SECTION A: 10 MARKS**BAHAGIAN A: 10 MARKAH****INSTRUCTION:**

This section consists of TEN (10) objective questions. Mark your answers in the OMR form provided.

ARAHAN:

Bahagian ini mengandungi SEPULUH (10) soalan objektif. Tandakan jawapan anda dalam borang OMR yang disediakan.

- CLO1 1. Choose the source for Alternating Current (AC) from the list of sources below:
C1 *Pilih bekalan untuk Arus Ulang-alik (AU) daripada senarai bekalan di bawah:*
- A. Generator
 - B. Solar
 - C. Battery
 - D. Turbine
- CLO1 2. Identify the power drawn by a pure capacitor.
C2 *Kenal pasti kuasa yang diserap oleh kapasitor tulen.*
- A. 0
 - B. 1
 - C. Infinite
 - D. Can't determined
- CLO1 3. Describe resonance in series RLC circuit.
C2 *Terangkan salun dalam litar sesiri RLC.*
- A. The inductive reactance equals the resistance
Regangan induktif sama dengan rintangan
 - B. The capacitive reactance plus the inductive reactance equals the resistance
Regangan kapasitif dengan regangan induktif bersamaan dengan rintangan
 - C. The capacitive reactance equals the resistance
Regangan kapasitif sama dengan rintangan
 - D. The inductive reactance equals to capacitive reactance
Regangan induktif sama dengan regangan kapasitif

	SULIT	DET2033 : ELECTRICAL CIRCUITS		SULIT	DET2033 : ELECTRICAL CIRCUITS
CLO1 C2	<p>4. Select the CORRECT explanation for 'three phase supply'. <i>Pilih keterangan yang BETUL untuk 'bekalan tiga fasa'.</i></p> <p>A. Three phase supply is generated when three coils are placed 180° apart and the whole coil is rotated in a uniform magnetic field. <i>Bekalan tiga fasa dihasilkan apabila tiga gegelung diletakkan 180° dan seluruh gegelung diputarkan dalam medan magnet seragam.</i></p> <p>B. Three phase supply is generated when three coils are placed 60° apart and the whole coil is rotated in a uniform magnetic field. <i>Bekalan tiga fasa dihasilkan apabila tiga gegelung diletakkan 60° dan seluruh gegelung diputarkan dalam medan magnet seragam.</i></p> <p>C. Three phase supply is generated when two coils are placed 120° apart the whole coil is rotated in a uniform magnetic field. <i>Bekalan tiga fasa dihasilkan apabila dua gegelung diletakkan 120° dan seluruh gegelung diputarkan dalam medan magnet seragam.</i></p> <p>D. Three phase supply is generated when three coils are placed 120° apart and the whole coil is rotated in a uniform electromagnetic field. <i>Bekalan tiga fasa dihasilkan apabila tiga gegelung diletakkan 120° dan seluruh gegelung diputarkan dalam medan magnet seragam.</i></p>		CLO2 C3	<p>7. Calculate the rms value of a sinusoidal current of maximum value 30A. <i>Kira nilai arus rms apabila diberi nilai arus maksima sinusoidal sebanyak 30A.</i></p> <p>A. 12.12mA B. 15.1 mA C. 21.21A D. 1A</p>	
CLO1 C1	<p>5. Describe the causes of Eddy Current in a transformer. <i>Terangkan penyebab berlakunya Arus Pusaran di dalam sebuah transformer.</i></p> <p>A. an increase in efficiency. <i>peningkatan dalam kecekapan.</i></p> <p>B. an increase in coupling between windings. <i>peningkatan dalam gandingan diantara belitan.</i></p> <p>C. an increase in core loss. <i>peningkatan dalam kehilangan teras.</i></p> <p>D. an increase in usable frequency range. <i>peningkatan dalam julat frekuensi berguna</i></p>		CLO2 C3	<p>8. Calculate the inductance of the coil if the coil has a reactance of 120Ω in a circuit with a supply frequency of 4kHz. <i>Kirakan nilai induktan bagi gegelung tersebut jika satu gegelung yang mempunyai nilai reaktans 120Ω disambungkan dengan bekalan frekuensi 4kHz dalam satu litar.</i></p> <p>A. 6.3mH B. 4.77mH C. 3.27mH D. 5.51mH</p>	
CLO1 C2	<p>6. Calculate the secondary voltage if the turns ratio of a transformer is 12 and the primary AC voltage is 6V. <i>Kira voltan sekunder sekiranya nisbah lilitan pengubah ialah 12 dan voltan AC primer adalah 6V.</i></p> <p>A. 0.5V B. 50V C. 72V D. 2V</p>		CLO2 C3	<p>9. Determine the resonant frequency of the circuit if a pure inductance of 150mH is connected in parallel with a $40\mu\text{F}$ capacitor across a 50V, variable frequency supply. <i>Tentukan nilai frekuensi resonan pada litar tersebut jika satu pearuh bernilai 150mH disambungkan secara selari dengan kapasitor $40\mu\text{F}$ dan merentasi bekalan frekuensi bolehubah 50V.</i></p> <p>A. 50Hz B. 63.77Hz C. 64.97Hz D. 120Hz</p>	
			CLO2 C3	<p>10. Calculate the phase voltage and phase current in a star connected three phase system if given the line voltage 415V and the line current 30A. <i>Kirakan voltan fasa dan arus fasa untuk sambungan bintang sistem tiga fasa jika diberi voltan talian 415V dan arus talian 30A.</i></p> <p>A. $V_{PH} = 415\text{V}$, $I_{PH} = 17.32\text{A}$ B. $V_{PH} = 415\text{V}$, $I_{PH} = 30.0\text{A}$ C. $V_{PH} = 239.6\text{V}$, $I_{PH} = 30.0\text{A}$ D. $V_{PH} = 239.6\text{V}$, $I_{PH} = 17.32\text{A}$</p>	

SECTION B: 60 MARKS**BAHAGIAN B: 60 MARKAH****INSTRUCTION:**

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

ARAHAH:

*Bahagian ini mengandungi **EMPAT (4)** soalan berstruktur. Jawab **SEMUA** soalan.*

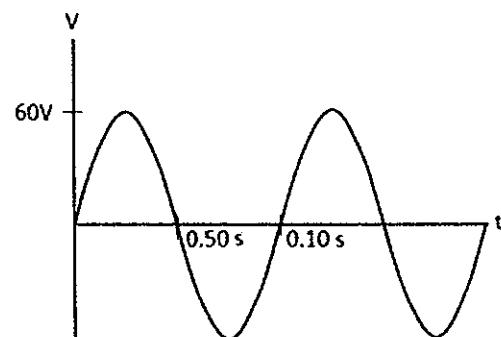
QUESTION 1**SOALAN 1**

Figure B1(a) / Rajah B1(a)

CLO1
C1

- (a) Based on Figure B1(a):

Berdasarkan Rajah B1(a):

- i) Define the time period, (T) of a sine waveform.

Berikan definisi tempoh masa, (T) bagi gelombang sinus.

[2 marks]

[2 markah]

- ii) Find the value of time period, (T).

Dapatkan nilai tempoh masa, (T).

[1 mark]

[1 markah]

CLO1
C2

- (b) Based on Figure B1(a);

Berdasarkan Rajah B1(a);

- i) State the peak voltage, V_p.

Nyatakan nilai voltan puncak, V_p

[2 marks]

[2 markah]

- ii) Write the sinusoidal waveform equation.

Tuliskan persamaan gelombang sinusoidal.

[3 marks]

[3 markah]

CLO2
C3

- (c) Calculate the following value for an AC voltage circuit given by $v(t) = 100 \sin 314t$ V.

Kirakan nilai berikut untuk litar voltan AU yang diberi oleh $v(t) = 100 \sin 314t$ V.

- i) The frequency and period time

Frekuensi dan tempoh

[4 marks]

[4 markah]

- ii) The value of the voltage at $t = 4$ ms

Nilai voltan pada ketika $t = 4$ ms

[3 marks]

[3 markah]

SULIT

CLO1
C1**QUESTION 2****SOALAN 2**

- (a) State the relation between inductive reactance, X_L and frequency, f . Draw the graph to illustrate this relation.

Nyatakan hubungkait di antara reaktan induktif, X_L dengan frekuensi, f . Lakarkan graf bagi menunjukkan hubungan ini.

[3 marks]

[3 markah]

CLO1
C2

- (b) Calculate the total impedance of a circuit and its circuit current when a RLC series circuit containing a resistance of 12Ω , an inductance of $0.15H$ and a capacitor of $100\mu F$ are connected in series across a $100V$, $50Hz$ supply.

Kirakan nilai galangan bagi suatu litar dan juga arus bagi litar tersebut apabila satu litar siri RLC yang mengandungi perintang 12Ω , induktor $0.15H$ dan kapasitor $100\mu F$ disambung secara siri disambung merentasi bekalan kuasa $100V$, $50Hz$.


[5 marks]

[5 markah]

SULIT

CLO2
C3

(c)

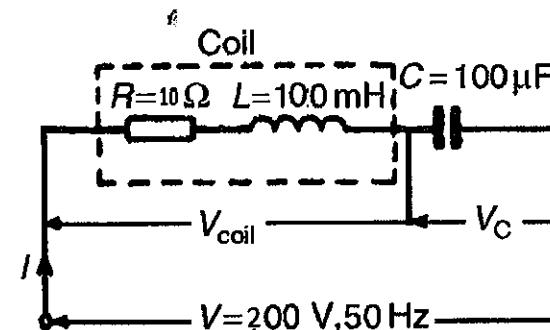**Figure B2(c) / Rajah B2(c)**

A coil of resistance 10Ω and inductance $100mH$ in series with capacitor $100\mu F$, is connected across $200V$, $50Hz$ power supply as in **Figure B2(c)**. Calculate :

*Suatu gelung dengan rintangan 10Ω dan peraruh $100mH$ disambungkan secara siri dengan kapasitor $100\mu F$ disambung kepada bekalan kuasa $200V$, $50Hz$ seperti dalam **Rajah B2(C)**. Kirakan :*

- i) Circuit impedance, Z

Galangan litar, Z

- ii) Circuit current, I

Arus Litar, I

- iii) Phase angle

Sudut fasa

- iv) Voltage across inductor

Voltan merentas peraruh

- v) Voltage across capacitor

Voltan merentas kapasitor

[7 marks]

[7 markah]

QUESTION 3**SOALAN 3**

- CLO1
C1 (a) List THREE (3) requirements contained in the three-phase power system.

Senaraikan TIGA (3) keperluan yang terdapat dalam sistem kuasa tiga fasa.

[3 marks]

[3 markah]

- CLO1
C2 (b) Describe and label clearly the delta connection in a three phase system using a circuit diagram.

Terangkan dan label dengan jelas sambungan delta di dalam sistem tiga fasa menggunakan gambarajah litar.

[5 marks]

[5 markah]

- CLO2
C3 (c) A three coil balanced load has 10Ω resistor and $100mH$ inductor, connected in star connection with a three phase supply system with $415V$, $50Hz$. Calculate the phase current (I_{PH}), the line current (I_L) and the power in three phase.

Tiga gelung yang seimbang mempunyai rintangan 10Ω dan pearuh $100mH$, disambung dalam bentuk bintang kepada sistem bekalan tiga fasa $415V$, $50Hz$. Kirakan arus fasa (I_{PH}), arus talian (I_L) dan kuasa dalam tiga fasa.

[7 marks]

[7 markah]

QUESTION 4**SOALAN 4**

- CLO1
C1 (a) State THREE (3) characteristics of a non-ideal transformer.

Nyatakan TIGA (3) ciri bagi pengubah tak unggul.

[3 marks]

[3 markah]

- CLO1
C2 (b) A step-down transformer has a turn ratio of $20:1$, a primary voltage of $4kV$ and a load of $10kW$. Neglecting losses, calculate the value of the secondary current.

Sebuah pengubah langkah turun mempunyai nisbah lilitan $20:1$, voltan primer $4kV$ dan $10kW$ beban. Dengan mengabaikan nilai kehilangan, kirakan nilai arus sekunder.

[5 marks]

[5 markah]

- (c) Referring to Figure B4(c), calculate:

Berdasarkan Rajah B4(c), kirakan:

- (i) The Voltage Induced In The Primary
Voltan Teraruh Pada Bahagian Utama
- (ii) The Secondary Current
Arus Sekunder
- (iii) The Primary Current
Arus Primer

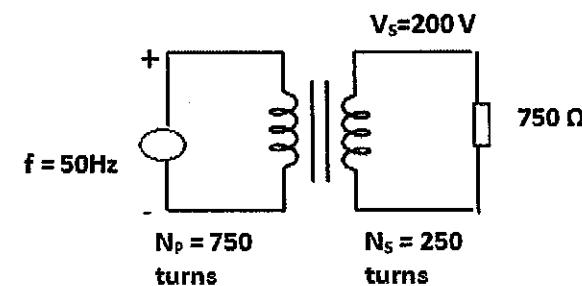


Figure B4(c) / Rajah B4(c)

[7 marks]

[7 markah]

SULIT

DET2033 : ELECTRICAL CIRCUITS

SECTION C: 30 MARKS**BAHAGIAN C: 30 MARKAH****INSTRUCTION:**

This section consists of **TWO (2)** essay questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi DUA (2) soalan eseai. Jawab SEMUA soalan.

CLO2
C3

A circuit consists of a resistor 15Ω , an inductor $0.1H$ and capacitor $80\mu F$ are connected in series to supply $100V$, $50Hz$. Calculate:

Satu litar mengandungi perintang 15Ω , pearuh $0.1H$ dan pemuat $80\mu F$ yang disambungkan secara sesiri dengan voltan masukan $100V$, $50Hz$. Kirakan:

- i) Total impedance

Jumlah galangan

- ii) Total circuit current

Jumlah arus litar

- iii) Voltage across each components

Nilai kejatuhan voltan merentasi setiap komponen

- iv) Sketch the vector diagram

Lakarkan gambarajah vektor litar

[15 marks]

[15 markah]

SULIT

DET2033 : ELECTRICAL CIRCUITS

QUESTION 2**SOALAN 2**

A circuit which consists of a 12Ω resistor, $45mH$ inductor and a $100\mu F$ capacitor is connected in series across a $220V$ AC supply. Calculate the upper and lower cut-off frequency. Then sketch and label the resonance graph Current versus Frequency with the obtained value.

Sebuah litar yang mengandungi satu perintang 12Ω , pearuh $45mH$ dan pemuat $100\mu F$ disambung secara siri merentasi bekalan AU $220V$. Kirakan nilai frekuensi terpotong atas dan bawah. Berdasarkan jawapan yang diperolehi, lakar dan label graf resonan Arus melawan Frekuensi.

[15 marks]

[15 markah]

SOALAN TAMAT