

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI
KEMENTERIAN PENDIDIKAN MALAYSIA**

JABATAN KEJURUTERAAN ELEKTRIK

PEPERIKSAAN AKHIR

SESI JUN 2018

DET1013 : ELECTRICAL TECHNOLOGY

**TARIKH : 14 NOVEMBER 2018
MASA : 8.30 PAGI - 10.30 PAGI (2 JAM)**

Kertas ini mengandungi **TIGA BELAS (13)** halaman bercetak.

Bahagian A: Objektif (10 soalan)
Bahagian B: Struktur (4 soalan)
Bahagian C: Esei (2 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

SECTION A: 10 MARKS
BAHAGIAN A: 10 MARKAH

INSTRUCTION:

This section consists of TEN (10) objective questions. Mark your answers in the OMR form provided.

ARAHAN:

Bahagian ini mengandungi SEPULUH (10) soalan objektif. Tandakan jawapan anda di dalam borang OMR yang disediakan.

CLO1

C1

1. Determine the right statement from the list below.

Tentukan pernyataan yang benar daripada senarai di bawah.

- A. A cell is a series of two or more connected battery.
Sel adalah sambungan sesiri dua atau lebih bateri yang bersambung.
- B. A battery changes electrical energy into chemical energy.
Bateri mengubah tenaga elektrik kepada tenaga kimia.
- C. A battery is a series of two or more connected cells.
Bateri adalah sambungan sesiri dua atau lebih sel.
- D. The total voltage of batteries that connected in parallel is the sum of each voltage in batteries.
Jumlah keseluruhan voltan bateri yang disambungkan secara selari adalah hasil tambah setiap voltan pada bateri.

CLO1

C2

2. Calculate the total current flowing into circuit in Figure A2.

Kirakan jumlah arus keseluruhan yang mengalir dalam litar pada Rajah A2.

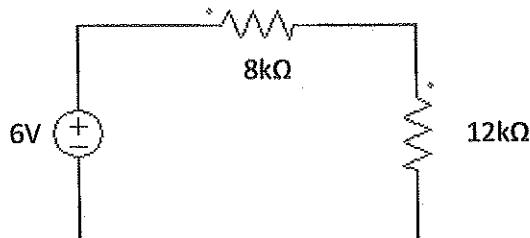


Figure A2/ Rajah A2

- A. 0.3A
- B. 300A
- C. 300mA
- D. 0.3mA

CLO1
C1

3. Identify equation that is related to the maximum power transfer.
Kenalpasti persamaan yang berkaitan dengan pindahan kuasa maksimum.

- A. $R_L = R_{TH}$
- B. $\sum I_{in} = \sum I_{out}$
- C. $\sum V_{supply} = \sum V_{drop}$
- D. $V = IR$

CLO2
C2

4. Based on Figure A4, calculate the Thevenin resistance, R_{TH} .

Berdasarkan Rajah A4, kirakan rintangan Thevenin, R_{TH} .

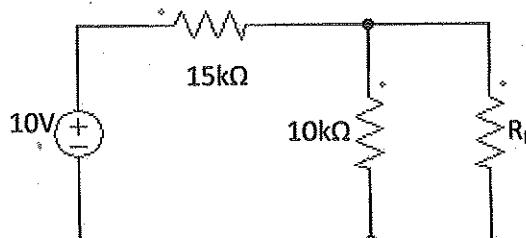


Figure A4/ Rajah A4

- A. 25kΩ
- B. 6kΩ
- C. 5kΩ
- D. 10kΩ

CLO1
C2

5. Using KCL, determine the value of current c in Figure A5.

Dengan menggunakan KCL, tentukan nilai arus c pada Rajah A5.

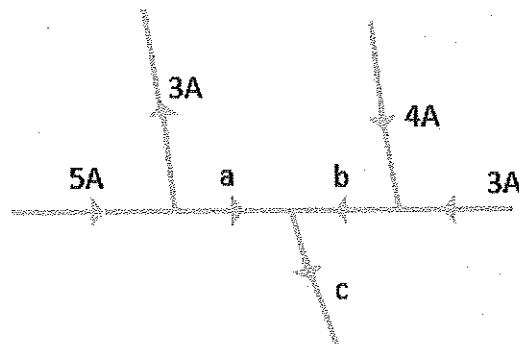


Figure A5/ Rajah A5

- | | |
|-------|--------|
| A. 5A | C. 15A |
| B. 9A | D. 4A |

CLO1
C1

6. State the material located between two plates of capacitor.

Nyatakan bahan yang terletak di antara dua plat kapasitor.

- A. Conductor
Pengalir
- B. Insulator
Penebat
- C. Induktor
Pearuh
- D. Dielectric
Dieletrik

CLO1
C2

7. Determine the total capacitance if three $30\mu F$ capacitors are connected in series.

Tentukan jumlah kemuatan jika tiga pemuat $30\mu F$ disambung secara sesiri.

- A. $10mF$
- B. $10\mu F$
- C. $90mF$
- D. $90\mu F$

CLO1
C1

8. State the definition of an inductor.

Nyatakan definisi pearuh.

- A. A component which restricts the flow of electric current
Komponen yang menyekat pengaliran arus elektrik
- B. A passive component that can store energy in an AC circuit
Komponen pasif yang boleh menyimpan tenaga dalam litar AU
- C. A component that conducts electric current in only one direction
Komponen yang menjalankan arus elektrik dalam satu arah sahaja
- D. A passive component that can store electric charge in an AC circuit
Komponen pasif yang boleh menyimpan cas elektrik di litar AU

CLO1
C2

9. Identify which of the following is NOT the characteristic of the magnetic flux.

Kenalpasti yang manakah antara yang berikut adalah BUKAN ciri fluks magnet.

- A. The flux lines are elastic and easily shaped.

Garis fluks adalah elastik dan mudah dibentuk.

- B. The flux lines will cross each other.

Garis fluks akan melintasi antara satu sama lain.

- C. The magnetic flux lines show the exiting direction from the north pole and entering direction to the south pole forming a complete loop.

Garis fluks magnet menunjukkan arah keluar dari kutub utara dan arah masuk melalui kutub selatan dan membentuk satu geling lengkap.

- D. All flux lines having the same orientation will combine and attract each other, while flux lines having the opposite orientation will repel one another.

Semua garis fluks yang mempunyai orientasi yang sama akan menarik antara satu sama lain, manakala garis fluks yang mempunyai orientasi yang bertentangan akan menolak antara satu sama lain.

CLO2
C2

10. Calculate the magnetic flux density in a magnetic field if the magnetic flux in 0.1m^2 cross sectional area is $600 \mu\text{Wb}$.

Kirakan ketumpatan fluks di dalam medan magnet jika fluks magnetik di dalam luas keratan rentas 0.1m^2 adalah $600 \mu\text{Wb}$.

- A. $6000 \mu\text{T}$

- B. $600 \mu\text{T}$

- C. 600 mT

- D. 60 T

SECTION B: 30 MARKS

BAHAGIAN B: 30 MARKAH

INSTRUCTION:

This section consists of FOUR (4) structured questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi EMPAT(4) soalan berstruktur. Jawab SEMUA soalan.

QUESTION 1

SOALAN 1

CLO1
C1

- a) State the definition of Ohm's Law.

Nyatakan definisi Hukum Ohm's.

[3 marks]

[3 markah]

CLO1
C2

- b) By referring to Figure B1(b), given that total resistance in the circuit is $1.5\text{k}\Omega$, determine R_2 .

Merujuk kepada Rajah B1(b), diberi nilai kerintangan dalam litar ialah $1.5\text{k}\Omega$, tentukan nilai R_2 .

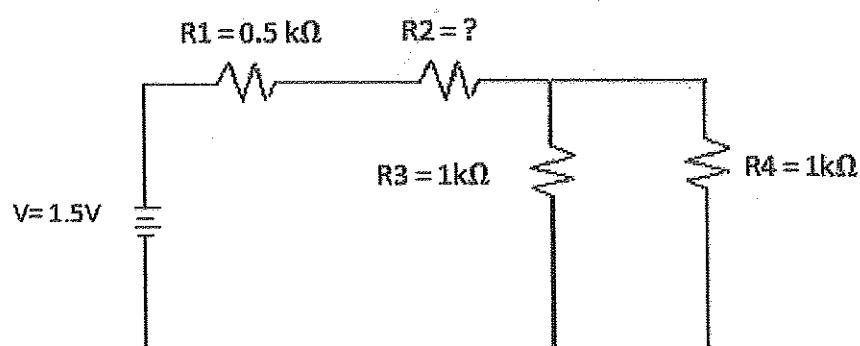


Figure B1 (b) / Rajah B1(b)

[5 marks]
[5 markah]

CLO2

C3

- c) Referring to Figure B1(c), using STAR-DELTA transformation, calculate the total resistor (R_T).

Merujuk Rajah B1 (c), menggunakan penukaran BINTANG-DELTA, Kirakan jumlah perintang(R_T).

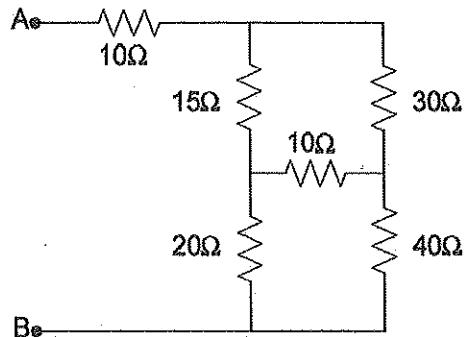


Figure B1(c) / Rajah B1(c)

[7 marks]
[7 markah]

QUESTION 2

SOALAN 2

CLO1
C1

- a) Define Norton's Theorem and sketch the NORTON'S Equivalent circuit.

Takrifkan Teorem Norton dan lakarkan litar setara Norton.

[3 marks]

[3 markah]

CLO1
C2

- b) Determine the network which is shown in Figure B2 (b) into an equivalent Thevenin circuit.

Tentukan rangkaian yang ditunjukkan dalam Rajah B2(b) kepada litar setara Thevenin.

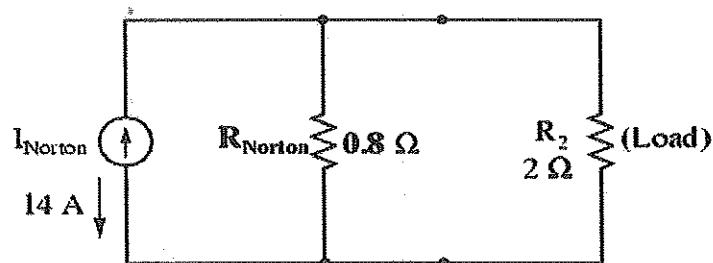


Figure B2 (b)/ Rajah B2 (b)

[5 marks]

[5 markah]

CLO 2
C3

c) Referring to Figure B2(c),

Merujuk pada Rajah B2(c),

- i. Determine the value of (R_L) to achieve maximum power transfer.

Tentukah nilai (R_L) untuk mencapai pindahan kuasa maksimum.

- ii. Calculate the current (I_L).

Kirakan nilai arus (I_L).

- iii. Calculate the maximum power (P_L).

Kirakan nilai kuasa maksimum (P_L).

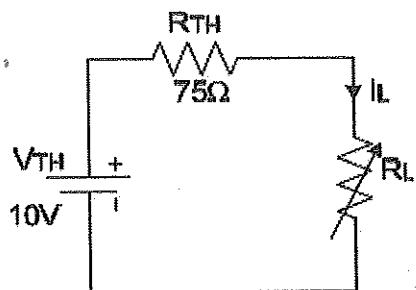


Figure B2(c)/Rajah B2(c)

[7 marks]

[7 markah]

QUESTION 3

SOALAN 3

CLO1
C2

- a) By suitable diagram, differentiate symbol between fixed inductor and variable inductor.

Dengan menggunakan gambarajah yang sesuai, bezakan simbol pearuh pearuh tetap dan pearuh boleh laras.

[3 marks]

[3 markah]

CLO1
C3

- b) Referring to Figure B3 (b), calculate the total inductance for circuit below.

Merujuk kepada Rajah B3 (b), tentukan jumlah kearahan bagi litar di bawah.

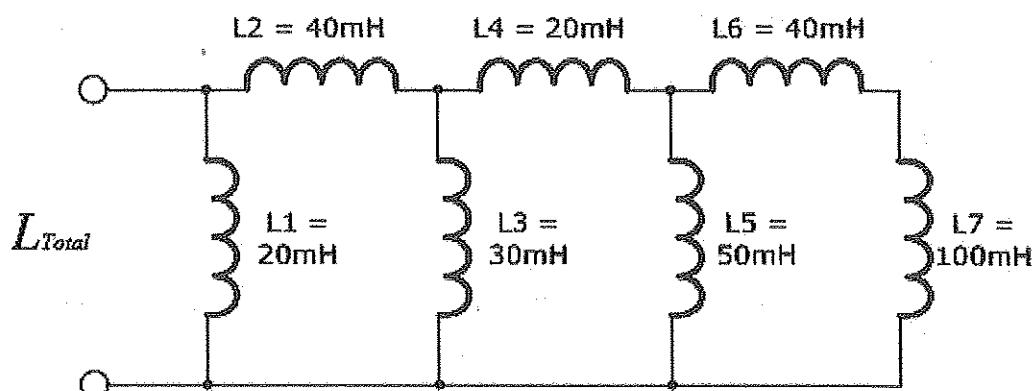


Figure B3 (b) / Rajah B3 (b)

[6 marks]

[6 markah]

CLO2
C3

- c) The winding of an electromagnet has an inductance of 3H and a resistance of 15Ω and connected to a 120V voltage supply. Calculate:

Suatu gelungan elektromagnet mempunyai kearahan sebanyak 3H and kerintangan 15Ω dan disambungkan dengan bekalan kuasa 120V. Kirakan:

- i. The maximum current flowing in the winding
Nilai arus maksima yang melalui gelung.

- ii. The time constant of the circuit.
Masa pemalar bagi litar tersebut.

- iii. The value of the induced e.m.f. after 0.1s.
Nilai bagi d.g.e terjana selepas 0.1s

[6 marks]

[6 markah]

QUESTION 4**SOALAN 4**

CLO1

C1

- a) State THREE (3) characteristics of magnetic field / flux lines.

Nyatakan TIGA (3) ciri medan magnet/garisan fluks

[3 marks]

[3 markah]

CLO 1

C2

- a) A current of 5A is passed through a 1000-turn coil wound on a circular magnetic circuit of radius 120 mm. Calculate the magnetomotive force, Fm and magnetic field strength,H.

Arus 5A melalui 1000 lilitan gegelung dalam litar magnet membentuk bulat dengan jejari 120mm. Kira daya gerak magnet, Fm dan kekuatan medan magnet,H.

[5 marks]

[5 markah]

CLO 2

C3

- b) Explain the Faraday's First Law and Faraday's Second Law with a suitable diagram.
Terangkan Hukum Faraday's Pertama dan Hukum Faraday's Kedua dan lukiskan gambarajah yang bersetujuan.

[7 marks]

[7 markah]

SECTION C: 50 MARKS**BAHAGIAN C: 50 MARKAH****INSTRUCTION:**

This section consists of TWO (2) essay questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi DUA (2) soalan eseai. Jawab SEMUA soalan.

QUESTION 1**SOALAN 1**

CLO2
C3

By applying Kirchoff's Current Law (KCL) and Kirchoff's Voltage Law (KVL), calculate the value of I_1 , I_2 and I_3 in **Figure C1**.

Dengan mengaplikasikan Hukum Arus Kirchoff (KCL) dan Hukum Voltage Kirchoff (KVL), kira nilai I_1 , I_2 dan I_3 dalam Rajah C1.

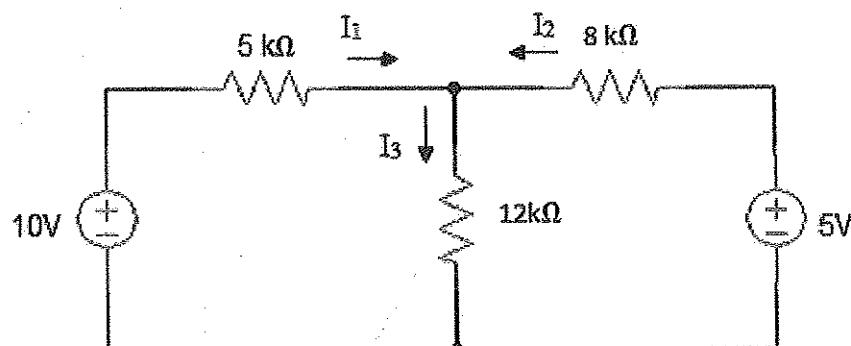


Figure C1/ Rajah C1

[15 marks]

[15 markah]

QUESTION 2

SOALAN 2

CLO2

C3

Figure C2 shows a $4700\mu F$ capacitor is connected in series with a $5.6 k\Omega$ resistor and a 6Vdc supply. When the switch is ON, calculate the time constant, initial charge current, time taken for capacitor voltage to increase to 3V, the voltage across the capacitor at 20s and energy stored in the capacitor.

Rajah C2 menunjukkan kapasitor $4700\mu F$ disambungkan secara sesiri dengan perintang $5.6 k\Omega$ dan bekalan 6V. Apabila suis dihidupkan, kirakan pemalar masa, arus awalan cas, masa diambil untuk voltan kapasitor meningkat kepada 3V, nilai voltan kapasitor pada 20s, dan tenaga yang tersimpan di dalam kapasitor.

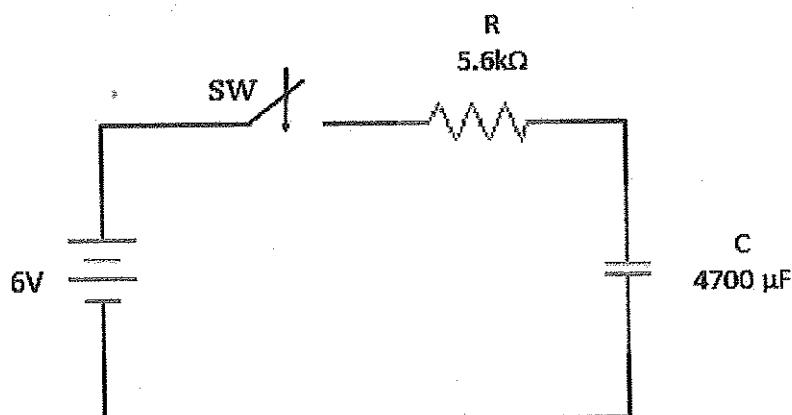


Figure C2 / Rajah C2

[15 marks]

[15 markah]

SOALAN TAMAT