

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI
KEMENTERIAN PENDIDIKAN MALAYSIA**

JABATAN KEJURUTERAAN ELEKTRIK

PEPERIKSAAN AKHIR

SESI JUN 2018

DET2033 : ELECTRICAL CIRCUITS

**TARIKH : 16 NOVEMBER 2018
MASA : 3.00 PETANG - 5.00 PETANG (2 JAM)**

Kertas ini mengandungi **SEBELAS (11)** halaman bercetak.

Bahagian A: Objektif (10 soalan)
Bahagian B: Struktur (4 soalan)
Bahagian C: Esei (2 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN
(CLO yang tertera hanya sebagai rujukan)

SULIT

SECTION A: 10 MARKS
BAHAGIAN A: 10 MARKAH

INSTRUCTION:

This section consists of TEN (10) objective questions. Mark your answers in the OMR form provided.

ARAHAN:

Bahagian ini mengandungi SEPULUH (10) soalan objektif. Tandakan jawapan anda di dalam borang OMR yang disediakan.

- CLO1 1. Identify the peak voltage when an alternating voltage is given by
 C1 $V = 75\sin(200\pi t - 0.25)$ volt.
*Berapakah nilai voltan puncak jika voltan ulang alik yang diberikan adalah,
 $V=75\sin(200\pi t - 0.25)$ volt.*
- A. 75V
 B. 200V
 C. 0.25V
 D. 53.02V
- CLO1 2. Determine the inductive reactance results in a current state
 C2 *Tentukan hasil kearuhan reaktans dalam keadaan semasa*
 A. Leads the voltage by 90°
Mendulu voltase 90°
 B. Is in phase with the voltage
Sefasa dengan voltase
 C. Leads the voltage by π rad
Mendulu voltase π rad
 D. Lags the voltage by $\pi/2$ rad
Mengekor voltase $\pi/2$ rad
- CLO1 3. Identify imaginary part in a series R-L-C circuit when resonance occurs.
 C2 *Kenal pasti bahagian khayalan dalam litar R-L-C siri apabila resonans berlaku.*
- A. 1
 B. 0.5
 C. 0
 D. 0.9

CLO1
C2

4. Select the CORRECT explanation which describes the phase current, line current and load current in a Y-Y source-load configuration.
Pilih keterangan yang BETUL yang menerangkan arus fasa, arus talian dan arus beban dalam konfigurasi sumber-beban Y-Y.
- A. Phase current, line current and load current are 120° out of phase.
Arus fasa, arus talian dan arus beban adalah berbeza fasa sebanyak 120° .
- B. Phase current, line current and load current are all equal in each phase.
Arus fasa, arus talian dan arus beban adalah kesemuanya sama fasa.
- C. Load current and line current are in phase, but both are out of phase with the phase current.
Arus beban dan arus talian adalah sama fasa, tetapi kedua-duanya berbeza fasa dengan arus fasa.
- D. Phase current and line current are in phase, but both are 120° out of phase with the load current.
Arus fasa dan arus talian adalah sama fasa, tetapi kedua-duanya adalah berbeza fasa dengan arus beban sebanyak 120° .

CLO1
C1

5. Choose the CORRECT effect in increasing the number of turns on the secondary part of a transformer.
Pilih kesan yang BETUL apabila berlaku penambahan bilangan lilitan pada bahagian sekunder sebuah pengubah.
- A. Increase the primary current
Meningkatkan arus primer
- B. Increase the secondary current
Meningkatkan arus sekunder
- C. Decrease the secondary current
Mengurangkan arus sekunder
- D. Have no effect on the secondary current
Tiada kesan ke atas arus sekunder

- CLO1 6. An ideal transformer has a turn's ratio of 2. Find the secondary power, if the primary power is 100 W.

C2 *Sebuah pengubah unggul mempunyai nisbah lilitan bersamaan 2. Cari kuasa bahagian sekunder, sekiranya kuasa bahagian primer adalah 100 W.*

- A. 50 W
- B. 75 W
- C. 100 W
- D. 200 W

- CLO2 7. Determine the frequency for the waveforms shown in Figure A(7).

C3 *Tentukan frekuensi bagi bentuk gelombang yang ditunjukkan dalam rajah A(7).*

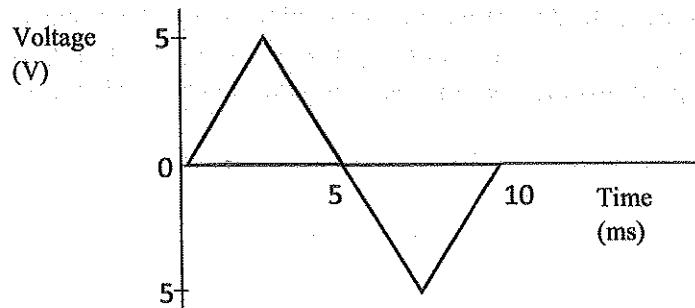


Figure A7/Rajah A7

- A. 10 Hz
- B. 0.1 Hz
- C. 100 Hz
- D. 50 Hz

- CLO2 8. Determine the capacitive reactance of a capacitor of $10\mu F$ when connected to a circuit of frequency 50 Hz.

C3 *Tentukan regangan kapasitor $10\mu F$ bila disambungkan dengan litar yang mempunyai nilai frekuensi 50 Hz.*

- A. 318.3Ω
- B. 0.796Ω
- C. 33.83Ω
- D. 31.83Ω

CLO2
C3

9. Determine the range between lower cut-off frequency, f_L and upper cut-off frequency, f_H of an RLC circuit that frequency resonant at 150 kHz and has a Q of 30.

Tentukan julat di antara frekuensi terpotong bawah, f_L dan frekuensi terpotong atas, f_H bagi satu litar RLC pada frekuensi resonans 150 kHz dan mempunyai nilai Q sebanyak 30.

- A. 100 kHz to 155 kHz
- B. 147.5 kHz to 152.5 kHz
- C. 149.97 kHz to 150.03 kHz
- D. 4500 kHz to 295.5 kHz

CLO2
C3

10. Calculate the phase current in a star connected three phase system, if given each load resistance is 30Ω per phase connected to 415V three phase supply.

Kirakan arus fasa dalam sistem tiga fasa sambungan bintang, jika diberi beban rintangan setiap fasa ialah 30Ω bersambung dengan bekalan kuasa tiga fasa 415V.

- A. 8.0 A
- B. 13.8 A
- C. 24.0 A
- D. 41.5 A

SECTION B: 60 MARKS**BAHAGIAN B: 60 MARKAH****INSTRUCTION:**

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

ARAHAN:

*Bahagian ini mengandungi **EMPAT (4)** soalan berstruktur. Jawab **SEMUA** soalan.*

QUESTION 1**SOALAN 1**

CLO1

C1

- a) Define the Amplitude, Frequency and Instantaneous Value.

Takrifkan Amplitude, Frekuensi dan Nilai seketika.

[3 marks]

[3 markah]

CLO1

C2

- b) Calculate the peak and mean values for a 240V voltage supply.

Kirakan nilai puncak dan nilai min bagi voltan bekalan 240 V.

[5 marks]

[5 markah]

CLO2

C3

- c) An alternating voltage is given by $V = 75\sin(200\pi t - 0.25)$ volts. Calculate:

Diberi voltan ulang alik $V = 75\sin(200\pi t - 0.25)$ volts. Kirakan:

- The amplitude value / *Nilai puncak*
- The peak to peak value / *Nilai puncak ke puncak*
- The r.m.s value / *Nilai p.p.g.d*
- The periodic / *Tempoh*
- The frequency / *Frekuensi*
- The phase angle (in degrees) / *Sudut fasa (dalam rajah)*

[7 marks]

[7 markah]

QUESTION 2**SOALAN 2**CLO1
C1

- a) With the aid of a diagram, state the relationship between the voltage and the current for pure capacitive circuit.

Dengan bantuan gambarajah, nyatakan hubungan antara voltan dan arus bagi litar kapasitan tulen.

[3 marks]

[3 markah]

CLO1
C2

- b) A coil has an inductance of 40mH and negligible resistance. Calculate its inductive reactance and the resulting current if connected to:

Satu gelung kearahan 40mH dan kerintangan diabaikan. Kirakan regangan aruhan dan arus yang terhasil sekiranya disambungkan pada:

- A 240V, 50Hz supply
- A 100V, 1KHz supply


[5 marks]

[5 markah]

CLO2
C3

- c) With reference to Figure B2(c), calculate the total impedance Z_T and total current I_T .

Merujuk pada Rajah B2(c), kirakan jumlah galangan dan jumlah arus.

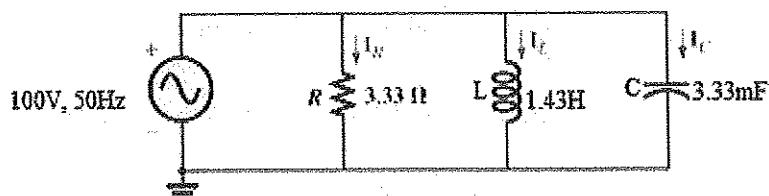**Figure B2(c)/ Rajah B2(c)**

[7 marks]

[7 markah]

QUESTION 3**SOALAN 3**

CLO1

C1

- a) List the phasor equations of the three phase voltages, E_A , E_B and E_C generated by a three-phase generator, and sketch its phasor diagram.

Senaraikan persamaan-persamaan fasa bagi tiga voltan fasa E_A , E_B dan E_C yang dijanakan oleh penjana tiga fasa, seterusnya lakarkan gambarajah fasanya.

[3 marks]

[3 markah]

CLO1

C2

- b) A three load resistance of 60Ω is connected in delta to a 500V, 3 phase supply.

Determine phase voltage and line current for the system.

Tiga beban rintangan 60Ω disambung secara delta kepada 500V, bekalan 3 fasa. Tentukan voltan fasa dan arus talian untuk sistem ini.

[5 marks]

[5 markah]

CLO2

C3

- c) A three coil balanced positive sequence Y-connected source with $E_{AN} = 100\angle 10^\circ V$ is connected to a Δ -connected balanced load with $(8+j4)\Omega$ per phase. Calculate the phase current and line current.

Tiga gelung seimbang jujukan positif bekalan sambungan Y dengan $E_{AN} = 100\angle 10^\circ V$ disambung kepada beban seimbang sambungan Δ dengan $(8+j4)\Omega$ setiap fasa. Kirakan arus fasa dan arus talian.

[7 marks]

[7 markah]

QUESTION 4**SOALAN 4**

CLO1

C1

- a) List THREE (3) types of transformer.

Senaraikan TIGA (3) jenis pengubah.

[3 marks]

[3 markah]

CLO1

C2

- b) An ideal transformer is connected to a power supply 240V, supplies a lamp of 12V, 150W. Calculate the transformer turns ratio and the current taken from the supply.

Sebuah pengubah unggul disambung kepada bekalan kuasa 240V, membekalkan lampu 12V, 150W. Kirakan nisbah lilitan pengubah dan arus pada bekalan kuasa.

[5 marks]

[5 markah]

CLO2

C3

- c) A 7.5kVA single phase transformer has a turns ratio of 8:1 and is fed from a 3kV supply. By neglecting losses, determine:

Sebuah pengubah satu fasa 7.5kVA mempunyai nisbah lilitan 8:1 dan dibekalkan dengan bekalan kuasa 3kV. Dengan mengabaikan kehilangan, tentukan:

- i. The full load secondary current

Arus sekunder beban penuh

- ii. The minimum load resistance which can be connected across the secondary winding to give full load kVA

Beban rintangan minimum yang boleh disambung merentangi belitan sekunder untuk menghasilkan kVA beban penuh

- iii. The primary current at full load kVA

Arus primer pada kVA beban penuh

[7 marks]

[7 markah]

SULIT

SECTION C: 30 MARKS**BAHAGIAN C: 30 MARKAH****INSTRUCTION:**

This section consists of TWO (2) essay questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi DUA (2) soalan eseai. Jawab SEMUA soalan.

QUESTION 1**SOALAN 1**

CLO2
C3

With reference to Figure C1, determine the total current flow (I) and sketch the voltage phase diagram of the circuit.

Merujuk kepada Rajah C1, tentukan jumlah nilai jumlah arus (I) dan lakarkan gambarajah voltan fasa litar tersebut.

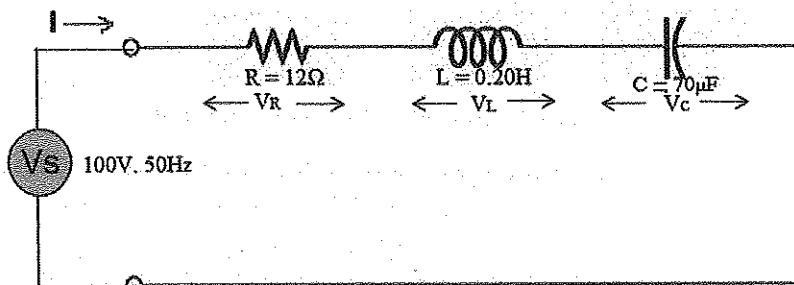


Figure C1 / Rajah C1

[15 marks]

[15 markah]

QUESTION 2**SOALAN 2**CLO2
C3

An RLC series circuit has a resonant frequency of 2kHz and a Q-factor at resonance of 40. If the impedance of the circuit at resonance is 30Ω , determine the values of:

Satu litar siri RLC mempunyai frekuensi resonan 2kHz dan faktor-Q 40 semasa resonan. Jika galangan litar semasa resonan ialah 30Ω , tentukan nilai-nilai berikut:

- i) The inductance

Kearuhan

- ii) The capacitance

Kemuatan

- iii) The bandwidth

Lebar jalur

- iv) The lower and upper cut-off frequencies

Frekuensi terpotong bawah dan frekuensi terpotong atas

- v) Sketch current versus frequency and label f_L , f_H , and f_r .

Lakarkan graf arus melawan frekuensi dan labelkan f_L , f_H and f_r .

[15 marks]

[15 markah]

SOALAN TAMAT