

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK
KEMENTERIAN PENDIDIKAN TINGGI**

JABATAN KEJURUTERAAN ELEKTRIK

**PEPERIKSAAN AKHIR
SESI DISEMBER 2017**

DET2033 : ELECTRICAL CIRCUITS

**TARIKH : 01 APRIL 2018
MASA : 2.30 PETANG - 4.30 PETANG (2 JAM)**

Kertas ini mengandungi **SEPULUH (10)** halaman bercetak.

Bahagian A: Objektif (10 soalan)
Bahagian B: Struktur (4 soalan)
Bahagian C: Esei (2 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

SECTION A : 10 MARKS
BAHAGIAN A : 10 MARKAH

INSTRUCTION:

This section consists of TEN (10) objective questions. Mark your answers in the OMR form provided.

ARAHAH :

Bahagian ini mengandungi SEPULUH (10) soalan objektif. Tandakan jawapan anda di dalam borang OMR yang disediakan.

- CLO1
C1
1. Select the correct statement on alternating current.
Pilih pernyataan yang betul berkaitan arus ulang alik
 - A. Constant magnitude and direction
Magnitud dan arah tetap
 - B. Varied magnitude but constant direction
Magnitud berubah tetapi arah tetap
 - C. Varied magnitude and direction
Magnitud dan arah berubah
 - D. Varied direction but constant magnitude
Arah berubah tetapi magnitud tetap
- CLO1
C2
2. Determine the voltage across the capacitor in RC series circuit.
Kenalpasti voltan yang merentasi kapasitor di dalam litar siri RC.
 - A. Voltage and current are in phase
Voltan dan arus adalah sefasa
 - B. Voltage lags current by 90°
Voltan mengekori arus sebanyak 90°
 - C. Voltage leads current by 90°
Voltan mendahului arus sebanyak 90°
 - D. Voltage lags current by 120°
Voltan mengekori arus sebanyak 120°
- CLO1
C2
3. Describe the condition during resonance in RLC series circuit
Terangkan keadaan semasa resonan di dalam litar siri RLC.
 - A. The total current in the circuit becomes minimum
Jumlah arus di dalam litar menjadi minimum
 - B. The total impedance of circuit becomes maximum
Jumlah galangan di dalam litar menjadi maksimum

C. The total current in the circuit is equal to the total impedance
Jumlah arus di dalam litar adalah sama dengan jumlah galangan

D. The total current in the circuit becomes maximum
Jumlah arus di dalam litar menjadi maksimum

CLO1
C2 4. Choose the correct statement about delta connection in three phase system.
Pilih pernyataan yang betul mengenai sambungan delta di dalam sistem tiga fasa.

A. Line voltage is equal to phase voltage
Voltan talian adalah sama dengan voltan fasa

B. Line current is equal to phase current
Arus talian adalah sama dengan arus fasa

C. Line Voltage is 3 times phase voltage
Voltan talian adalah 3 kali voltan fasa

D. Line voltage is $\sqrt{3}$ times of phase voltage
Voltan talian adalah $\sqrt{3}$ kali voltan fasa

CLO1
C1 5. Identify the main function of a transformer.
Kenalpasti fungsi utama pengubah.

A. To change direct current (dc) to alternating current (ac)
Untuk menukar arus terus (dc) kepada arus ulang alik (ac)

B. To step up or step down ac voltage
Untuk menaikkan atau menurunkan voltan ac

C. To change alternating current (ac) to direct current (dc)
Untuk menukar arus ulang alik (ac) kepada arus terus (dc)

D. To step up or step down circuit impedance
Untuk menaikkan atau menurunkan galangan litar

CLO1
C2 6. Identify the characteristics of non-ideal transformer.
Kenalpasti ciri-ciri pengubah tidak unggul.

i. Winding resistance
Rintangan lilitan

ii. Magnetic flux leakage
Kebocoran fluks magnet

iii. Winding capacitance
Kapasitan lilitan

- iv. Loss in the core
Kehilangan di dalam teras

- A. i,ii
- B. ii,iii,iv
- C. i,ii,iv
- D. i,ii,iii,iv

CLO2 7. Calculate the value of average voltage for the circuit given by the equation
 C3 $V(t) = 100 \sin(280t + 40^\circ)$ volt.

*Kirakan nilai voltan purata bagi litar yang diberi oleh persamaan
 $V(t) = 100 \sin(280t + 40^\circ)$ volt.*

- A. 0.707 V
- B. 70.7 V
- C. 0.637 V
- D. 63.7 V

CLO2 8. A resistor of 50Ω and inductor $0.15H$ are connected in series to $240V, 50Hz$ supply. Calculate the total impedance of the circuit.
 C3 *Satu perintang 50Ω dan pearuh $0.15H$ disambungkan secara siri dengan bekalan $240V, 50Hz$. Kirakan jumlah galangan litar.*

- A. $68.7 \angle 43.29^\circ \Omega$
- B. $67.8 \angle 76.0^\circ \Omega$
- C. $76.0 \angle 67.8^\circ \Omega$
- D. $0.76 \angle 68.7^\circ \Omega$

CLO2 9. Based on Figure A9, calculate the value of the capacitor if the resonance frequency of the circuit is $100Hz$.
 C3 *Berdasarkan Rajah A9, kira nilai pemuat sekiranya frekuensi salun litar adalah $100Hz$.*

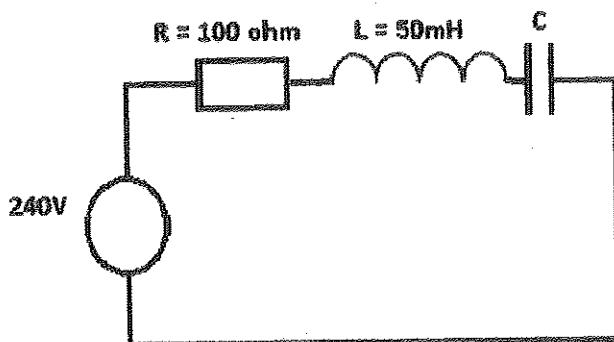


Figure A9/ Rajah A9

- A. $5.07 \mu F$
- B. $7.05 \mu F$
- C. $50.7 \mu F$
- D. $0.75 \mu F$

- CLO2
C3
10. A balanced load with delta connection has 20Ω resistor in series with $159.2mH$ inductor is supplied with $400V, 50Hz$. Calculate the line current.
Satu beban seimbang yang disambung secara delta mempunyai perintang 20Ω sesiri dengan pearuh $159.2mH$ dibekalkan dengan $400V, 50Hz$. Kira arus talian.
- A. 12.87 A
 B. 7.43 A
 C. 53.85 A
 D. 74.3 A

SECTION B : 60 MARKS***BAHAGIAN B : 60 MARKAH*****INSTRUCTION:**

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

ARAHAN:

*Bahagian ini mengandungi **EMPAT (4)** soalan berstruktur. Jawab **SEMUA** soalan.*

QUESTION 1***SOALAN 1***

- CLO1
C1
- (a) List **TWO (2)** methods to generate alternating current.
*Senaraikan **DUA (2)** kaedah untuk menjana arus ulangalik.*
- [3 marks]
 [3 markah]
- CLO1
C2
- (b) Calculate the rms voltage if peak to peak value voltage is $14V$.
Kirakan nilai voltan ppgd jika nilai voltan puncak ke puncak adalah $14V$.
- [5 marks]
 [5 markah]
- CLO2
C3
- (c) The current in an AC circuit at any time t seconds is given by
 $i = 20 \sin (60\pi t + 0.38)$ A. Calculate the period, frequency and the value of the current when $t = 0$.
Arus yang mengalir melalui litar AU pada mana -mananya masa t saat adalah $i = 20 \sin (60\pi t + 0.38)$ A. Kirakan tempoh, frekuensi dan nilai arus ketika $t = 0$.
- [7 marks]
 [7 markah]

QUESTION 2**SOALAN 2**CLO1
C1

- (a) Draw a phasor diagram to represent relation between current and voltage for a purely resistive AC circuit, a purely inductive AC circuit and a purely capacitive AC circuit.

Lakarkan gambarajah fasa untuk menunjukkan hubungan antara arus dan voltan bagi litar AU rintangan tulen, litar AU induktif tulen dan litar AU kapasitif tulen.


[3 marks]

[3 markah]

CLO1
C2

- (b) By referring to the **Figure B2 (b)**, determine the total impedance, Z_T for the series circuit which has a frequency of 30 kHz.

*Dengan merujuk kepada **Rajah B2 (b)**, tentukan jumlah galangan, Z_T untuk litar siri tersebut yang mempunyai frekuensi 30kHz.*

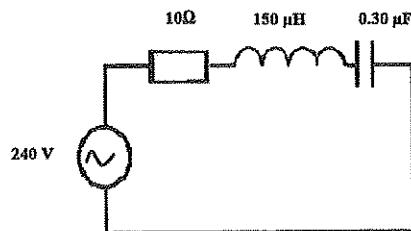**Figure B2 (b) / Rajah B2 (b)**

[5 marks]

[5 markah]

CLO2
C3

- (c) With reference to the Figure B2(c), calculate the value of the total current, I_T flowing in the circuit.

Dengan merujuk kepada Rajah B2(c), kirakan jumlah arus, I_T yang mengalir di dalam litar.

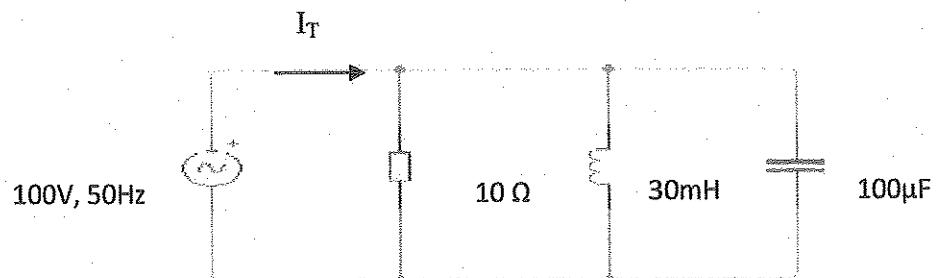


Figure B2 (c) / Rajah B2 (c)

[7 marks]

[7 markah]

QUESTION 3***SOALAN 3***CLO1
C1

- (a) List THREE (3) advantages of a three phase system.

Senaraikan TIGA (3) kebaikan bagi sistem tiga fasa.

[3 marks]

[3 markah]

CLO1
C2

- (b) Draw and label the circuit diagram for star connection in a three phase system.

Lukis dan label gambarajah litar sambungan bintang di dalam sistem tiga fasa.

[5 marks]

[5 markah]

CLO2
C3

- (c) Each phase in Delta connection consists of
- 10Ω
- resistor and connected in series with the inductor,
- $0.019H$
- . This three phase load is supplied with line voltage,
- $415V$
- and frequency,
- $50Hz$
- . Calculate the phase and line current.

Setiap fasa di dalam sambungan Delta terdiri daripada perintang 10Ω yang disambung secara siri dengan induktor $0.019H$. Beban tiga fasa ini dibekalkan dengan voltan talian $415V$ dan frekuensi $50Hz$. Tentukan nilai arus fasa dan arus talian.

[7 marks]

[7 markah]

QUESTION 4

SOALAN 4

CLO1
C1

- (a) Define mutual inductance.
Definaskan aruhan saling.

[3 marks]
[3 markah]

CLO1
C2

- (b) Based on the Figure B4(b), determine the type of transformer and identify THREE (3) advantages of this transformer.

Berdasarkan kepada Rajah B4 (b), nyatakan jenis pengubah dan kenalpasti TIGA (3) kelebihan pengubah ini.

[5 marks]
[5 markah]

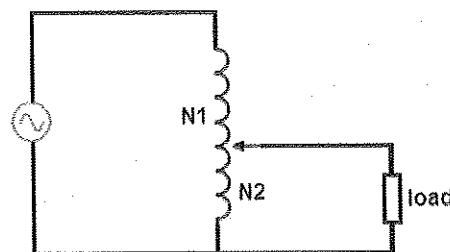


Figure B4(b) / Rajah B4(b)

CLO2
C3

- (c) By referring to the Figure B4 (c), calculate the ratio between primary and secondary winding and the primary current of the transformer. Assuming the transformer is an ideal transformer.

Dengan merujuk kepada Rajah B4 (c), kirakan nisbah antara lilitan primer dan lilitan sekunder dan arus primer pengubah tersebut. Andaikan pengubah tersebut adalah pengubah unggul.

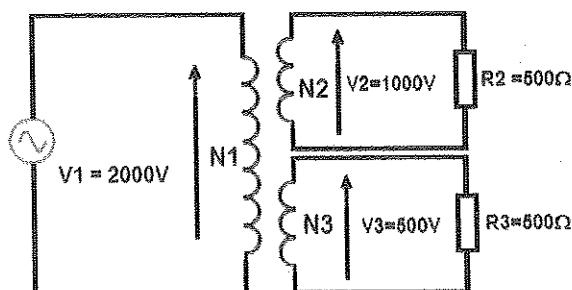


Figure B4 (c) / Rajah B4 (c)

[7 marks]
[7 markah]

SECTION C : 30 MARKS**BAHAGIAN C : 30 MARKAH****INSTRUCTION:**

This section consists of TWO (2) essay questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi TWO (2) soalan esei. Jawab SEMUA soalan.

QUESTION 1**SOALAN 1**

CLO2
C3

A 90Ω resistor, $0.3H$ inductor, $10\mu F$ capacitor and $1H$ inductor are connected in series to $100V$, $50Hz$ supply. Calculate the voltage across each component and real power dissipation of the circuit

Satu perintang 90Ω , peraruh $0.3H$, kapasitor $10\mu F$ dan pearuh $1H$ telah disambung secara siri kepada bekalan $100V, 50Hz$. Kirakan voltan merentasi setiap komponen dan pelesapan kuasa sebenar litar.

[15marks]

[15 markah]

QUESTION 2**SOALAN 2**

CLO2
C3

A series resonance circuit consists of 50Ω resistor, a capacitor of $8\mu F$ and an inductor of $40mH$. When the circuit is connected to a $10V$ AC supply, calculate the current and the lower cut-off frequency and upper cut-off frequency during resonance. Then sketch and label the resonance graph current versus frequency with the obtained value.

Satu litar salun sambungan secara sesiri terdiri daripada perintang 50Ω , kapasitor $8\mu F$ dan pearuh $40mH$. Apabila litar disambungkan kepada bekalan kuasa $10V$ AU kira arus dan frekuensi terpotong bawah dan frekuensi terpotong atas ketika salun berlaku. Kemudian lakukan dan label graf salun arus melawan frekuensi berdasarkan nilai yang diperolehi.

[15marks]

[15 markah]

SOALAN TAMAT