

SULIT



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENDIDIKAN POLITEKNIK
KEMENTERIAN PENDIDIKAN TINGGI**

JABATAN KEJURUTERAAN ELEKTRIK

**PEPERIKSAAN AKHIR
SESI DISEMBER 2016**

DEE2023: SEMICONDUCTOR DEVICES

**TARIKH : 04 APRIL 2017
MASA : 2.30 PM – 4.30 PM (2 JAM)**

Kertas ini mengandungi **DUABELAS (12)** halaman bercetak.

Bahagian A : Objektif (10 soalan)

Bahagian B : Struktur (4 soalan)

Bahagian C : Esei (2 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

SECTION A : 10 MARKS
BAHAGIAN A : 10 MARKAH

INSTRUCTION:

This section consists of **TEN (10)** objective questions. Mark your answers in the OMR form provided.

ARAHAN:

Bahagian ini mengandungi **SEPULUH (10)** soalan objektif. Tandakan jawapan anda di dalam borang OMR yang disediakan.

CLO1
C1

1. The p-type semiconductor is produced by doping _____ atoms into a pure semiconductor.

Separuh pengalir jenis- p dihasilkan melalui pendopanan atom _____ ke dalam separuh pengalir tulen.

- A. Tetravalence / tetravalens
- B. Electrovalence / elektrovalens
- C. Pentavalence / pentavalens
- D. Trivalence / trivalens

CLO1
C2

2. A P-N junction acts as a closed switch when it _____.

Simpang P-N menjadi seperti suis tertutup apabila ia _____.

- A. cannot overcome its barrier voltage
tidak boleh melepas voltan sawar
- B. has a wide depletion region
mempunyai kawasan susutan yang luas
- C. is reversed biased
dipincang balikan
- D. has a low junction resistance
mempunyai rintangan simpang yang rendah

CLO1
C1

3. Figure A(3) as shown below represents an output waveform where t_0 to t_1 is representing the output waveform of positive half-cycle, while t_1 to t_2 is representing the output waveform of the negative half-cycle. Identify the correct circuit which can generate the waveform.

Rajah A(3) seperti yang ditunjukkan di bawah merupakan satu bentuk gelombang keluaran yang mana t_0 hingga t_1 mewakili gelombang keluaran positif setengah kitaran, manakala t_1 hingga t_2 mewakili gelombang keluaran separuh kitaran negatif. Kenal pasti litar yang betul yang boleh menjana gelombang tersebut.

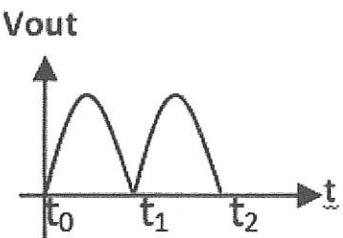
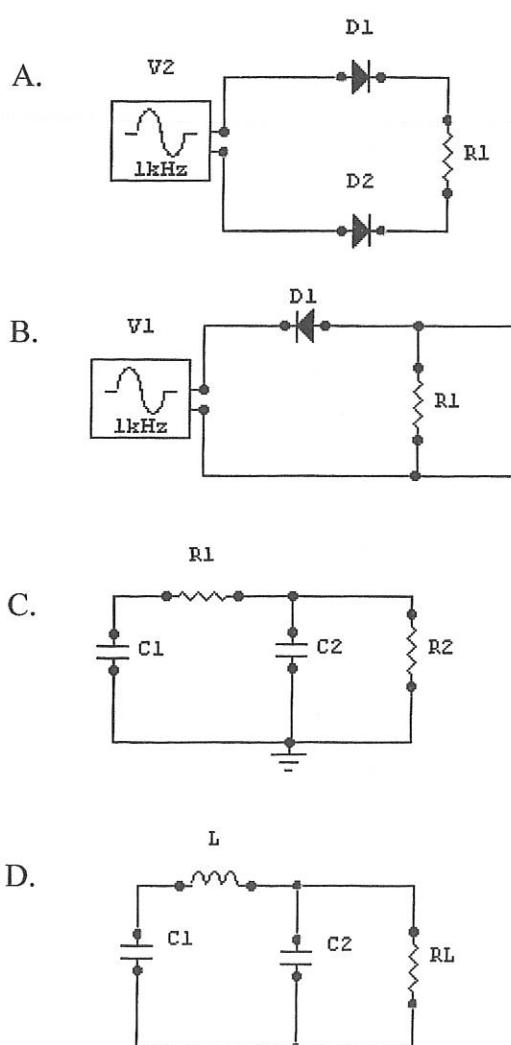


Figure A(3)
Rajah A(3)

CLO2
C3

4. In the full-wave rectifier circuit in figure A(4), the transformer primary winding is connected across an AC source of 230V (rms), 50Hz. For this circuit, calculate the DC output voltage.

Dalam litar penerus gelombang penuh bagi rajah A(4), gelung pengubah utama disambungkan menerusi sumber AU 230V (rms), 50Hz. Bagi litar ini, kirakan voltan keluaran AT.

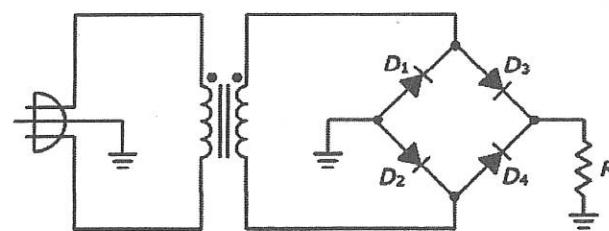


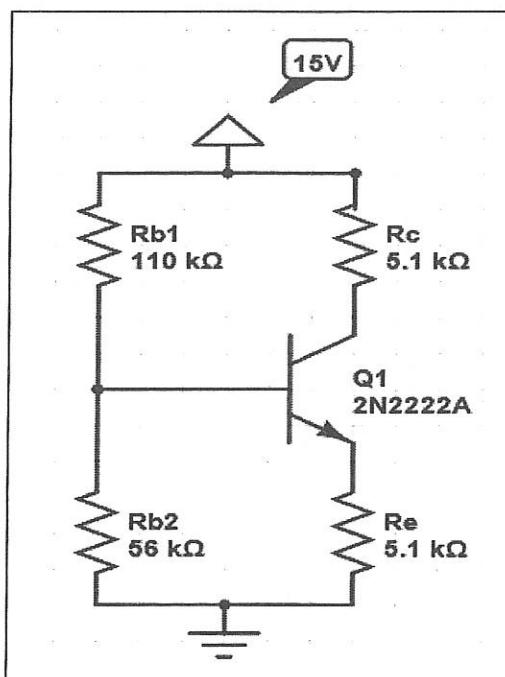
Figure A(4)
Rajah A(4)

CLO1
C1

- A. 230V
B. 460V
C. 207V
D. 325V
5. The meaning of DC Operating Point (Q-Point) is
Maksud Titik Operasi AT (Q-Point) adalah
- A. The saturation currents and voltages that are present at the terminals of device when DC supplies are connected to it.
Arus dan voltan tepu yang terdapat di terminal peranti apabila bekalan AT disambungkan kepadanya.
- B. The breakdown currents and voltages that are present at the terminals of device when DC supplies are connected to it
Arus dan voltan pecahbat yang terdapat di terminal peranti apabila bekalan AT disambungkan kepadanya
- C. The quiescent (or idle) currents and voltages that are present at the terminals of device when DC supplies are connected to it.
Arus dan voltan tenang yang terdapat di terminal peranti apabila bekalan AT disambungkan kepadanya.
- D. The load currents and voltages that are present at the terminals of device when DC supplies are connected to it
Arus dan voltan beban yang wujud pada terminal peranti apabila bekalan AT disambungkan.

CLO2
C3

6.

Figure A(6)
Rajah A(6)


Referring to Figure A(6), given $R_{b1}=110\text{ k}\Omega$, $R_{b2}=56\text{ k}\Omega$, $R_c=5.1\text{ k}\Omega$, $R_e=5.1\text{k}\Omega$ and $V_{cc}=15\text{V}$, calculate the value for $I_{c(sat)}$.

Merujuk Rajah A(6), diberi $R_{b1}=110\text{k}\Omega$, $R_{b2}=56\text{k}\Omega$, $R_c=5.1\text{k}\Omega$, $R_e=5.1\text{k}\Omega$ dan $V_{cc}=15\text{V}$, kira nilai $I_{c(sat)}$.

- A. 14.7mA
- B. 147mA
- C. 1.47mA
- D. 1.47nA

CLO1
C2

7.

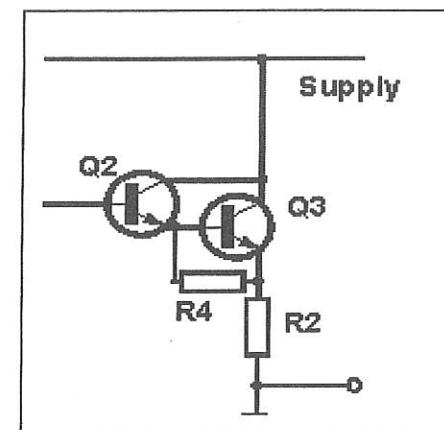Figure A(7)
Rajah A(7)

Referring to the circuit in Figure A(7), name the circuit.

Merujuk kepada litar dalam Rajah A(7), namakan litar tersebut.

- A. The CE-CC configuration
Konfigurasi CE-CC
 - B. The Darlington Pair
Pasangan Darlington
 - C. RC Coupling circuit
Litar penjodoh RC
 - D. The bypass capacitor
Pemuat pintasan
8. A JFET always operates when
JFET sentiasa beroperasi apabila
- A. The gate to source pn junction reverse-biased
Get ke punca simpang pn dalam pincang songsang
 - B. The gate to source pn junction forward-biased
Get ke punca simpang pn dalam pincang depan
 - C. The drain connected to ground
Salur disambungkan ke bumi
 - D. The gate connected to the source
Get disambungkan ke punca

CLO1
C2

9. In JFET, electric charge flow through a semiconducting channel between _____ and _____ terminal.

Dalam JFET, cas elektrik mengalir melalui saluran separapengalir di antara terminal _____ dan _____


- A. Source,drain
Punca, salur
- B. Gate,source
Get, punca
- C. Gate,drain
Get, salur
- D. Source,gate
Punca, get

CLO1
C1


10. Which physical structure represent DIAC?

Struktur fizikal manakah yang mewakili DIAK?


A.

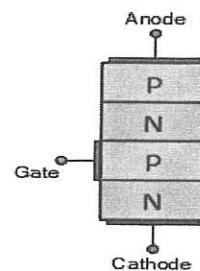


B.

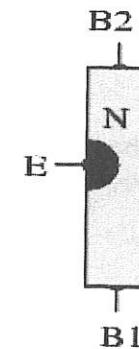

C.

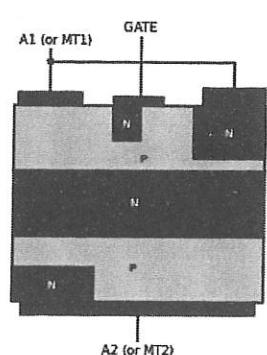

D.

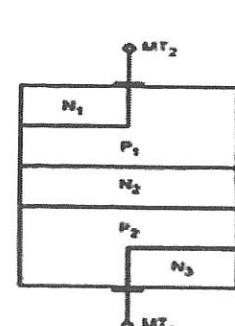

SECTION B : 60 MARKS
BAHAGIAN B : 60 MARKAH

INSTRUCTION:

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi **EMPAT (4)** soalan berstruktur. Jawab semua soalan.

QUESTION 1**SOALAN 1**CLO1
C1

- a) List down **THREE (3)** types of material that are classified in semiconductor's family.

*Senaraikan **TIGA (3)** jenis bahan yang tergolong dalam keluarga semikonduktor.*

[3 marks]
[3 markah]

CLO1
C2

- b) Differentiate **TWO (2)** between N-Type material and P-Type material.

*Bezakan **DUA (2)** di antara bahan jenis N dan bahan jenis P.*

[5 marks]
[5 markah]

CLO2
C3

- c) Discuss the operation of forward biased and the effect of depletion layer.

Bincangkan operasi bagi pincang hadapan dan kesannya ke atas lapisan susutan.

[7 marks]
[7 markah]

CLO1
C1**QUESTION 2****SOALAN 2**

- a) State **TWO (2)** types of Field Effect Transistor (FET)

Nyatakan DUA (2) jenis Transistor Kesan Medan

[3 marks]
[3 markah]

CLO2
C2

- b) Describe briefly the construction of a MOSFET in enhancement mode.

Huraikan dengan jelas binaan MOSFET bagi mod-enhancement.

[5 marks]
[5 markah]

CLO2
C3

- c) Relate **ONE (1)** similarities and **TWO (2)** differences between JFET and MOSFET .

Huraikan SATU (1) persamaan dan DUA (2) perbezaan diantara JFET dan MOSFET.

[7 marks]
[7 markah]

QUESTION 3**SOALAN 3**CLO1
C2

- a) Describe multistage amplifier.

Terangkan penguat pelbagai peringkat.

[3 marks]
[3 markah]

CLO2
C3

- b) Using a suitable diagram, illustrate the operation of Darlington Pair.

Dengan menggunakan gambarajah yang sesuai, ilustrasikan operasi litar Darlington Pair.

[6 marks]
[6 markah]

CLO2
C3

- c) Based on the Figure B3(c), calculate the gain of second stage (A2), input voltage at the first stage (V1) and overall voltage gain in dB if the output at the first stage (V2) is 0.2Vrms and the output voltage at the second stage (V3) is 4Vrms.

Merujuk kepada Rajah B3(c), kirakan gandaan pada peringkat kedua (A2), voltan masukan pada peringkat pertama (V1) dan voltan gandaan keseluruhan dalam dB jika voltan keluaran pada peringkat pertama (V2) adalah 0.2Vrms dan voltan keluaran pada peringkat kedua (V3) adalah 4Vrms.

$V3 = 4 \text{ Vrms}$

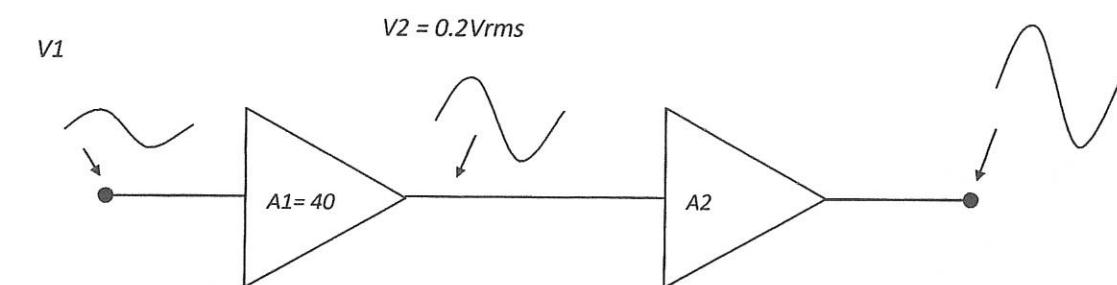


Figure B3(c) / Rajah B3(c)

[6 marks]
[6 markah]

QUESTION 4**SOALAN 4**CLO1
C1

- a) List **THREE (3)** other electronic devices
Senaraikan TIGA (3) peranti elektronik yang lain

[3 marks]
[3 markah]

CLO1
C3

- b) Sketch the symbol of SCR and relate **TWO (2)** its applications.
Lakarkan simbol SCR dan nyatakan DUA (2) kegunaannya.

[5 marks]
[5 markah]

CLO2
C3

- c) Draw the graph for I-V characteristic of SCR
Lukis bagi graf ciri I-V untuk SCR

[7 marks]
[7 markah]

SECTION C : 30 MARKS
BAHAGIAN C : 30 MARKAH

INSTRUCTION:

This section consists of TWO (2) essay questions. Answer ALL questions.

ARAHAN:

Bahagian ini mengandungi DUA (2) soalan eseai. Jawab semua soalan.

CLO2
C3

QUESTION 1**SOALAN 1**

Referring to the common emitter circuit in Figure C1, if the transistor used is silicon. Calculate the value of I_B , I_C , V_{CQ} , $I_{C\text{ (saturation)}}$ and $V_{C\text{ (cut off)}}$. Given $V_{BE} = 0.7V$ and $\beta = 50$.

Dengan merujuk kepada litar pemancar sepunya di Rajah C1, transistor yang digunakan adalah silikon. Tentukan nilai bagi I_B , I_C , V_{CQ} , $I_{C\text{ (tepu)}}$ dan $V_{C\text{ (potong)}}$. Diberi $V_{BE} = 0.7V$ dan $\beta = 50$.

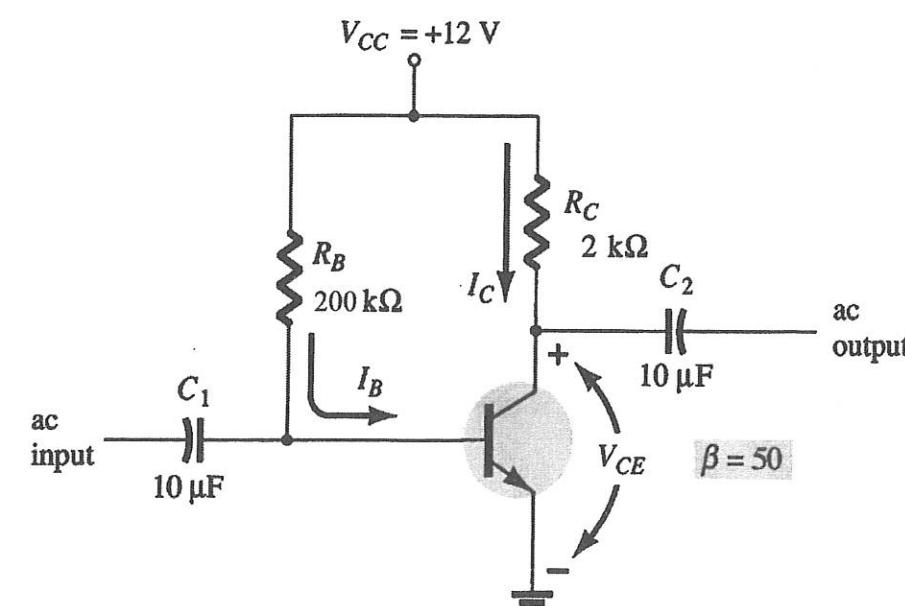


Figure C1 / Rajah C1

[15 marks]
[15 markah]

QUESTION 2**SOALAN 2**

CLO2
C3

By using a suitable diagram, illustrate the operation of a two diode full-wave rectifier circuit in detail.

Dengan menggunakan gambarajah yang bersesuaian, ilustrasikan dengan jelas operasi penerus gelombang penuh dua diod.

[15 marks]

[15 markah]

SOALAN TAMAT