

SULIT



BAHAGIAN PEPERIKSAAN DAN PENILAIAN
JABATAN PENGAJIAN POLITEKNIK
KEMENTERIAN PENGAJIAN TINGGI

JABATAN KEJURUTERAAN ELEKTRIK

PEPERIKSAAN AKHIR
SESI JUN 2013

EU801: BIOMEDICAL SENSOR AND TRANSDUCERS

TARIKH : 23 OKTOBER 2013
TEMPOH : 2 JAM (2.30 PM – 4.30 PM)

Kertas ini mengandungi **TUJUH (7)** halaman bercetak.

Bahagian A: Struktur (10 soalan)

Bahagian B: Esei (3 soalan)

Dokumen sokongan yang disertakan : Tiada

JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN

(CLO yang tertera hanya sebagai rujukan)

SULIT

SULIT

EU801: BIOMEDICAL SENSOR AND TRANSDUCERS

SECTION A : 40 MARKS

BAHAGIAN A : 40 MARKAH

INSTRUCTION:

This section consists of **TEN (10)** structured questions. Answer **ALL** questions.

ARAHAN:

Bahagian ini mengandungi **SEPULUH (10)** soalan berstruktur. Jawab semua soalan.

QUESTION 1

SOALAN 1

Define sensor and transducer.

Definisikan sensor dan transduser.

[4 marks]

[4 markah]

CLO1

C1

CLO1

C2

QUESTION 2

SOALAN 2

Describe the sensor characteristics listed below:

Terangkan ciri-ciri sensor di bawah:

- i. Sensitivity
Kepekaan
- ii. Noise
Hingar

[4 marks]

[4 markah]

CLO1

C2

QUESTION 3

SOALAN 3

Explain how limitation in capacitance measurement is applied in deciding the design in detector circuit.

Terangkan bagaimana had pengukuran kapasitan digunakan dalam penentuan rekabentuk litar pengesan.

[4 marks]

[4 markah]

CLO1

QUESTION 4**SOALAN 4**

A resistive position transducer with full output wiper 9 cm as Figure 1. Total of resistance to circuit is $4.5\text{k}\Omega$. A 25V power supply was connected to the circuit.

Determine the output voltage of the circuit if the wiper is at position:

Sebuah pengesan kerintangan dengan jumlah panjang gelangsa 9cm seperti Rajah 1.

Jumlah kerintangan bagi litar tersebut adalah $4.5\text{k}\Omega$. Satu sumber bekalan kuasa 25v telah disambung kepada litar tersebut. Kira voltan keluaran untuk litar tersebut

sekiranya gelangsa tersebut berada pada posisi berikut:

a) 9cm

b) 3cm

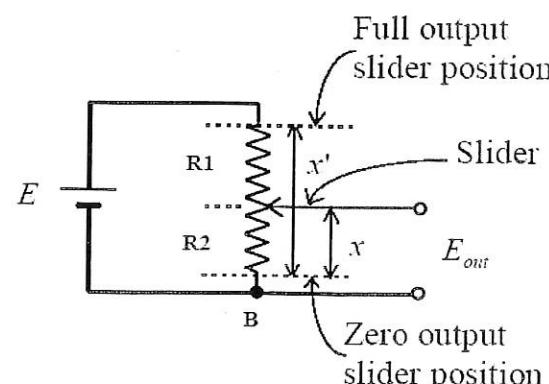


Figure 1 / Rajah 1

[4 marks]

[4 markah]

CLO1
C1**QUESTION 5****SOALAN 5**

List **TWO (2)** methods for air flow measurement.

Senaraikan DUA (2) kaedah pengukuran pergerakan udara.

[4 marks]

[4 markah]

CLO1
C4**QUESTION 6****SOALAN 6**

During experiments with a copper-constants thermocouple it was found that $c = 3.75 \times 10^{-2} \text{ mV}/^\circ\text{C}$ and $k = 4.5 \times 10^{-5} \text{ mV}/^\circ\text{C}^2$. If $T_1=150^\circ\text{C}$ and the cold junction T2 is kept in ice. Compute the output voltage.

Dalam eksperimen copper-constants thermocouple didapati bahawa $c = 3.75 \times 10^{-2} \text{ mV}/^\circ\text{C}$ dan $k = 4.5 \times 10^{-5} \text{ mV}/^\circ\text{C}^2$. Jika $T_1 = 150^\circ\text{C}$ dan simpang sejuk T2 diletakkan dalam ais. Kirakan voltan keluaran.

[4 marks]

[4 markah]

CLO1
C2**QUESTION 7****SOALAN 7**

Explain how motion artifact can be happen in ECG measurement.

Terangkan bagaimana motion artifact boleh berlaku semasa pengukuran ECG.

[4 marks]

[4 markah]

CLO1
C3**QUESTION 8****SOALAN 8**

Explain the effect when oxidation and reduction occurs to electrode-electrolyte interface.

Jelaskan kesan yang berlaku apabila pengoksidaan dan penurunan berlaku kepada antaramuka elektrod-elektrolit.

[4 marks]

[4 markah]

CLO1
C4**QUESTION 9****SOALAN 9**

Differentiate between Light Emitting Diodes and Laser Diodes.

Nyatakan perbezaan diod pemancar cahaya antara dan diod laser.

[4 marks]

[4 markah]

CLO1
C4**QUESTION 10****SOALAN 10**

Draw the pin configuration for USB type micro AB.

Lukis konfigurasi pin untuk USB jenis micro AB.

[4 marks]

[4 markah]

SECTION B : 60 MARKS**BAHAGIAN B : 60 MARKAH****INSTRUCTION:**

This section consists of THREE (3) essay questions. Answer ALL questions.

ARAHAH:

Bahagian ini mengandungi TIGA (3) soalan eseai. Jawab SEMUA soalan.

QUESTION 1**SOALAN 1**

- (a) List FOUR (4) medical equipments that used the application of mechanical sensor.

Senaraikan EMPAT (4) peralatan perubatan yang menggunakan aplikasi sensor mekanikal.

[4 marks]

[4 markah]

CLO1
C1

CLO1
C3

CLO1
C3

QUESTION 2**SOALAN 2**

- (a) By using a suitable diagram, explain what is hot and cold junction respectively.

Dengan menggunakan gambarajah yang sesuai, terangkan apakah yang dimaksudkan sebagai simpang panas dan simpang sejuk dalam pengesan thermocouple.

[6 marks]

[6 markah]

CLO1
C3

CLO1
C4

- (b) Explain clearly basic construction and operation for thermocouple.

Huraikan dengan jelas binaan asas dan operasi thermocouple.

[6 marks]

[6 markah]

- (c) At room temperature (25°C), the voltmeter in Figure B3 gives a reading of 2 V. The temperature of a material is measured using the Thermistor and the voltmeter now shows a reading of 4 V. If V_T is 20 V, β is 4000 K, R_C is 1k Ω and the voltmeter is ideal, what is the temperature of the measured material?

Pada suhu bilik (25°C), voltmeter pada Rajah B3 memberikan nilai 2V. Thermistor digunakan untuk mengukur suhu suatu bahan dan voltmeter memberikan bacaan 4 V. sekiranya voltan input, V_t adalah 20 V, β ialah 4000 K, R_C pula 1k Ω dan the voltmeter adalah ideal, berapakah suhu yang diukur untuk material tersebut?

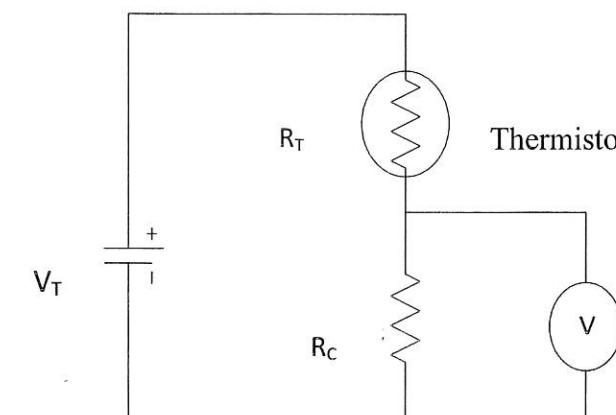


Figure 2 / Rajah 2

[8 marks]

[8 markah]

[8 marks]

[8 markah]

QUESTION 3**SOALAN 3**

- CLO1 (a) Differentiate radiometry and photometry.

Nyatakan apakah perbezaan antara radiometry dan photometry.

[4 marks]

[4 markah]

- CLO1 (b) List THREE (3) medical equipment that used the application of optical sensor.

Senaraikan TIGA(3) peralatan perubatan yang menggunakan aplikasi pengesan optik.

[3 marks]

[3 markah]

- CLO1 (c) Describe the LED basic operation as a light source in optical sensor

Huraikan operasi asas LED sebagai sumber cahaya dalam pengesan optik

[7 marks]

[7 markah]

- CLO1 (d) A beam of light is propagating through diamond and strikes the diamond-air interface at an angle of incidence of 28 degrees. Given:

Satu alur cahaya merambat melalui berlian dan terkena pada antara muka berlian-udara pada sudut insiden 28 darjah. Diberi:

n for air : 1.00

n for diamond : 2.42

n for water : 1.33

- i. Calculate the total internal reflection.

Kirakan pantulan dalam penuh.

- ii. Calculate the total internal reflection when diamond is surrounding by water.

Kirakan pantulan dalam penuh apabila berlian tersebut di kelilingi air.

[6 marks]

[6 markah]

SOALAN TAMAT