

**SULIT**



**BAHAGIAN PEPERIKSAAN DAN PENILAIAN  
JABATAN PENDIDIKAN POLITEKNIK DAN KOLEJ KOMUNITI  
KEMENTERIAN PENDIDIKAN MALAYSIA**

**JABATAN KEJURUTERAAN ELEKTRIK**

**PEPERIKSAAN AKHIR**

**SESI JUN 2018**

**DEE2023: SEMICONDUCTOR DEVICES**

**TARIKH : 01 NOVEMBER 2018**

**MASA : 11.15 PAGI - 1.15 TENGAHARI (2 JAM)**

---

Kertas ini mengandungi **DUA BELAS (12)** halaman bercetak.

Bahagian A: Objektif (10 soalan)

Bahagian B: Struktur (4 soalan)

Bahagian C: Esei (2 soalan)

Dokumen sokongan yang disertakan : Tiada

---

**JANGAN BUKA KERTAS SOALANINI SEHINGGA DIARAHKAN**

**(CLO yang tertera hanya sebagai rujukan)**

**SULIT**

**SECTION A: 10 MARKS**  
**BAHAGIAN A: 10 MARKAH****INSTRUCTION:**

This section consists of TEN (10) objective questions. Mark your answers in the OMR form provided.

**ARAHAN:**

Bahagian ini mengandungi SEPULUH (10) soalan objektif. Tandakam jawapan anda di dalam boring OMR yang disediakan.

CLO1

C1

1. Figure A1 shows the example of an atom structure. State the name of "X".

Rajah A1 menunjukkan contoh struktur atom. Nyatakan nama bahagian yang ditanda "X".

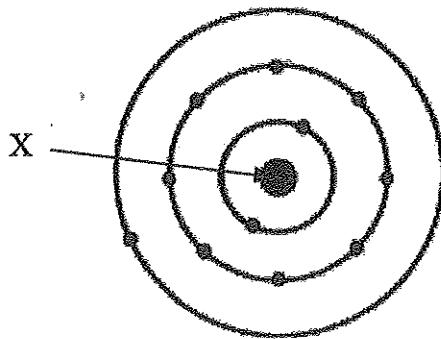


Figure A1/Rajah A1

- A. Electron  
*Elektron*
- B. Proton  
*Proton*
- C. Nucleus  
*Nukleus*
- D. Valence  
*Valensi*

- CLO1      2. Identify the factor that determine whether the material is a conductor, a semiconductor or an insulator.

*Kenal pasti faktor yang menentukan sesuatu bahan itu adalah pengalir, separuh pengalir atau penebat.*

- A.      Numbers of Electron  
*Bilangan Elektron*
- B.      Numbers of Shell  
*Bilangan Petala*
- C.      Size of Atom  
*Saiz Atom*
- D.      Numbers of electron valence.  
*Bilangan Elektron Valensi*

- CLO1      3. A half wave rectifier consists of \_\_\_\_\_.

*Penerus separuh gelombang terdiri daripada \_\_\_\_\_.*

- A.      One diode  
*Satu diod*
- B.      Two diodes  
*Dua diod*
- C.      Three diodes  
*Tiga diod*
- D.      Four diodes  
*Empat Diod*

- CLO2      4. Calculate the output voltage of a bridge rectifier that consists of four germanium diodes if the value of secondary is equal to 20Vp.

*Kirakan voltan keluaran penerus tetimbang yang mengandungi empat diod germanium jika nilai sekunder bersamaan 20Vp.*

- A.      18.6V
- B.      19.7V
- C.      19.4V
- D.      18.8V

- CLO1 | 5. Which of the following is NOT a transistor configuration?  
*Yang mana kah antara berikut BUKAN konfigurasi transistor?*

- A. Anode configuration  
*Konfigurasi Anod.*
- B. Base configuration  
*Konfigurasi Tapak*
- C. Gate configuration  
*Konfigurasi Get*
- D. Collector configuration  
*Konfigurasi Pengumpul*

- CLO2 | 6. Referring to Figure A6, derive the voltage equation for input circuit by using Kirchoff's voltage law.  
*Merujuk Rajah A6, dapatkan persamaan voltan untuk masukkan litar dengan menggunakan hukum voltan Kirchoff.*

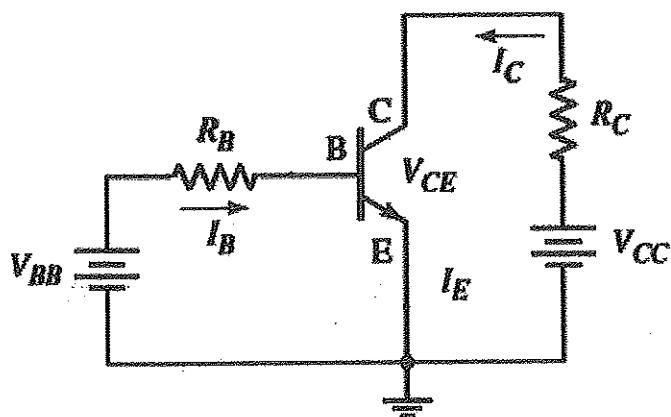


Figure A6/Rajah A6

- A.  $V_{CC} - I_C R_C = 0$
- B.  $V_{BB} - V_{RB} - V_{BE} = 0$
- C.  $V_{BB} - V_{RB} = 0$
- D.  $V_{CC} - V_{RC} - V_{CE} = 0$

CLO1

C2

7. Identify which statement below about negative feedback in amplifier is FALSE.

*Kenalpasti yang mana kenyataan di bawah adalah SALAH tentang suapbalik negatif.*

- A. Poor frequency response.  
*Tindak balas frekuensi yang lemah.*
- B. It increases the gain bandwidth  
*Meningkatkan gandaan lebar jalur*
- C. It improves gain stability.  
*Meningkatkan gandaan kestabilan.*
- D. It reduces linear distortion.  
*Mengurangkan herotan linear.*

CLO1

C1

8. The three terminals of Field Effect Transistor (FET) are Source, \_\_\_\_\_ and \_\_\_\_\_.

*Ketiga-tiga terminal asas Transistor Kesan Medan (FET) adalah terdiri daripada Sumber, \_\_\_\_\_ dan \_\_\_\_\_.*

- A. Anode, cathode  
*Anod, Katod*
- B. Gate, base  
*Get, Tapak*
- C. Gate, drain  
*Get, Salir*
- D. Collector, emitter  
*Pengumpul, pemancar*

- CLO1 | C2 9. Determine the suitable  $V_{GS}$  value to reach the maximum current of any JFET components.

*Tentukan nilai  $V_{GS}$  yang sesuai untuk mencapai arus maksimum bagi mana-mana komponen JFET.*

- A.  $V_{GS} > 0$
- B.  $V_{GS} < 0$
- C.  $V_{GS} = 0$
- D. None of the above  
*Tiada satu pun di atas*

- CLO1 | C1 10. State the number of terminals in TRIAC.

*Nyatakan jumlah terminal bagi TRIAK.*

- A. 2 or 3  
*2 atau 3*
- B. 2
- C. 3 or 4  
*3 atau 4*
- D. 3

**SECTION B : 60 MARKS**  
**BAHAGIAN B : 60 MARKAH**

**INSTRUCTION:**

This section consists of **FOUR (4)** structured questions. Answer **ALL** questions.

**ARAHAN:**

*Bahagian ini mengandungi EMPAT (4) soalan berstruktur. Jawab SEMUA soalan.*

**QUESTION 1**

**SOALAN 1**

CLO1  
C1

- a) State **THREE (3)** particles in an atom.

*Nyatakan TIGA (3) partikel yang terdapat di dalam atom.*

[3marks]  
[3markah]

CLO1  
C2

- b) Describe **TWO (2)** characteristics of N-type semiconductor and state **TWO (2)** examples of pentavalent impurities.

*Terangkan TWO (2) ciri-ciri semikonduktor jenis N dan nyatakan DUA (2) contoh bendasing pentavalen.*

[5 marks]  
[5 markah]

CLO2  
C3

- c) Illustrate the meaning of forward biased voltage and reverse biased voltage supplied across a P-N Junction.

*Illustrasikan maksud voltan pincang hadapan dan voltan pincang balikan yang dibekalkan pada simpang P-N.*

[7 marks]  
[7 markah]

**QUESTION 2**  
**SOALAN 2**CLO1  
C1

- (a) Draw the schematic symbol and physical structure for N-Channel of JFET.

*Lukiskan simbol skematik dan struktur fizikal bagi Saluran-N JFET.*[3 marks]  
[3 markah]CLO2  
C2

- (b) With the aid of a diagram, explain the operation of Depletion-Mode MOSFET.

*Dengan menggunakan bantuan gambarajah yang sesuai, terangkan operasi MOSFET Mod-Susutan*[5 marks]  
[5 markah]CLO2  
C3

- (c) Illustrate the operation of P-channel E-MOSFET circuit as a switch.

*Ilustrasikan operasi litar E-MOSFET saluran-P sebagai suis.*[7 marks]  
[7 markah]

**QUESTION 3****SOALAN 3**

- CLO1 (a) Draw the block diagram of feedback.

*Lukiskan gambarajah blok suapbalik*

[3 marks]  
[3 markah]

- CLO2 (b) Differentiate between positive and negative feedback.

*Bezakan antara suapbalik positif dan negatif.*

[6 marks]  
[6 markah]

- CLO2 (c) Figure B3(c) shows two stages amplifier connected in cascade where the gain at first stage ( $A_1$ ) is 25 and the output voltage at third stage ( $V_3$ ) is 5 V. The overall total gain for this amplifier is 1250. Calculate the input and output voltage of first stage ( $V_1$  &  $V_2$ ) and the gain at second stage ( $A_2$ ).

*Rajah B3(c) menunjukkan dua peringkat penguat disambung secara berturutan di mana gandaan peringkat pertama ( $A_1$ ) ialah 25 dan voltan keluaran di peringkat ketiga ( $V_3$ ) adalah 5V. Jumlah gandaan keseluruhan bagi penguat tersebut ialah 1250. Kirakan voltan masukan dan voltan keluaran di peringkat pertama ( $V_1$  &  $V_2$ ) dan gandaan pada peringkat kedua ( $A_2$ ).*

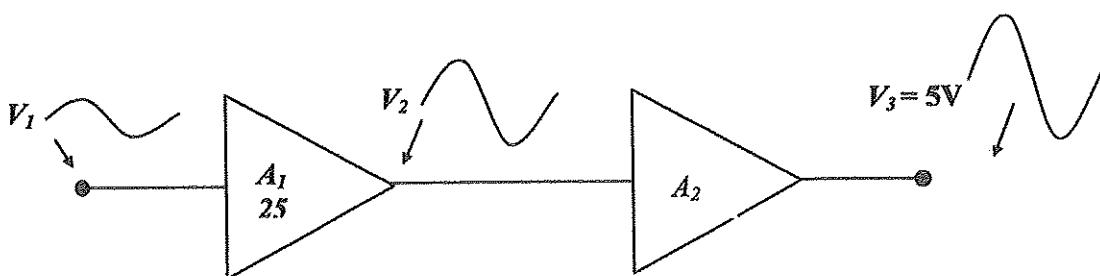


Figure B3(c) / Rajah B3(c)

[6 marks]  
[6 markah]

**QUESTION 4**  
**SOALAN 4**CLO1  
C1

- a) Draw the schematic symbol of SCR and UJT.

*Lukiskan simbol skematik bagi SCR dan UJT.*

[3 marks]  
[3 markah]

CLO2  
C3

- b) List TWO (2) conditions to turn off SCR operation.

*Senaraikan DUA (2) syarat untuk mematikan kendalian SCR.*

[5 marks]  
[5 markah]

CLO1  
C3

- c) Draw and label the I-V characteristic curve for SCR.

*Lukis dan labelkan lengkuk ciri I-V untuk SCR.*

[7 marks]  
[7 markah]

SULIT

**SECTION C: 30 MARKS**  
**BAHAGIAN C: 30 MARKAH**

**INSTRUCTION:**  
 This section consists of TWO (2) essay question. Answer ALL question.

**ARAHAN:**  
*Bahagian ini mengandungi DUA (2) soalan eseai. Jawab SEMUA soalan.*

**QUESTION 1****SOALAN 1**

- CLO2      By assuming that a silicon transistor is used, calculate the value of  $V_{BE}$ ,  $I_{BO}$ ,  $I_{CQ}$ ,  $V_{CEQ}$ , saturation current and cut off voltage as shown in Figure C1. Given  $V_{CC}=12V$ ,  $R_B=240K\Omega$ ,  $R_C=2.2K\Omega$  and  $C_1=C_2=10\mu F$ .

*Dengan menganggap transistor silikon digunakan, kira nilai  $V_{BE}$ ,  $I_{BO}$ ,  $I_{CQ}$ ,  $V_{CEQ}$ , arus tepu dan voltan takat alih seperti dalam Rajah C1. Diberi  $V_{CC}=12V$ ,  $R_B=240K\Omega$ ,  $R_C=2.2K\Omega$  dan  $C_1=C_2=10\mu F$ .*

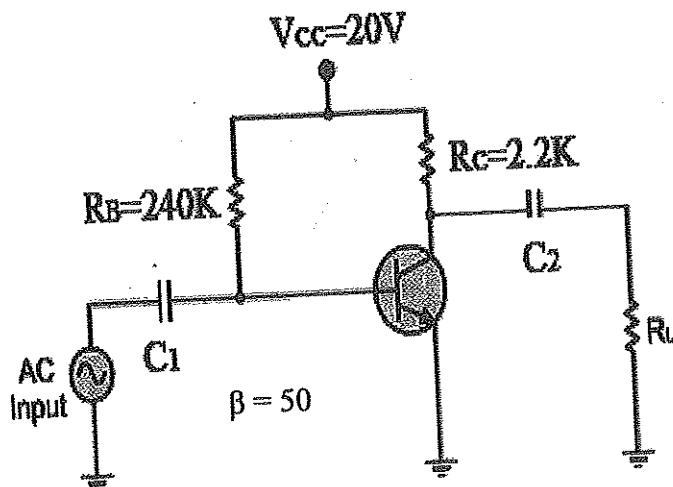


Figure C1/ Rajah C1

[15 Marks]  
 [15 markah]

**QUESTION 2**  
**SOALAN 2**

CLO2  
C3 A Full-wave Rectifier (Bridge) operates with a silicon diode. Draw the circuit with the input and output waveform and explain the full operation of the circuit.

*Satu Penerus Gelombang penuh (Titik) beroperasi menggunakan diod silicon. Lukiskan litar tersebut dengan isyarat gelombang masukan dan keluaran dan terangkan tentang kendalian penuh litar itu.*

[15 Marks]  
[15 markah]

**SOALAN TAMAT**